

BJT: Mathematical Problems


Faculty: Aroni Ghosh (AGS)

Course No: CSE 251

Course Title: Electronic Devices and Circuits

Example 1


Find expression of **f**

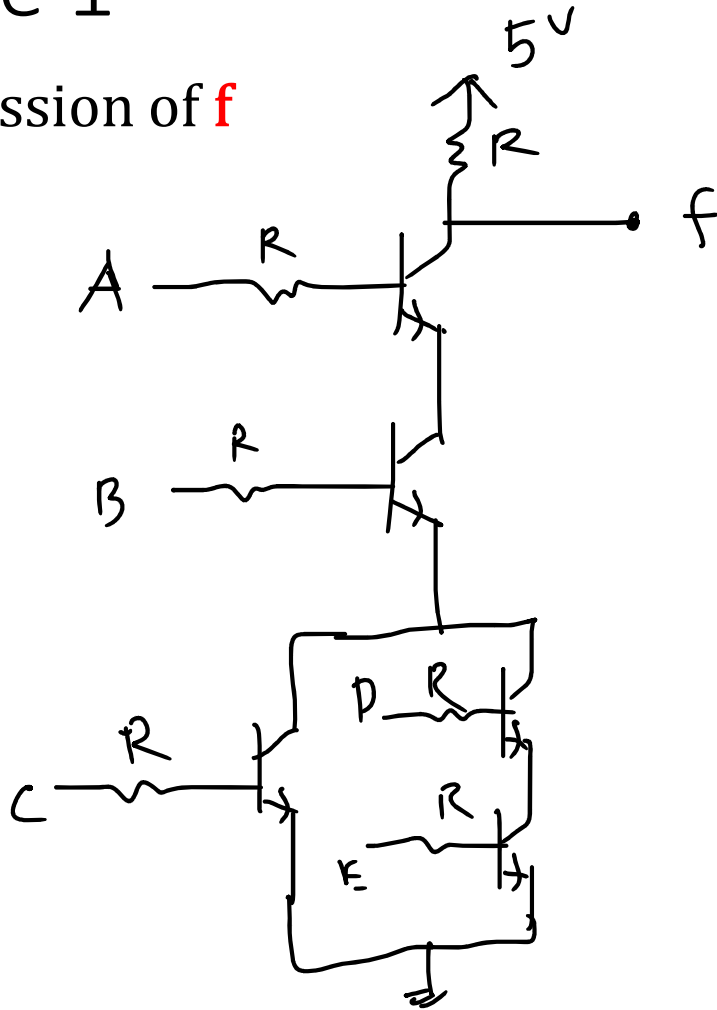

$$f = \overline{AB(C + DE)}$$

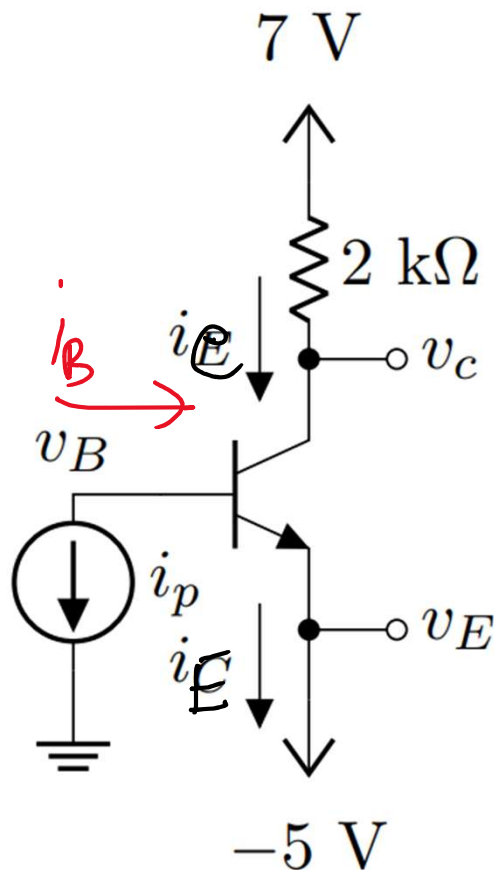Example 2

Analyze the circuit above to find i_B , i_C , i_E and v_{CE} . Assume, the BJT is in **Saturation**. Here, use the Method of Assumed State. You must validate your assumptions. Assume, $i_p = -1\text{ mA}$



Solⁿ:

$$i_B = -i_p = -(-1) = 1\text{ mA}$$

$$V_E = -5\text{ V}$$

In saturation mode

$$\text{So, } V_{BE} = 0.8\text{ V \&}$$

$$V_{CE} = 0.2\text{ V}$$

$$\Rightarrow V_C - V_E = 0.2\text{ V} \Rightarrow V_C = 0.2 + V_E = 0.2 + (-5)$$

$$\therefore V_C = -4.8\text{ V}$$

$$i_C = (7 - V_C)/2 = (7 + 4.8)/2 = 5.9\text{ mA}$$

$$i_E = i_C + i_B = 6.9\text{ mA}$$

Verify:


$$\beta = 100$$

$$i_C / i_B = 5.9 / 1 = 5.9 < \beta$$

\therefore Assumption Correct

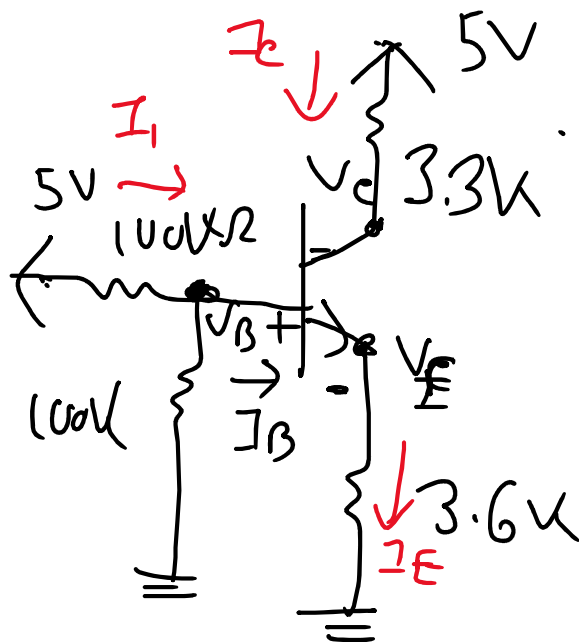Example 3

Analyze the circuit above to find i_B , i_C , i_E and v_{CE} . Here, use the Method of Assumed State. You must validate your assumptions. $\beta = 100$, $\alpha = (\beta)/(\beta+1) = 0.99$



Solⁿ:

Assume, Active mode

So, $V_{BE} = 0.7 \text{ V}$ & $I_C = \beta I_B = \alpha I_E$

Nodal analysis (at base terminal):

$$\frac{V_B - 5}{100 \text{ k}\Omega} + \frac{V_B}{100 \text{ k}\Omega} + I_B = 0 \text{ --- (1)}$$

KVL:

$$5 - 0 = 100 I_1 + V_{BE} + 3.6 I_E$$

$$5 = 100 \frac{5 - V_B}{100 \text{ k}\Omega} + 0.7 + 3.6 \frac{\beta}{\alpha} I_B \text{ --- (2)}$$

Solving, eqⁿ 1 & 2, $V_B = 2.28 \text{ V}$, $I_B = 4.35 \text{ uA}$

$I_C = \beta I_B = 0.435 \text{ mA}$, $I_E = I_C + I_B = 0.43935 \text{ mA}$

$V_C = 5 - 3.3 I_C = 3.5645 \text{ V}$


$V_E = 3.6 I_E = 1.582 \text{ V}$

$V_{CE} = V_C - V_E = 1.983 \text{ V}$

So, $V_{CE} > 0.2 \text{ V}$

\therefore Assumption Correct!

Example 4

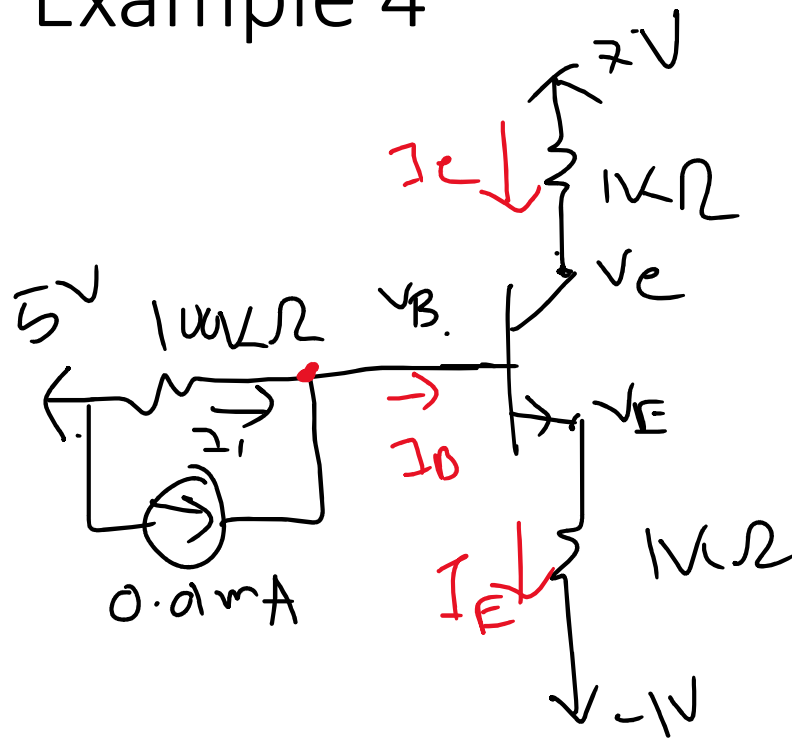

Analyze the circuit above to find v_{CE} . Here, use the Method of Assumed State. You must validate your assumptions. $\beta = 100$, $\alpha = (\beta)/(\beta+1) = 0.99$

Solⁿ:

Assume, Active mode

So, $V_{BE} = 0.7 \text{ V}$ & $I_C = \beta I_B = \alpha I_E$

KCL (at base terminal):

$$I_1 + 0.01 = I_B$$

$$\therefore I_1 = I_B - 0.01$$

KVL:

$$5 - (-1) = 100I_1 + V_{BE} + 1I_E$$

$$6 = 100(I_B - 0.01) + 0.7 + \frac{\beta}{\alpha}I_B \quad \text{--- (2)}$$

$$\therefore I_B = 0.0313 \text{ mA}$$

$$I_C = \beta I_B = 3.13 \text{ mA}, I_E = I_C + I_B = 3.1613 \text{ mA}$$

$$V_C = 7 - 1I_C = 3.87 \text{ V}$$


$$V_E = 1I_E - 1 = 2.16 \text{ V}$$

$$V_{CE} = V_C - V_E = 1.709 \text{ V}$$

$$\text{So, } V_{CE} > 0.2 \text{ V}$$

\therefore Assumption Correct!

Example 5

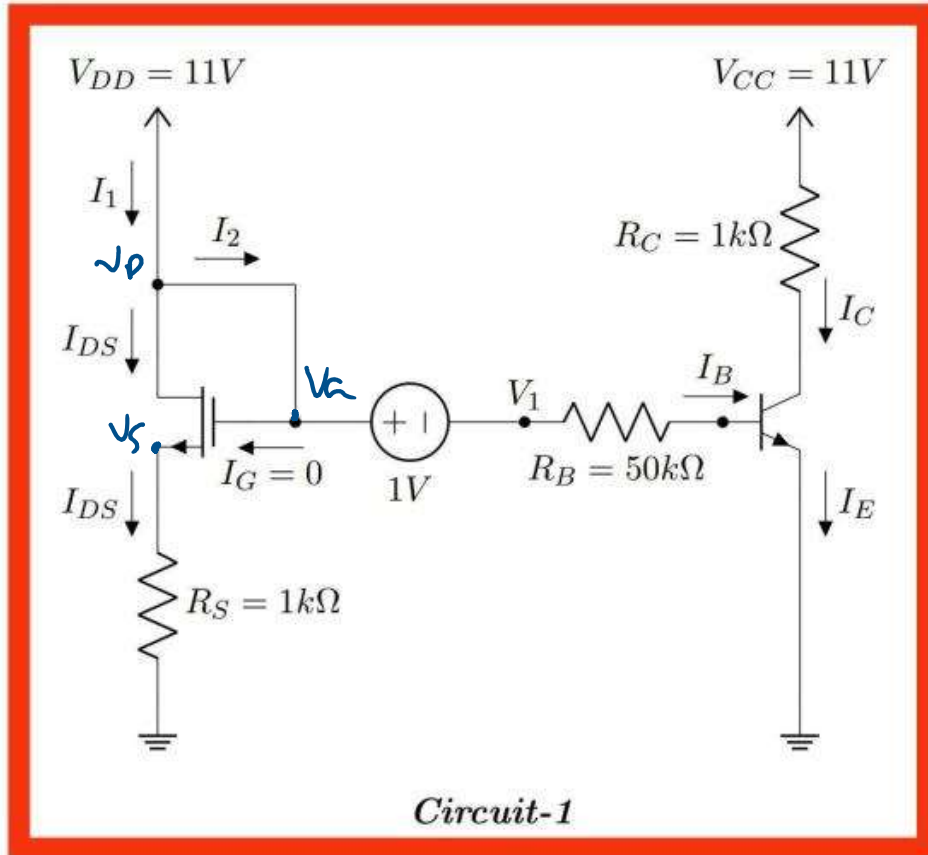

- Find out the gate voltage of the MOSFET.
- Calculate V_1 .
- Find out the expression for V_{GS} , V_{DS} and V_{OV} .
- Find the operating mode of the MOSFET using the expressions from ©. [Hint: You don't need any assumption]
- Calculate I_{DS} and V_{DS} using the given parameters.
- Assume that the BJT is in the saturation mode. Now, calculate I_B , I_C , I_E . You must **validate** the given assumption.

The MOSFET and BJT in Circuit-1 have the following parameters,

$k = 5 \text{ mA/V}^2$, $V_T = 0.7 \text{ V}$, $\beta = 85$, $V_{BE(\text{Active})} = 0.7 \text{ V}$, $V_{BE(\text{Saturation})} = 0.8 \text{ V}$, $V_{CE(\text{Saturation})} = 0.2 \text{ V}$

Solⁿ:

a) $V_G = V_D = 11 \text{ V}$ [Drain & Gate short]

b) Applying voltage difference formula, $V_G - V_1 = 1 \Rightarrow V_1 = V_G - 1 = 11 - 1 \therefore V_1 = 10 \text{ V}$

c) Assume, $I_{DS} = x$

Now, $V_S = 1 \text{ k}\Omega \times I_{DS} = I_{DS} \therefore V_S = x$

$V_{GS} = V_G - V_S = 11 - x$, $V_{OV} = V_{GS} - V_T = 11 - x - 0.7 = 10.3 - x$

$V_{DS} = V_D - V_S = V_G - V_S = V_{GS} = 11 - x$ [as $V_D = V_G$]

d) As Drain & Gate are short ($V_D = V_G$ or $V_{DS} = V_{GS}$), for this MOSFET, V_{DS} will be always greater than V_{OV} ($= V_{GS} - V_T$)

So, the MOSFET is in saturation mode

$$I_{DS} = \frac{k}{2} V_{OV}^2$$
$$x = \frac{5}{2} (10.3 - x)^2$$

$\therefore x = 12.54 \text{ or } 8.46$

If $x = 12.54$, then $V_{OV} = 10.3 - 12.54 = -2.24 \text{ V}$

But V_{OV} cannot be negative as $V_{OV} < 0$ means $V_{GS} < V_T$ which will result the MOSFET to be in cutoff mode.

$\therefore x = 8.46$

Solⁿ:

e) $I_{DS} = x = 8.46 \text{ mA}$

$V_{DS} = 11 - x = 2.54 \text{ V}$

f) Given, BJT is in saturation mode

So, $V_{BE} = 0.8 \text{ V}$ & $V_{CE} = 0.2 \text{ V}$

$V_E = 0 \text{ V}$ (ground connected) $\rightarrow V_B = 0.8 \text{ V}, V_C = 0.2 \text{ V}$

$$I_B = \frac{V_1 - V_B}{R_B} = \frac{10 - 0.8}{50 \text{ k}\Omega} = 0.184 \text{ mA}$$


$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{11 - 0.2}{1 \text{ k}\Omega} = 10.8 \text{ mA}$$

$$I_E = I_C + I_B = 10.984 \text{ mA}$$

$$\frac{I_C}{I_B} = 58.7 < \beta$$

So, Assumption Correct!

Example 5

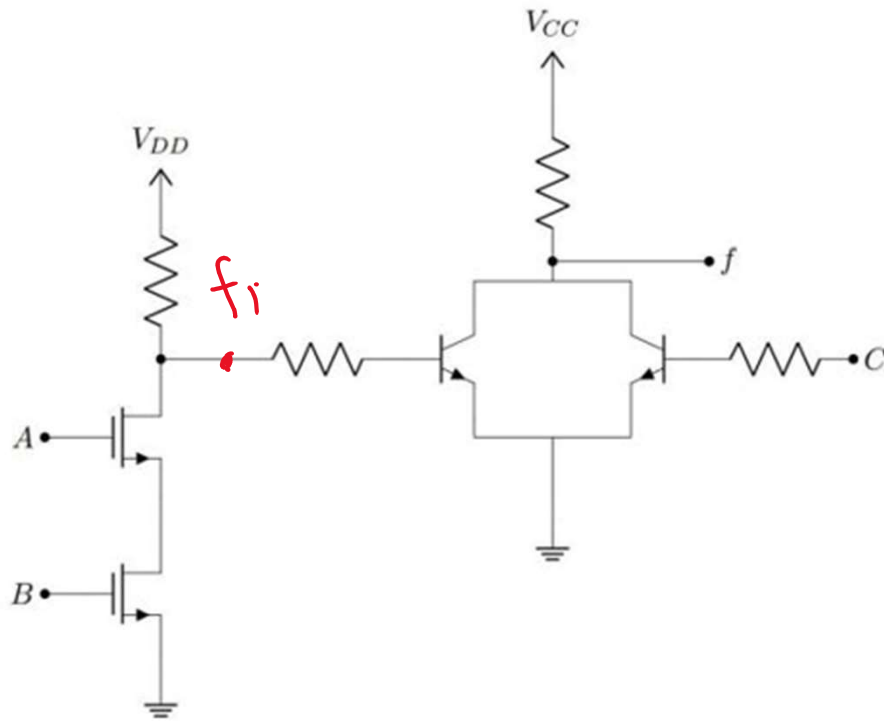


$$f_i = \overline{AB}$$

$$f = \overline{f_i + C}$$
$$= \overline{\overline{AB} + C}$$

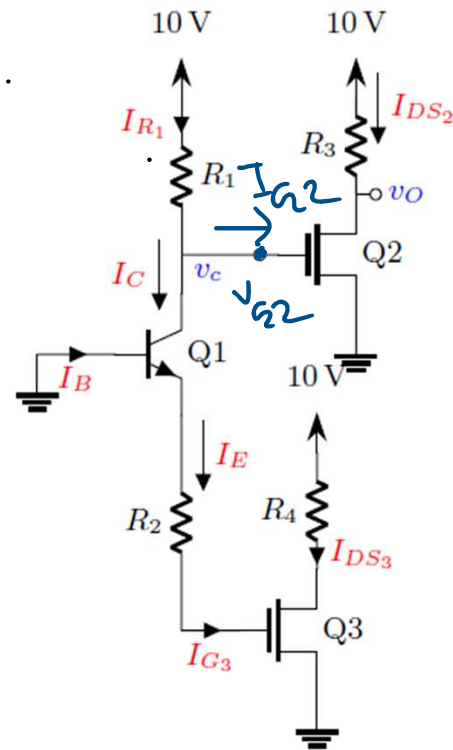Example 6

For the following circuit, $R_1 = 1\text{k}\Omega$, $R_2 = 2\text{k}\Omega$, $R_3 = 3\text{k}\Omega$, $R_4 = 4\text{k}\Omega$



For BJT

$$\beta = 100$$

$$\alpha = 0.99$$

$$v_{BE(\text{Active})} = 0.7\text{ V}$$

$$v_{BE(\text{Saturation})} = 0.8\text{ V}$$

$$v_{CE(\text{Saturation})} = 0.2\text{ V}$$

for MOSFETs

$$V_T = 1\text{ V}$$

$$k = 5\text{ mA/V}^2$$

- [5 marks] Analyze the circuit to determine the values of I_C , I_B , I_E , v_C .
- [5 marks] Analyze the circuit to determine the value of I_{DS2} , v_O .

Solⁿ:

a) As gate current of MOSFET is zero

b) So, $I_{G3} = 0 \text{ mA} = I_E$

$\therefore I_B = 0 \text{ mA}, I_C = 0 \text{ mA}$

So, the BJT is in cutoff mode

$$V_C = 10 - 1 \cdot I_{R1} = 10 - 1 \cdot (I_C + I_{G2}) = 10 - 1 \cdot (0 + 0) = 10 \text{ V}$$

d) Assume, saturation mode

$V_{G2} = V_C = 10 \text{ V}$ [Collector of BJT and Gate of MOSFET (top one) are short]

$$V_{GS} = V_{G2} - V_S = 10 - 0 = 10 \text{ V}, \quad V_{OV} = 10 - 1 = 9 \text{ V}$$

$$\begin{aligned} I_{DS2} &= \frac{k}{2} V_{OV}^2 \\ &= \frac{5}{2} (9)^2 = 202.5 \text{ mA} \end{aligned}$$

$$V_{DS} = 10 - 3 \cdot I_{DS2} = -597.5 \text{ V}$$

$$V_{DS} < V_{OV}$$

\therefore Assumption wrong!

Solⁿ:

Now, assume triode mode

If $I_{DS2} = x$, $V_{DS} = 10 - 3I_{DS2} = 10 - 3x$

$$I_{DS2} = \frac{k}{2} (2(V_{GS} - V_T)V_{DS} - V_{DS}^2)$$
$$x = \frac{5}{2} (2(10 - 1)(10 - 3x) - (10 - 3x)^2)$$

$x = 3.31$ or -2.69

As current cannot be negative, so $x = 3.31$

$I_{DS2} = x = 3.31 \text{ mA}$

$V_{DS} = 10 - 3x = 0.07 \text{ V}$


$V_{DS} < V_{OV}$

\therefore Assumption correct!

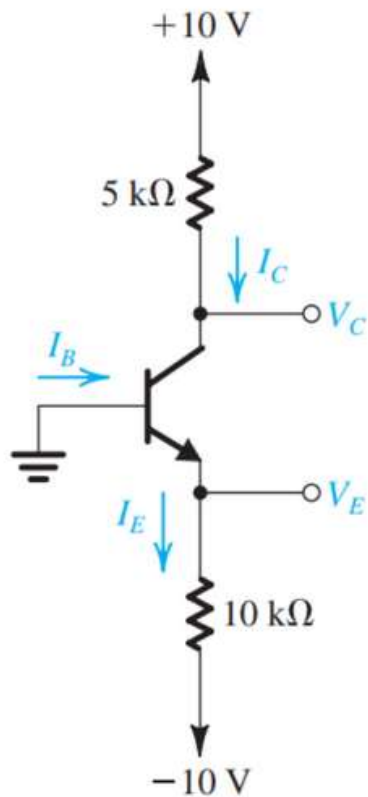Example 7

In the circuit shown in Fig. the voltage at the emitter was measured and found to be -0.7 V .

If $\beta = 50$, find I_E , I_B , I_C , and V_C .



Solⁿ:

$$I_E = \frac{V_E - (-10)}{10\text{ k}\Omega} = \frac{-0.7 + 10}{10} = 0.93\text{ mA}$$
$$\alpha = \frac{\beta}{\beta + 1} = \frac{50}{51}$$

Assuming forward active mode,

$$I_C = \alpha I_E = 0.9118\text{ mA}$$

$$V_C = 10 - 5I_C = 5.44\text{ V}$$

So, $V_{CE} = V_C - V_E = 6.141\text{ V} > 0.2\text{ V}$ so, forward active mode

Assumption correct!

$$I_B = I_E - I_C = 18.2\text{ }\mu\text{A}$$

Example 8

Analyze the circuit above to find i_C , i_E , i_B , and v_{o1} . Here, use the Method of Assumed State.

Solⁿ:

Assuming forward active mode,

$$V_{BE} = 0.7 \text{ V} \rightarrow V_B - V_E = 0.7 \text{ V} \therefore V_B = 0.7 \text{ V} = V_C$$


So, $V_{CE} = V_C - V_E = 0.7 \text{ V} > 0.2 \text{ V}$ so, forward active mode
Assumption correct!

$$i_C = \frac{5 - V_C}{1 \text{ k}\Omega} = \frac{5 - 0.7}{1} = 4.3 \text{ mA}$$

$$I_C = \alpha I_E$$

$$\therefore I_E = 4.3 / 0.995 = 4.3216 \text{ mA}$$

$$I_B = I_E - I_C = 21.6 \text{ }\mu\text{A}$$

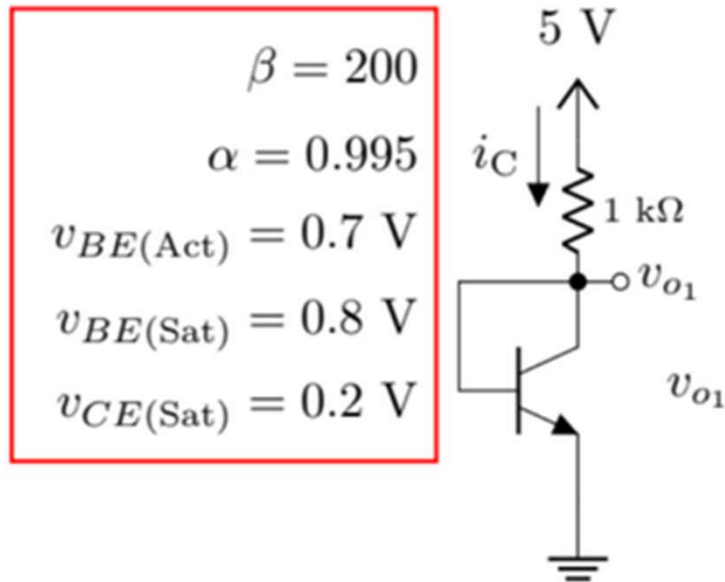

Example 9

Solⁿ:

Assuming Active mode,

$$V_{BE}=0.7\text{ V} \rightarrow V_B - V_E = 0.7\text{ V} \therefore V_E = (-1) - 0.7\text{ V} = -1.7\text{ V}$$

$$I_B = \frac{0 - V_B}{R_B} = \frac{0 - (-1)}{500\text{ k}\Omega} = 2\text{ }\mu\text{A}$$

$$I_E = \frac{V_E - (-3)}{R_E} = \frac{-1.7 + 3}{4.8\text{ k}\Omega} = 0.271\text{ mA}$$

$$I_C = I_E - I_B = 0.269\text{ mA}$$

$$\beta = \frac{I_C}{I_B} = 134.5$$


$$\alpha = \frac{I_C}{I_E} = 0.9926$$

$$V_{CE} = V_C - V_E = 3 - (-1.7) = 4.7\text{ V} > 0.2\text{ V} \text{ so, forward active mode}$$


Assumption correct!

In the circuit shown in adjacent figure, the values of measured parameters are shown.

Determine β , α , and the other labeled currents and voltages.

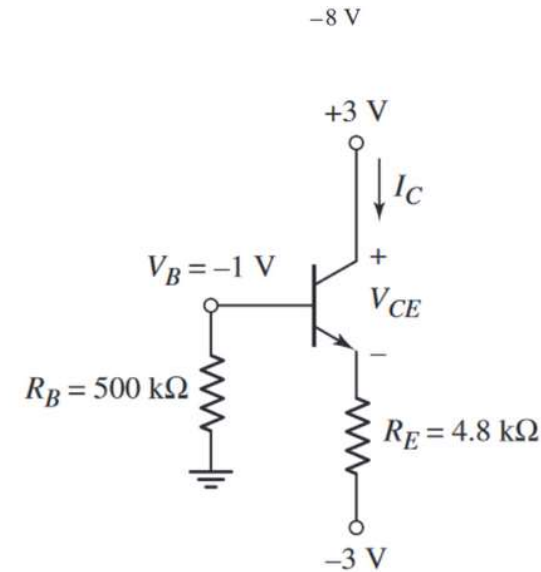

Example 10

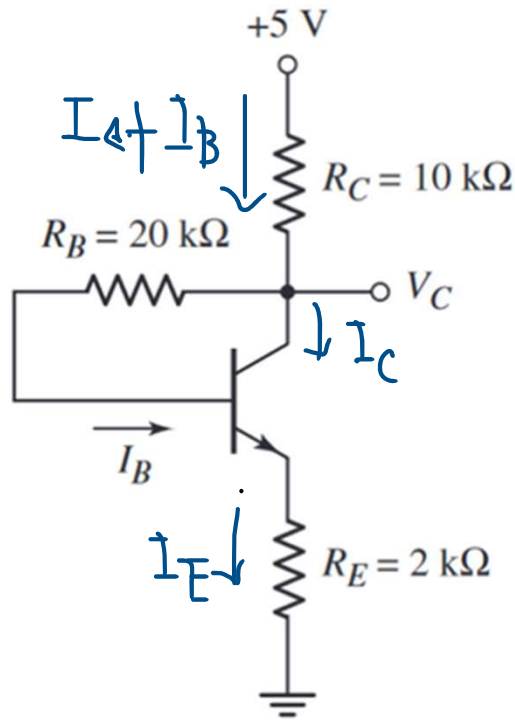

$\beta = 75$. Find the labelled voltages and currents.

Solⁿ:

Assuming Active mode,

$$V_{BE} = 0.7 \text{ V}$$

$$5 - 0 = R_C(I_C + I_B) + R_B I_B + V_{BE} + R_E I_E$$

$$5 = 10(\beta I_B + I_B) + 20I_B + 0.7 + 2 \frac{\beta}{\alpha} I_B$$

$$\therefore I_B = 4.604 \text{ uA}$$

$$I_C = \beta I_B = 0.345 \text{ mA}$$

$$V_C = 5 - 10(I_C + I_B) = 1.5 \text{ V}$$

$$I_E = I_C + I_B = 0.3496 \text{ mA}$$

$$V_E = 2I_E = 0.7 \text{ V}$$

$V_{CE} = V_C - V_E = 1.5 - 0.7 = 0.8 \text{ V} > 0.2 \text{ V}$ so, forward active mode
Assumption correct!