

Zener Diode Problems

Lecture 10

Course No: CSE 251

Course Title: Electronic Devices and Circuits

Course instructor:

Aroni Ghosh (AGS)

Lecturer, CSE, Brac University



Example 1

The Zener diode is specified as $V_{Z0}=3V$, $r_Z=0\Omega$, $I_{ZK}=1mA$. The load current can vary from 0mA to 50mA. The source has a nominal value of 5V and can vary $\pm 10\%$.

a) Find $V_S(\min)$, $V_S(\max)$, $I_L(\min)$, $I_L(\max)$


So: 10% of $5V = 0.5V$

$V_S(\min) = 5 - 0.5 = 4.5V$

$V_S(\max) = 5 + 0.5 = 5.5V$

$I_L(\min) = 0\text{ mA}$

$I_L(\max) = 50\text{ mA}$

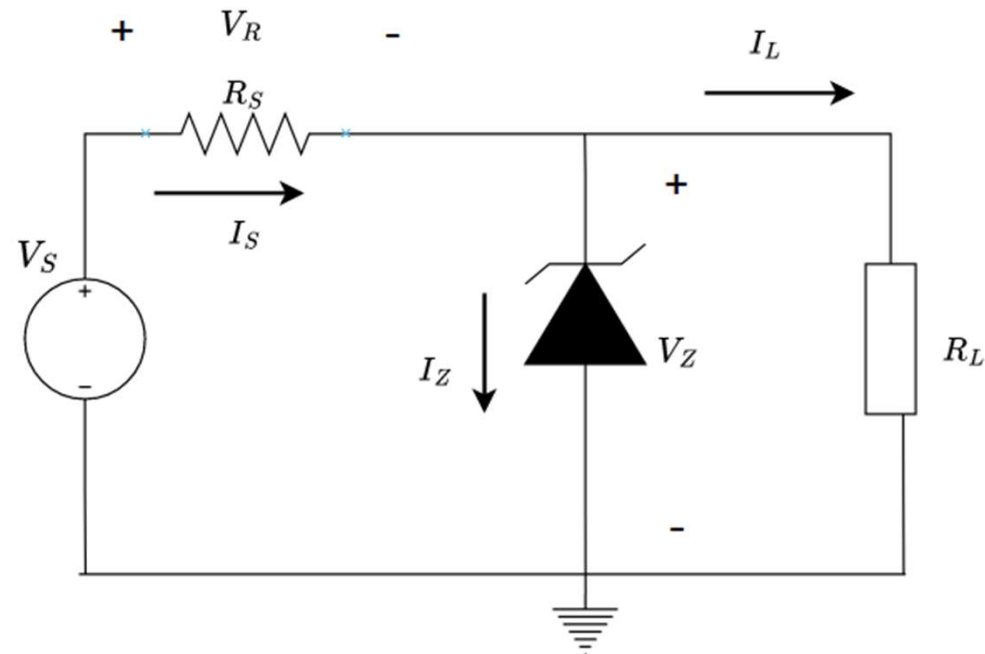

Example 1

b) What is the worst case I_L , I_Z and V_s ?

Sol: In worst case, I_{ZK} will flow through the zener diode. [If the current falls below this, the regulation will not be maintained]

$$\text{KCL} \Rightarrow I_Z = I_S - I_L$$
$$\text{and } I_S = (V_s - V_L) / R_s$$

So, I_Z is minimum when I_L is maximum. and V_s is minimum.

$$\text{Worst case} \Rightarrow I_L = I_L(\text{max}) = 50\text{mA}$$

$$I_Z = I_Z(\text{min}) = I_{ZK} = 1\text{ mA}$$

$$V_s = V_s(\text{min}) = 4.5\text{V}$$

c) For worst case, what is the value of I_s ?

$$\text{Sol: } I_s = I_Z + I_L = 1 + 50 = 51\text{mA}$$

Example 1

d) For worst case, what is the value of V_R ?

Sol: In worst case scenario, the zener diode will barely maintain its voltage.

$$\text{So, } V_L = V_Z = V_{Z0} + I_Z r_Z = 3V$$

$$V_R = V_S - V_L = 4.5 - 3 = 1.5V$$

e) Find the value of R_S , for which the Zener diode maintains regulation in worst case scenario.

$$\text{Sol: } R_S = V_R / I_S = 1.5V / 51mA = 30\Omega$$

Example 2

The Zener diode is specified as $V_{Z0}=3V$, $r_Z=0\Omega$, $I_{ZK}=1mA$.
 $R_S=100\Omega=0.1k\Omega$, $R_L=10k\Omega$.

Find the minimum value of V_S for which the Zener diode maintains regulation.

In worst case, $I_Z=I_{ZK}=1mA$

$$I_L=V_L/R_L=3V/10k\Omega=0.3mA$$

$$KCL \rightarrow I_S = I_Z + I_L = 1 + 0.3 = 1.3mA$$


$$I_S = (V_S - V_L)/R_S$$

$$\Rightarrow 1.3mA = (V_S - 3)/0.1k\Omega$$

$$\text{So, } V_S = 3.13V$$

As in worst case scenario, I_Z is minimum which happens when I_L is maximum. and V_S is minimum,

$$V_S(\min) = 3.13V$$

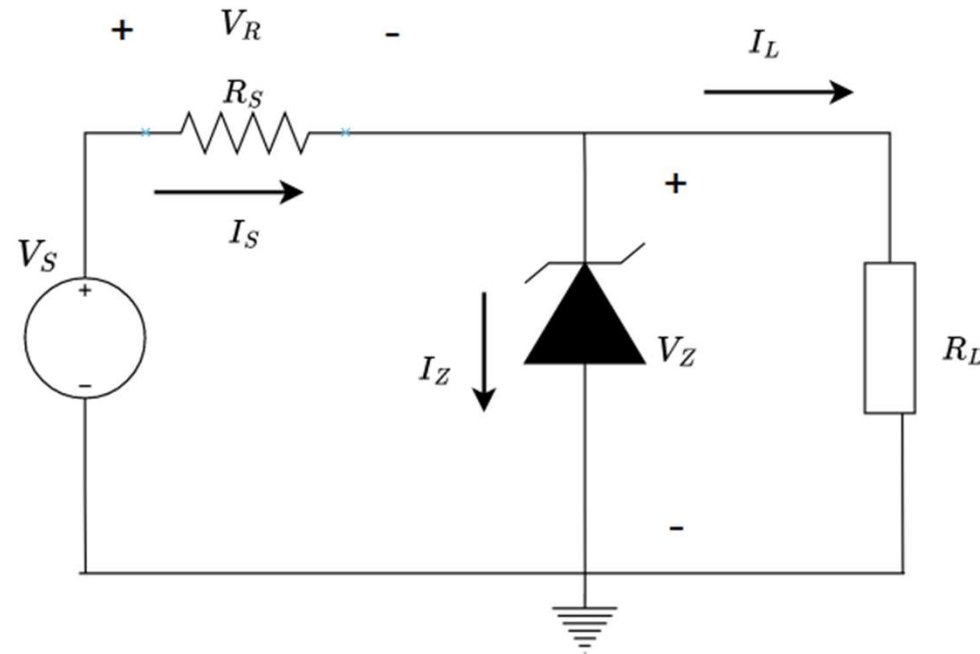

Example 3

The Zener diode is specified as $V_{Z0}=3V$, $r_Z=0\Omega$, $I_{ZK}=1mA$.
 $R_S=100\Omega=0.1k\Omega$. The source has a nominal value of 5V and can vary $\pm 10\%$.

Find the minimum value of R_L for which the Zener diode maintains regulation.

In worst case, $I_Z=I_{ZK}=1mA$

$$V_L = V_Z = V_{Z0} + I_Z r_Z = 3V$$

$$10\% \text{ of } 5V = 0.5V$$


In worst case, $V_S=V_S(\min)=5-0.5=4.5V$

$$I_S=(V_S-V_L)/R_S=(4.5-3)/0.1k\Omega=15mA$$


$$I_L = I_S - I_Z = 15-01 = 14mA$$

$$R_L = V_L / I_L = 3V / 14mA = 214\Omega$$

$$R_L(\max) = 214\Omega$$

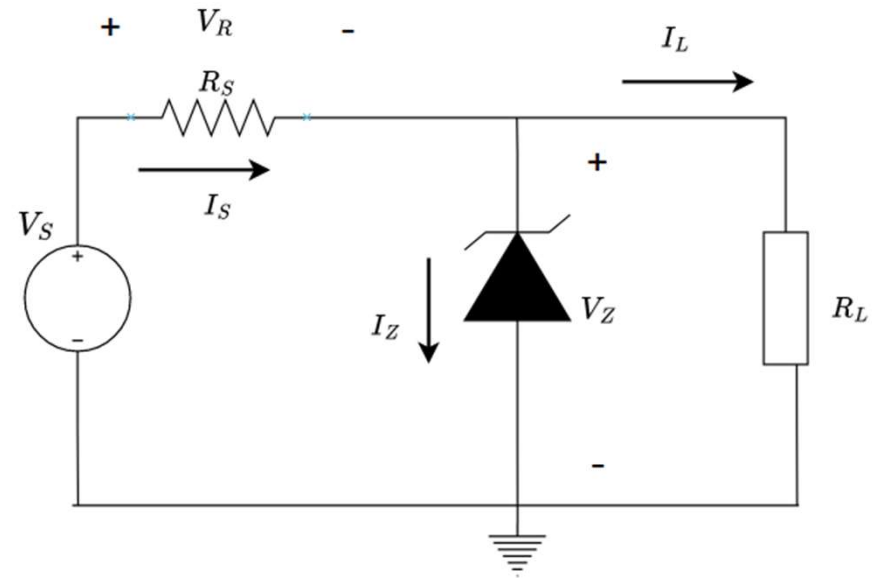


Example 4

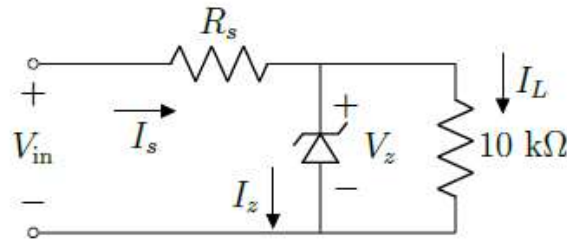

In the circuit, the input voltage V_{in} has a nominal voltage of 10 V with a fluctuation of $\pm 10\%$. The Zener diode in the circuit is specified with parameter $V_z = 5.75$ V at $I_z = 5$ mA, $r_z = 0.05$ k Ω , and $I_{zk} = 0.3$ mA.

- (a) Compute the Zener diode parameter V_{z0} . [2]
- (b) Identify the worst-case conditions and calculate the Zener current (I_z), Zener voltage (V_z), and the input voltage in this worst-case scenario. [1+1+1+1]
- (c) Calculate the load current I_L and the source current I_s in the worst-case conditions. [2]
- (d) Design the circuit, i.e., find the value of R_s , such that even in the worst-case scenario voltage regulation is maintained. [2]

Example 5

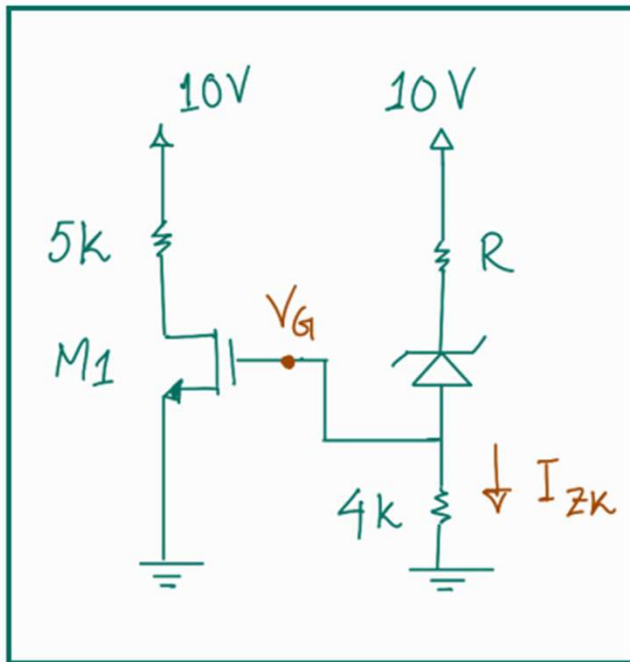

Given, $R_2 = 100\Omega$, $I_{ZK} = 1.2\text{ mA}$
 $V_{Z0} = 3.3\text{ V}$

(Q1) : Find the maximum value of R so that the zener diode stays in knee-voltage condition

(Q2) : Find the operating region of the Mosfet $M1$ using the value of R in (Q1).

$$K_n = 1\text{ mA/V}^2$$
$$V_T = 0.2\text{ V}$$

**Thank
You**