
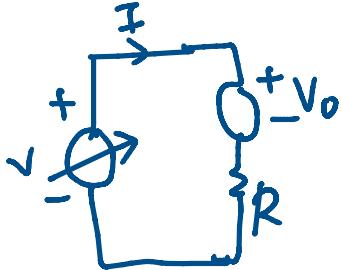


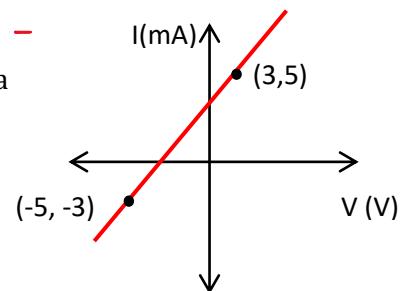Q1. Design the device from the given I-V characteristics assuming you have two 1V sources and three $3\text{k}\Omega$ resistors.

Sol: As the graph doesn't go through origin, we can assume the device is a Voltage Source in series with a Resistor.



$$V = IR + V_0 \\ I = \frac{V}{R} - \frac{V_o}{R} \quad \dots \dots (1)$$




The straight-line equation of the given I-V curve-

$$\frac{I - 5}{V - 3} = \frac{5 - (-3)}{3 - (-5)} = 1$$


$$\text{or, } I = V + 2 \quad \dots \dots (2)$$

From equation (1) and (2), $\frac{1}{R} = 1 \therefore R = 1\text{k}\Omega$ and $-\frac{V_o}{R} = 2 \therefore V_o = -2V$

So, the device is:

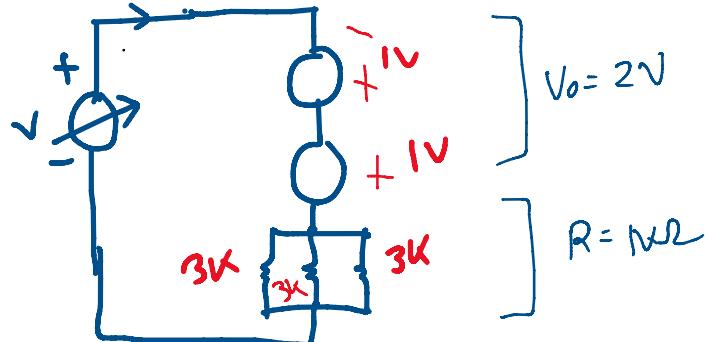

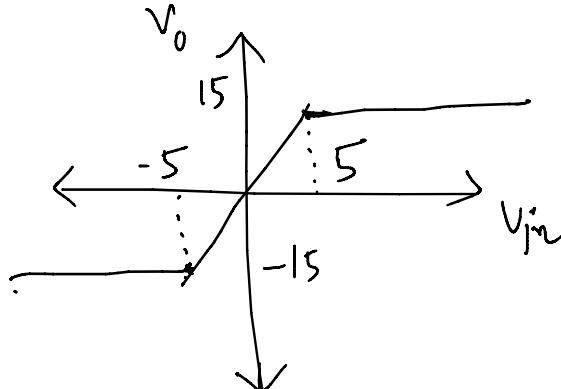Q2. Find out the valid range of V_{in} , V_o and the value of open loop gain from the following VTC-



Soln:

The valid region of an amplifier is the linear region not the saturation regions. So, valid input range is:

$$-5 \leq V_{in} \leq 5$$



Valid output range is:

$$-15 \leq V_o \leq 15$$


gain = A = slope of linear region

$$\text{Slope} = \frac{15 - (-15)}{5 - (-5)} = \frac{30}{10} \\ \therefore A = 3$$

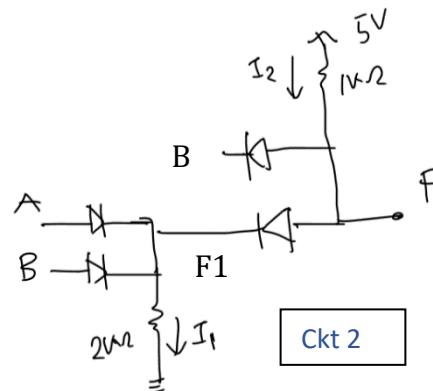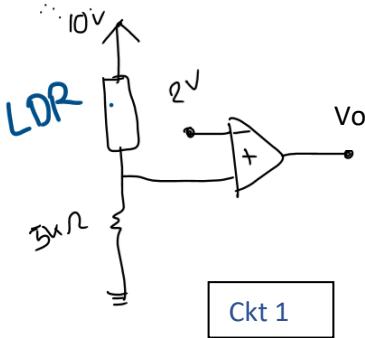Q3. For ckt 1, Assume, light is on \rightarrow LDR resistance = $1k\Omega$ \rightarrow Op-amp output, $V_o = A$
 light is off \rightarrow LDR resistance = $50 k\Omega$ \rightarrow Op-amp output, $V_o = B$
 $V_{S+} = 10V, V_{S-} = -5V$, Find the value of F, I_1 and I_2





Sol:

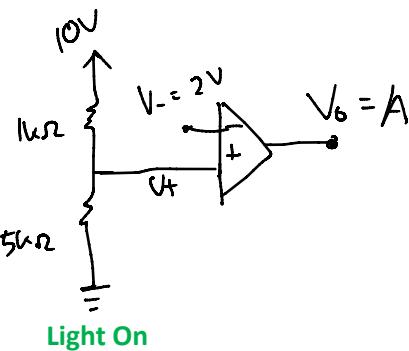

When light is on, $V_+ = \frac{5k\Omega}{5k\Omega + 1k\Omega} * 10V = 8.33V$
 $V_- = 2V$, So $V_+ > V_- \therefore V_o = A = V_{S+} = 10V$

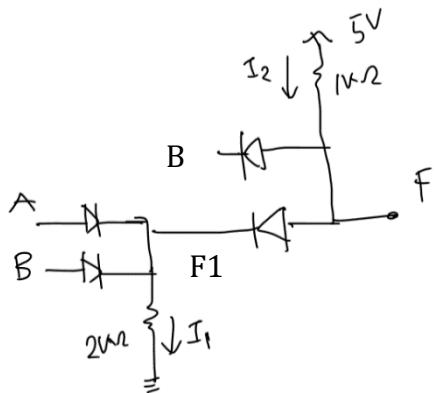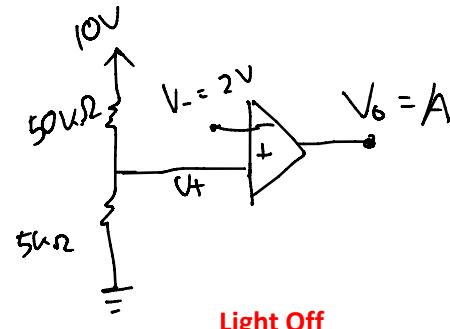When light is off, $V_+ = \frac{5k\Omega}{5k\Omega + 50k\Omega} * 10V = 0.909V$
 $V_- = 2V$, So $V_+ < V_- \therefore V_o = B = V_{S-} = -5V$



Now,


$$\begin{aligned} F1 &= A \text{ or } B \\ &= \max(A, B) \\ &= \max(10V, -5V) = 10V \end{aligned}$$

$$\begin{aligned} F &= B \text{ and } F1 \\ &= \min(B, F1) \\ &= \min(-5V, 10V) \\ \therefore F &= -5V \end{aligned}$$

$$\text{Current, } I_1 = \frac{F1}{2k\Omega} = \frac{10V}{2k\Omega} = 5mA$$

$$\text{Current, } I_2 = \frac{5V - F}{1k\Omega} = \frac{5V - (-5V)}{1k\Omega} = 10mA$$

Q4. Draw VTC of the following circuit.

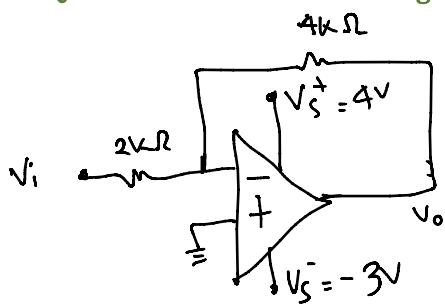


Sol: This is an inverting op-amp.

$$V_o = -\frac{R_2}{R_1} V_i$$

So. gain = $-\frac{R_2}{R_1} = -\frac{4k\Omega}{2k\Omega} = -2$ = slope of linear region in VTC


VTC:

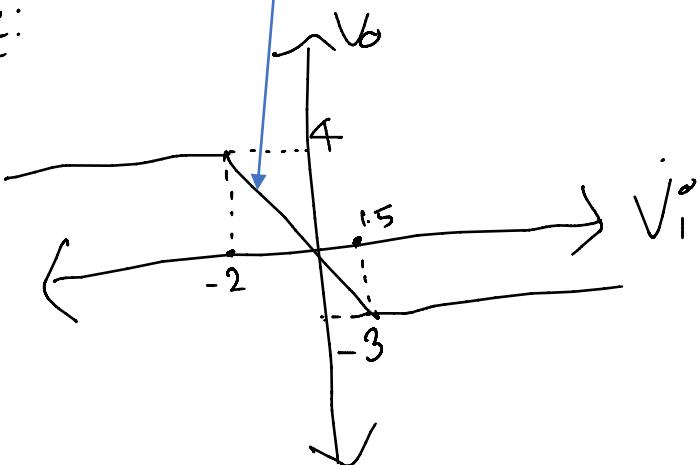

Q5. Implement $f = (A + \bar{B})C + \bar{D}$ with diode logic gates.

Sol: There are **not gates** (\bar{B}, \bar{D}) in this expression. But inverter (not gate) cannot be implemented by **diodes**. So, the given function cannot be implemented by diode logic gates.

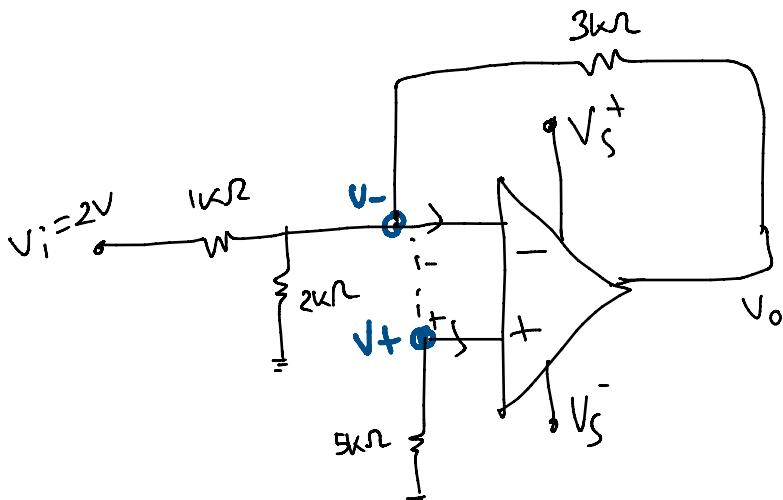Q6. Find V_o from the given op-amp circuit.



Sol:

In ideal op-amp $i_+ = i_- = 0 \text{ mA}$

As $i_+ = 0 \text{ mA}$, so $V_+ = 0V$ [no voltage drops across 5 kΩ due to 0 current]

So, $V_- = V_+ = 0V$ [virtual short circuit]


2 kΩ is shorted (both node voltage = 0V)

So, this is basically an inverting op-amp

$$V_o = -\frac{R_2}{R_1} V_i = -\frac{3 \text{ k}\Omega}{1 \text{ k}\Omega} * 2V = -6V$$

2 kΩ and 5 kΩ are just dummy resistors here. They have no effect on the output of the circuit.

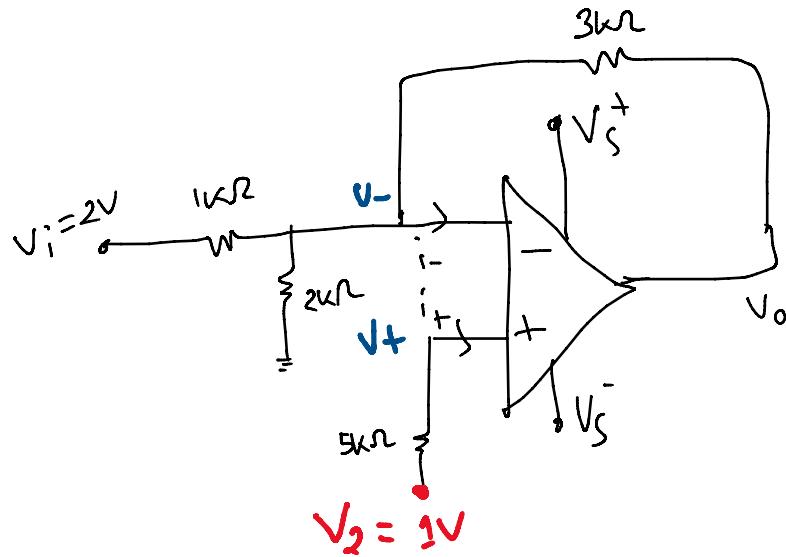Q7. Find V_o from the given op-amp circuit.



Sol:

In this case, $5\text{k}\Omega$ is not connected to ground anymore.

In ideal op-amp $i_+ = i_- = 0 \text{ mA}$

As $i_+ = 0 \text{ mA}$, so $V_+ = V_2 = 1\text{V}$ [no voltage drops across $5\text{k}\Omega$ due to 0 current]

So, $V_- = V_+ = 1\text{V}$ [virtual short circuit]

Here, $2\text{k}\Omega$ is not shorted like Q6

Nodal equation (node V_-):

$$\begin{aligned} \frac{V_-}{2\text{k}\Omega} + \frac{V_- - Vi}{1\text{k}\Omega} + \frac{V_- - V_o}{3\text{k}\Omega} &= 0 \\ \Rightarrow \frac{1\text{V}}{2\text{k}\Omega} + \frac{1\text{V} - 2\text{V}}{1\text{k}\Omega} + \frac{1\text{V} - V_o}{3\text{k}\Omega} &= 0 \\ \therefore V_o &= -\frac{1}{2}\text{V} = -0.5\text{V} \end{aligned}$$


Q8: Design separate circuits, using only diodes, to implement the following functions,

a) $z = \min(v_I, 7)$ and $v_O = \max(z, 2)$

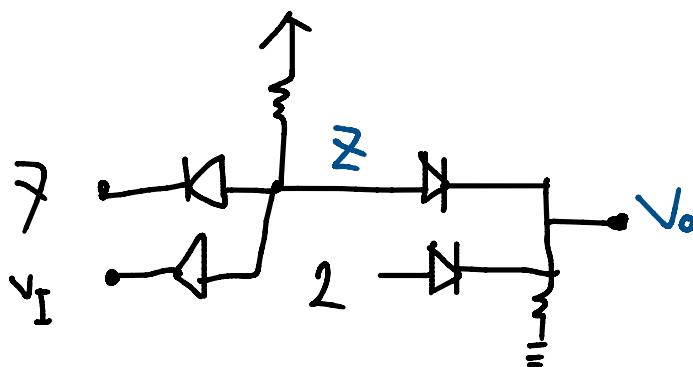b) Draw the VTC curve. [Hint: v_O vs v_I]

Sol: a) $z = 7v_I$ [as minimum operation means AND gate]

$v_O = 2+z$ [as maximum operation means OR gate]




b) $v_o = 2 + z = 2 + 7v_I$


If $v_I \leq 2V$, $v_o = 2 + 7v_I = \max(2V, \min(7, v_I)) = \max(2V, v_I) = 2V$ (constant)

If $2V < v_I < 7V$, $v_o = \max(2V, \min(7, v_I)) = \max(2V, v_I) = v_I$ (straight line)

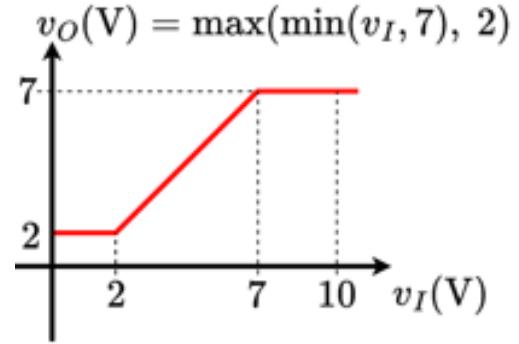If $v_I \geq 7V$, $v_o = \max(2V, \min(7, v_I)) = \max(2V, 7V) = 7V$ (constant)



Q9. Find v_o if $v_I = 0.5$ V.

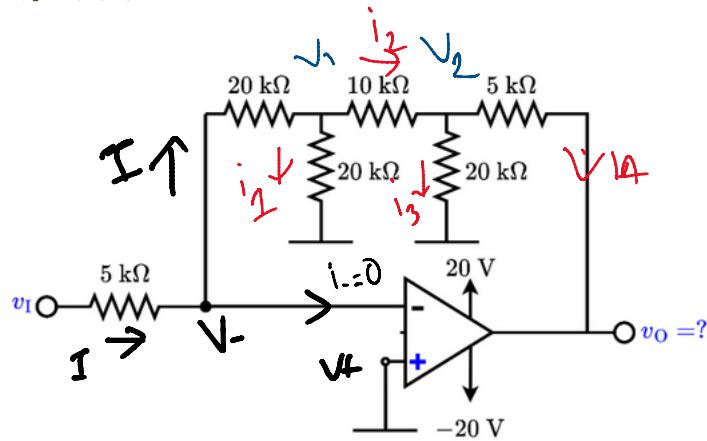

$V_+ = 0V$, So, $V_- = V_+ = 0V$ [virtual short circuit]

$$\text{Current, } I = \frac{v_I - V_-}{5 \text{ k}\Omega} = \frac{0.5 \text{ V}}{5 \text{ k}\Omega} = 0.1 \text{ mA}$$

$$\text{Current, } I = \frac{(V_-) - V_1}{20 \text{ k}\Omega} = \frac{-V_1}{20 \text{ k}\Omega} = 0.1 \text{ mA} \Rightarrow V_1 = -2 \text{ V}$$


$$i1 = \frac{V_1}{20 \text{ k}\Omega} = \frac{-2 \text{ V}}{20 \text{ k}\Omega} = -0.1 \text{ mA}$$

$$i2 = I - i1 = 0.2 \text{ mA} = \frac{V_1 - V_2}{10 \text{ k}\Omega} = \frac{-2 \text{ V} - V_2}{20 \text{ k}\Omega} \Rightarrow V_2 = -4 \text{ V}$$

$$i3 = \frac{V_2}{20 \text{ k}\Omega} = \frac{-4 \text{ V}}{20 \text{ k}\Omega} = -0.2 \text{ mA}$$

$$i4 = i2 - i3 = 0.4 \text{ mA} = \frac{V_2 - v_o}{5 \text{ k}\Omega} = \frac{-4 \text{ V} - v_o}{5 \text{ k}\Omega} \Rightarrow v_o = -6 \text{ V}$$

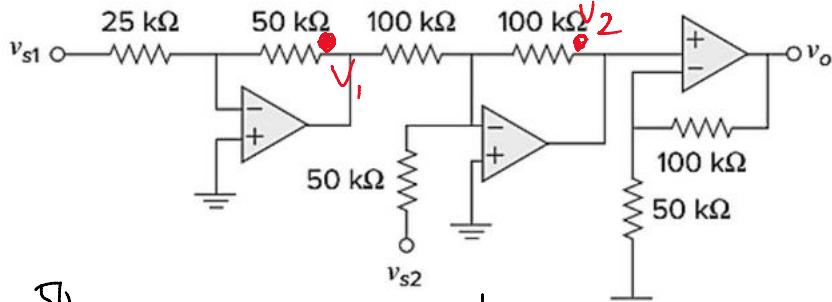Q10. Determine v_o , when $v_{s1} = 1V$ and $v_{s2} = 2V$ are given as inputs.




$$v_1 = -\frac{50}{25} \times v_{s1} = -2V \quad (\text{inverting op-amp})$$

$$\begin{aligned} v_2 &= -\left(\frac{100}{100} v_1 + \frac{100}{50} v_{s2}\right) \\ &= -(-2V + 4V) = -2V \end{aligned} \quad (\text{inverting adder})$$

$$v_o = \left(1 + \frac{100}{50}\right)v_2 \quad (\text{non-inverting op-amp})$$

$$\boxed{v_o = -6V}$$

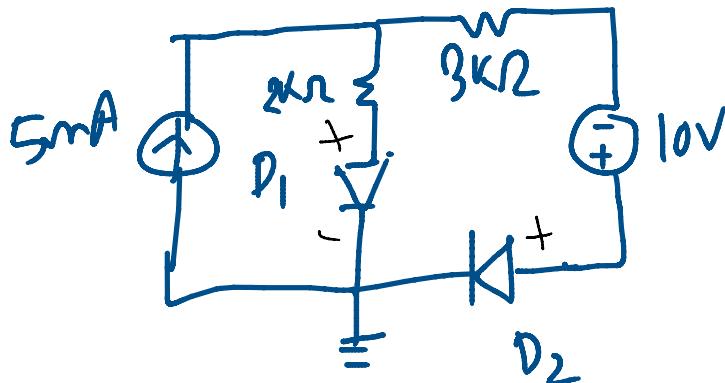Q11. Find diode states for the circuit shown below. Assume ideal diodes.



Assuming D1 off (open ckt), D2 on (short ckt)

$I_1 = 5 \text{ mA} (>0)$ assumption ok for D2


KVL: $10 \text{ V} - 3k \times 5 \text{ mA} + V_1 = 0$


$$\Rightarrow V_1 = 15 \text{ V} - 10 \text{ V} = 5 \text{ V}$$

$$V_a = V_1 = 15 \text{ V} \quad (\text{as open ckt}) \quad V_c = 0 \text{ V}$$

Voltage difference across D1, $V_D = V_a - V_c = 15 \text{ V} (> 0 \text{ V})$ assumption wrong for D2

So, assumption wrong!

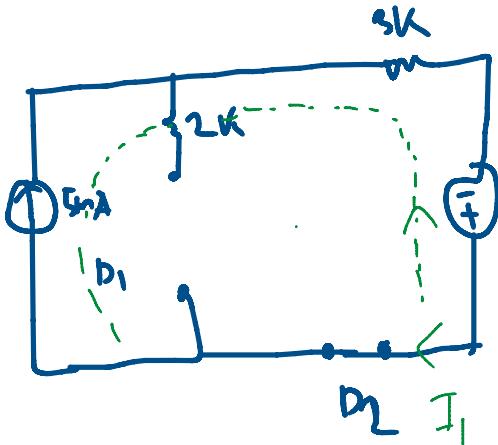

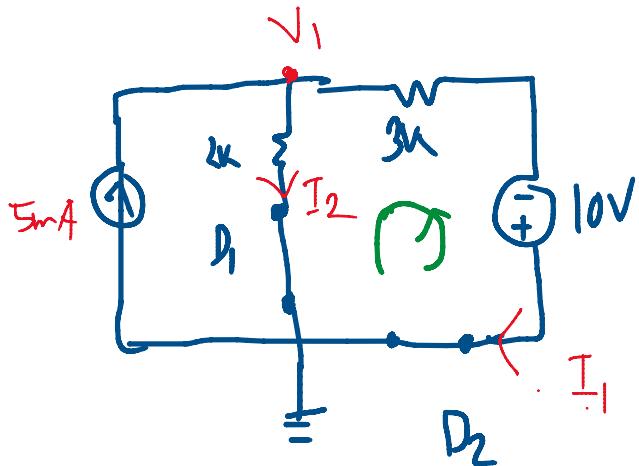

Now, Assuming D1, D2 both on (short ckt)


$$\text{KVL: } 10 \text{ V} - 3k * I_1 + 2k * I_2 = 0 \quad \text{---(1)}$$

$$\text{KCL: } I_1 + I_2 = 5 \text{ mA} \quad \text{---(2)}$$

Solving (1) & (2), $I_1 = 4 \text{ mA}$ and $I_2 = 1 \text{ mA}$

As both diode current is positive that means both D1 & D2 are ON.
Assumption Correct!

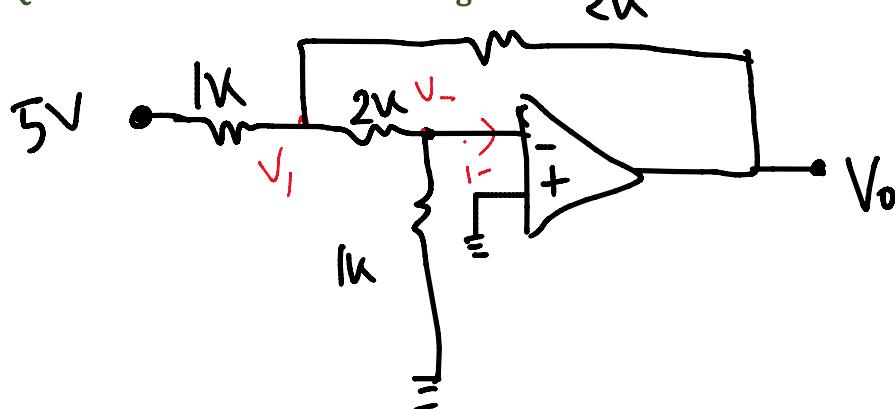Q12. Find out V_o for the following circuit.



Soln: $V_+ = 0 = V_-$ [virtual short]

nodal analysis: $\frac{(V_+) - V_1}{2\text{k}} + \frac{V_-}{1\text{k}} = 0$

$$\Rightarrow \frac{0 - V_1}{2\text{k}} + \frac{0}{1\text{k}} = 0 \quad \boxed{\therefore V_1 = 0 \text{ V}}$$



nodal analysis: $\frac{V_1 - 0 \text{ V}}{2\text{k}} + \frac{V_1 - 5 \text{ V}}{1\text{k}} + \frac{V_1 - V_o}{2\text{k}} = 0$

$$\Rightarrow \frac{0 - 0}{2\text{k}} + \frac{0 - 5 \text{ V}}{1\text{k}} + \frac{0 - V_o}{2\text{k}} = 0$$

$$\Rightarrow \boxed{V_o = -\frac{2\text{k}}{1\text{k}} \times 5 \text{ V} = -10 \text{ V}}$$



same as inverting op-amp

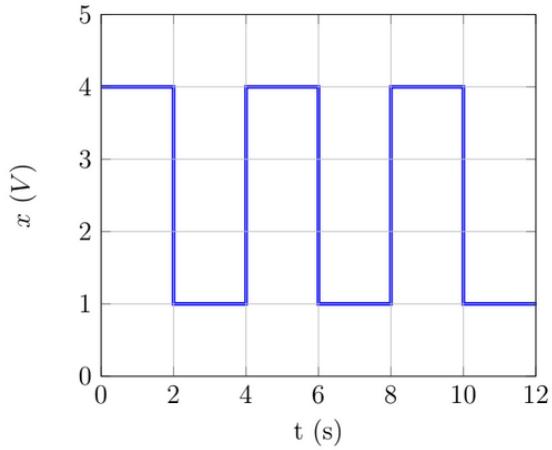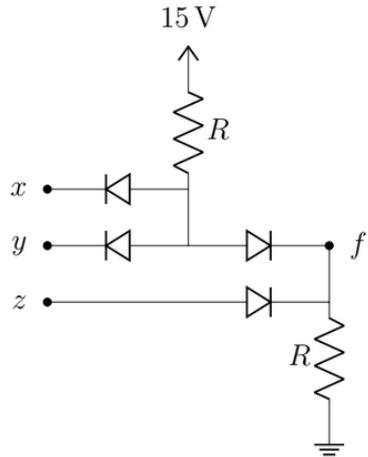Q13: Draw the waveform (voltage vs time graph) of f , where $y = 2 \text{ V}$, $z = 3 \text{ V}$, and x has a waveform as shown in the figure on the right.



Soln:

$$f = x + y + z = \max(\min(x, y), z)$$

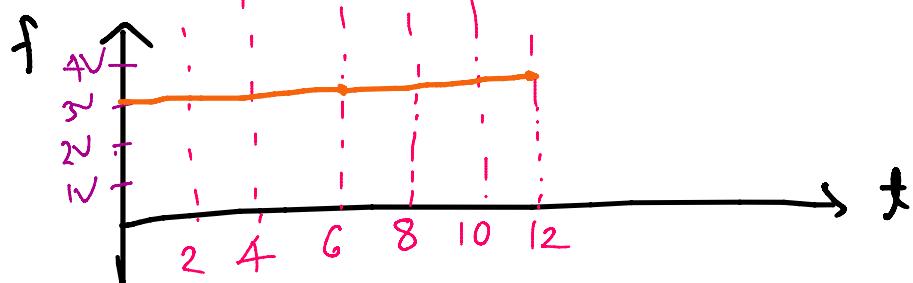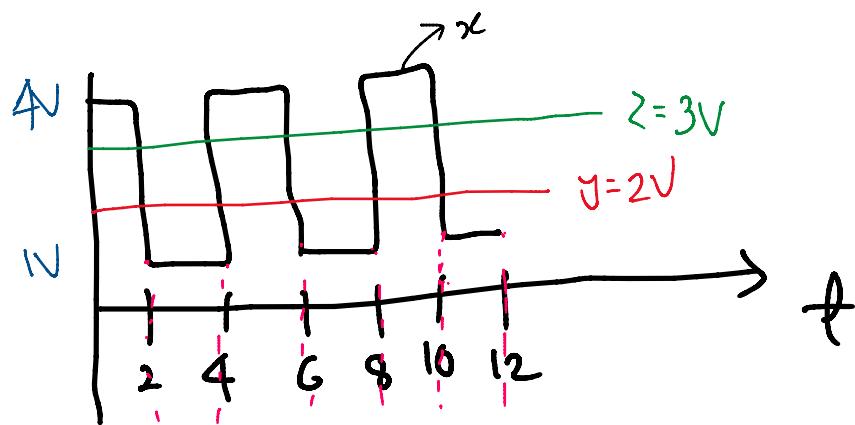

$0 \leq t \leq 2\text{s}:$

$$\begin{aligned} f &= \max(\min(4\text{V}, 2\text{V}), 3\text{V}) \\ &= \max(2\text{V}, 3\text{V}) \\ &= 3\text{V} \end{aligned}$$


$2\text{s} \leq t \leq 4\text{s}:$

$$\begin{aligned} f &= \max(\min(1\text{V}, 2\text{V}), 3\text{V}) \\ &= \max(1\text{V}, 3\text{V}) = 3\text{V} \end{aligned}$$


$4\text{s} \leq t \leq 6\text{s}:$

$$\begin{aligned} f &= \max(\min(4\text{V}, 2\text{V}), 3\text{V}) \\ &= \max(2\text{V}, 3\text{V}) \\ &= 3\text{V} \end{aligned}$$

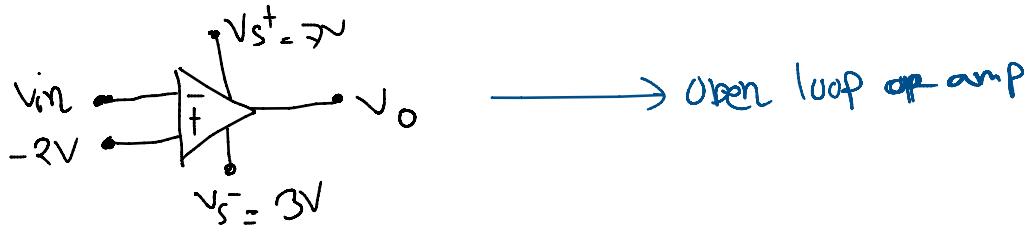Q14: Draw the VTC of the following circuit-




Soln:

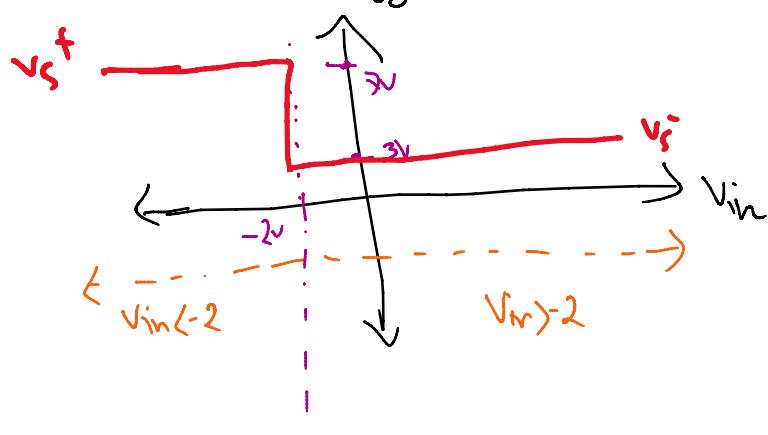


$$\begin{aligned}
 v_d &= (v_+) - (v_-) \\
 &= -2 - v_{in} \\
 v_d > 0 \rightarrow v_o &= v_s^+ \\
 \Rightarrow -2 - v_{in} > 0 &\Rightarrow v_{in} < -2 \Rightarrow v_o = v_s^+ = 3V \\
 \text{So, } v_{in} > -2 \rightarrow v_o &= v_s^- = 3V
 \end{aligned}$$

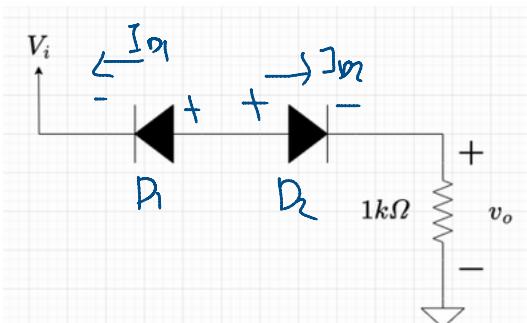Q15: Find V_o and the states of the diodes if $V_i = 10\text{ V}$ [consider ideal diodes].



but in that case, $I_{D2} = 0$ [open circuit]
 \therefore wrong assumption!
 \therefore Both diodes are off.

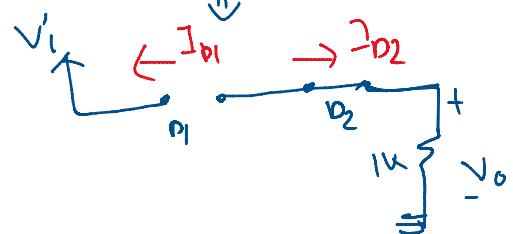If we assume, D_1 off, D_2 on
 \downarrow
open \downarrow short



$$V_o = 0\text{ V}$$

If two diodes are connected back-to-back (both cathodes are short (a) or both anodes are short (b)), then both of the diodes must be off.

