

CSE251: Electronic Devices and Circuits

Lecture 10 – Zener Diodes

Prepared By:


Shadman Shahid (HAD)

Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University

Email: ext.shadman.shahid@bracu.ac.bd

Voltage Regulators

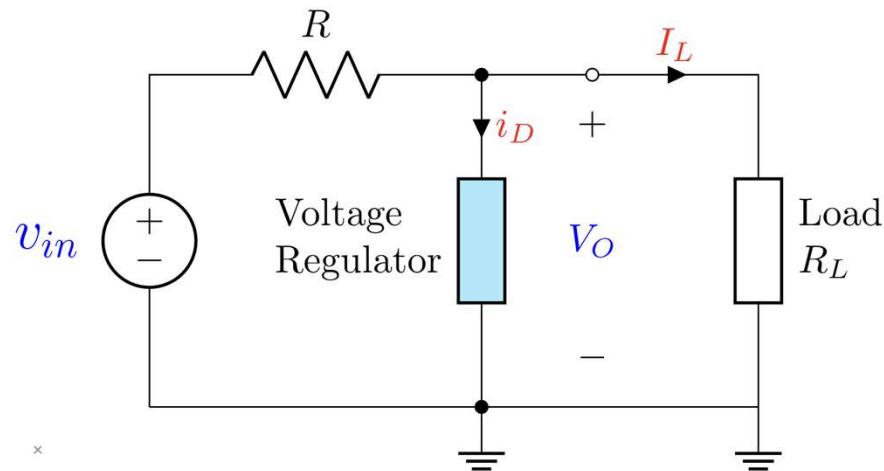- **Voltage Regulation** is the measure of how well a system can provide near constant voltage.
- **Voltage Regulators** provide steady voltage independent of how much power is drawn from the power source




Voltage Regulator:

Tries to maintain a voltage constant at V_O

Voltage Regulators

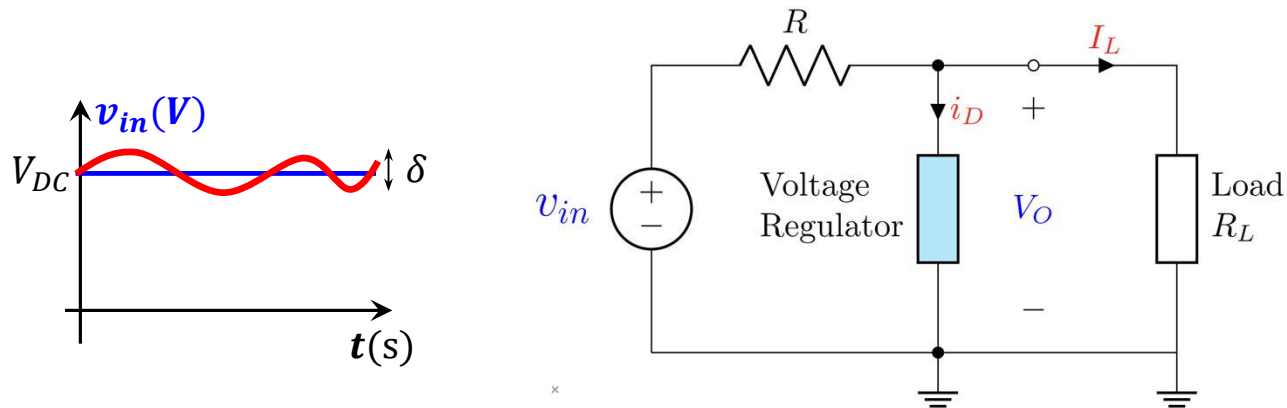Let's assume that v_{in} is not a perfect DC source. It supplies a voltage of $(V_{DC} \pm \delta)$ V



Voltage Regulator:

Tries to maintain a voltage constant at V_O even when v_{in} is varying.


Variables: V_O should remain constant irrespective of the changes in the following quantities:

1. **Input Voltage:** v_{in}
2. **Load Current:** I_L
3. **VR current:** i_D

Voltage Regulator – Worst Case Scenario

Worst Case Scenario occurs when the three variables (v_{in} , I_L , and i_D) change in such a way, such that maintaining V_O constant requires the most power (current) from the **Voltage Regulator**.

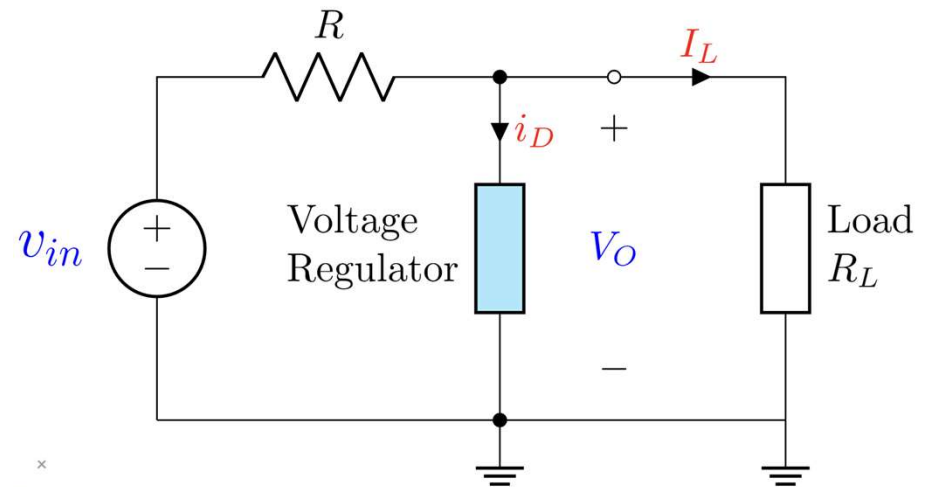The **Voltage regulator** is at its maximum capacity at the worst case.




Worst Case Scenario occurs when



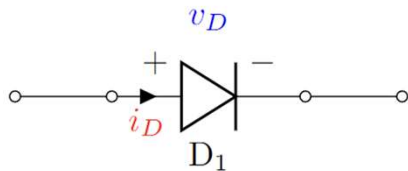
1. **Input Voltage is minimum:** $v_{in}(\min)$
2. **Load Current is maximum:** $I_L(\max)$
3. **VR current minimum:** $i_D(\min)$

Diodes as Voltage Regulators


Diodes have (IV) characteristics that makes them ideal for voltage regulation.



Exponential IV characteristics of diodes

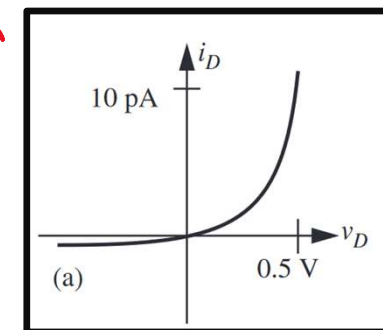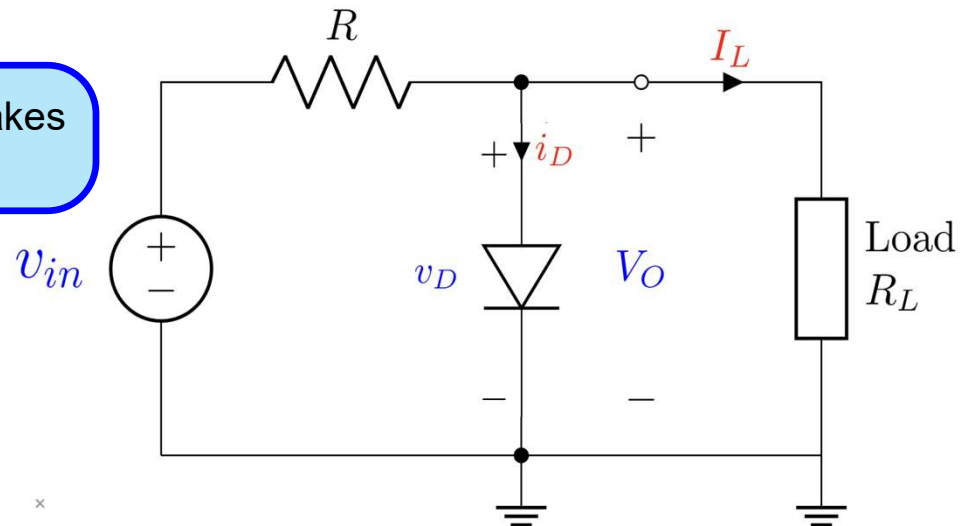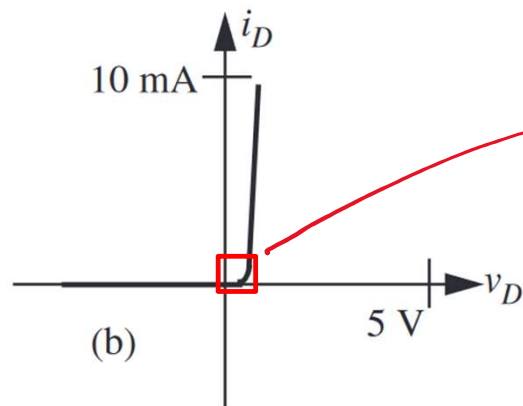

Diodes Revisited

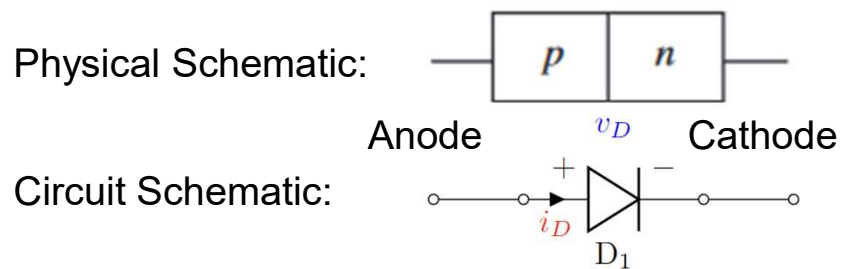



Forward Bias

Net positive Voltage across $p - n$ junction

Reverse Bias

Net negative Voltage across $p - n$ junction

Exponential IV characteristics of diodes

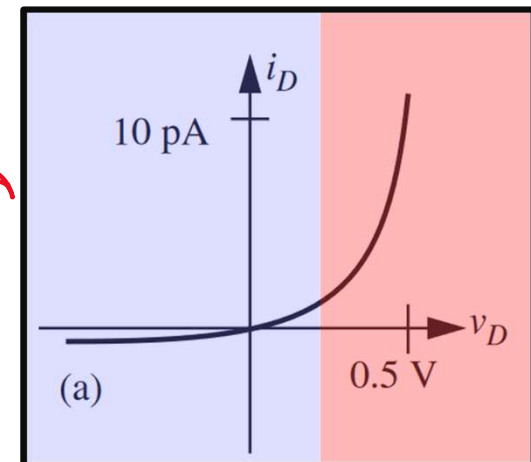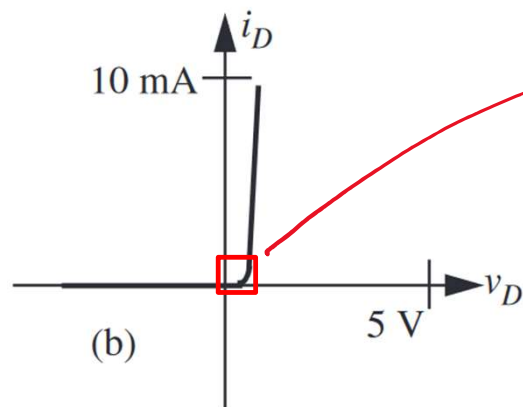

Diodes Revisited

1. Ideal Diode Model:
2. Constant Voltage Drop (CVD) Model:
3. Voltage Source in Series with Resistor Model (CVD+R) Model
4. Exponential Model:

Simple


Increasing Accuracy

Complex

v_D : Total Voltage Across diode
 v_d : AC component of the Voltage
 V_d : DC component of Voltage


 V_{Do} : Diode Cut-off voltage

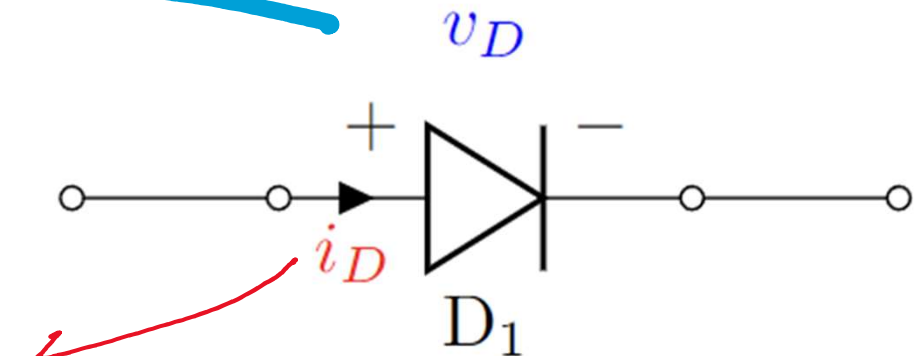i_D : Total current through diode (Anode to Cathode)




Diode Models

1. Ideal Diode Model:

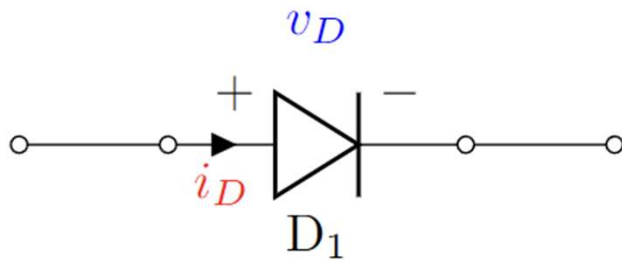


Not suitable as
**VOLTAGE
REGULATOR**

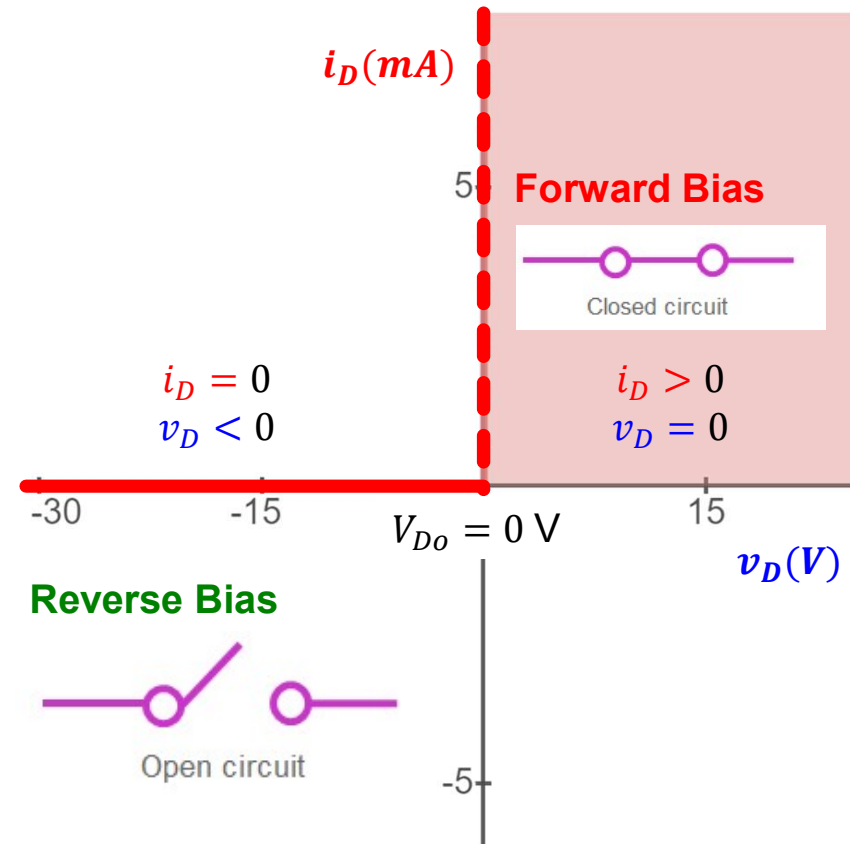


Diode Models

2. Constant Voltage Drop (CVD) Model:

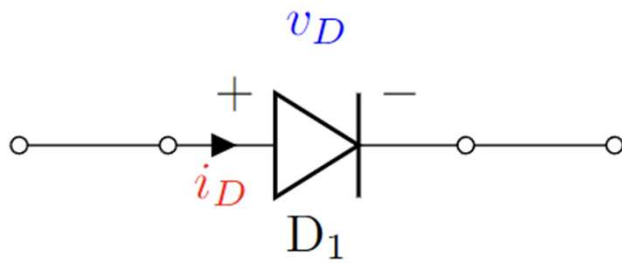

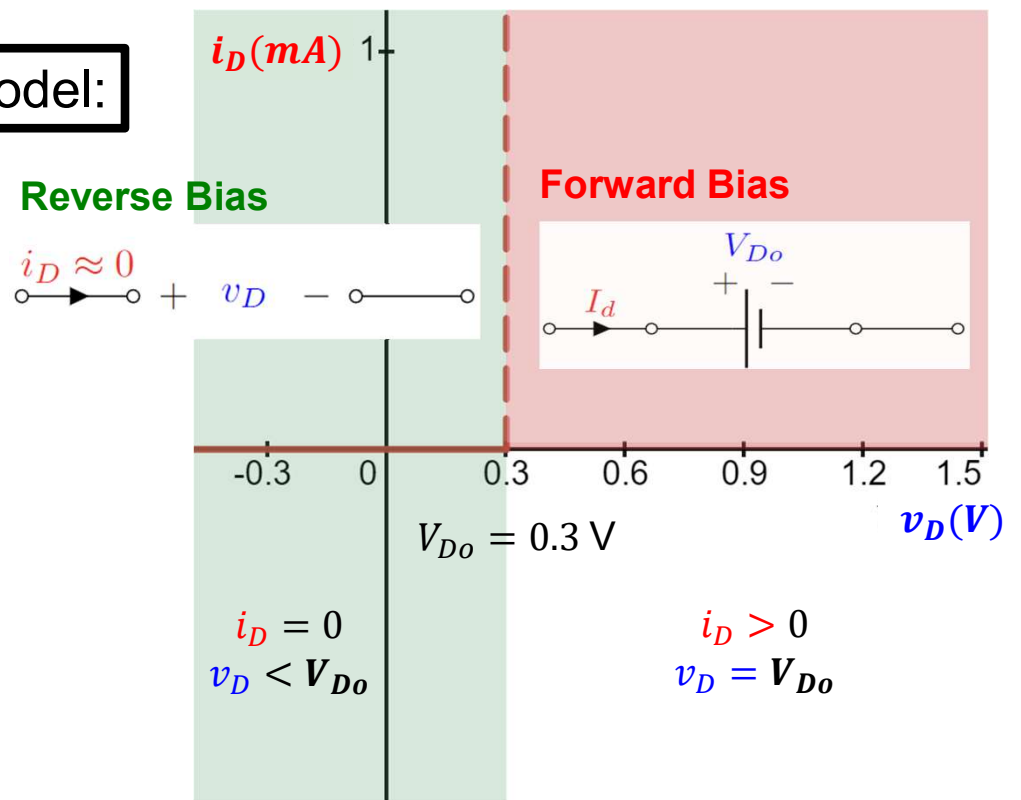Suitable as
**VOLTAGE
REGULATOR ?**
Maybe!



Diode Models


2. Constant Voltage Drop (CVD) Model:

Reverse Bias




$$\begin{aligned} i_D &= 0 & y &= 0 \\ v_D &< V_{Do} & x &< V_{Do} \end{aligned}$$

Forward Bias

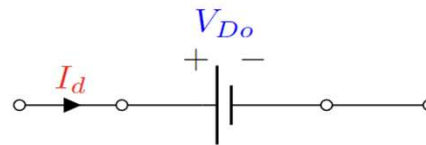
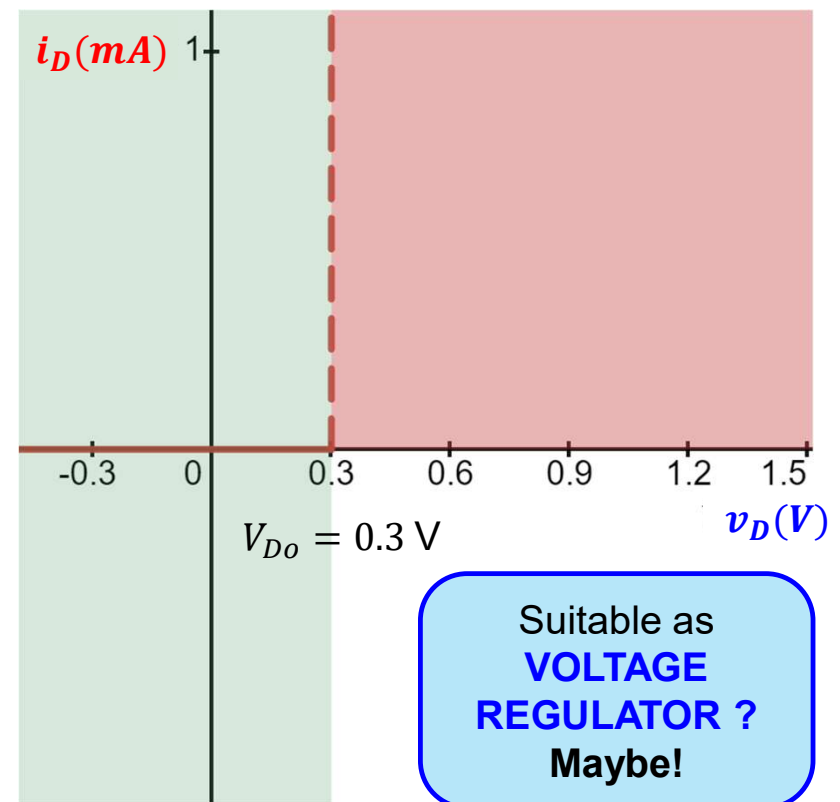
$$\begin{aligned} i_D &> 0 & y &> 0 \\ v_D &= V_{Do} & x &= V_{Do} \end{aligned}$$



Practice Problem 1

The circuit of the adjacent **Figure** is specified to have the following parameters. The supply voltage V_{in} is nominally 3 V but can vary by ± 0.1 V. R_L can draw a maximum of 10 mA and $i_D(\min) = 1$ mA.


What is R for worst case scenario if v_D (V_O) is to be regulated at 0.6 V? [Since r_o is not provided, you can consider the CVD model.]

Solution:

Worst Case Scenario occurs when

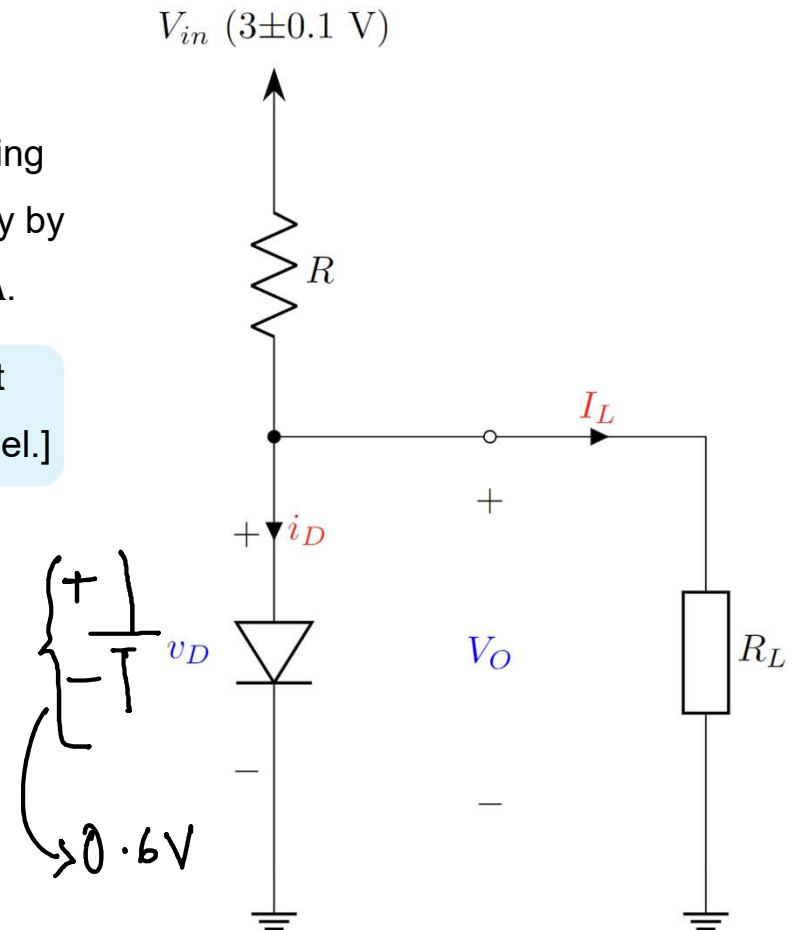1. $v_{in}(\min) = 3 - 0.1 \text{ V} = 2.9 \text{ V}$
2. $I_L(\max) = 10 \text{ mA}$
3. $i_D(\min) = 1 \text{ mA}$

$$\frac{v_{in}(\min) - 0.6}{R} = I_L(\max) + i_D(\min)$$



Practice Problem 1


The circuit of the adjacent **Figure** is specified to have the following parameters. The supply voltage V_{in} is nominally 3 V but can vary by ± 0.1 V. R_L can draw a maximum of 10 mA and $i_D(\min) = 1$ mA.

What is R for worst case scenario if v_D (V_O) is to be regulated at 0.6 V? [Since r_o is not provided, you can consider the CVD model.]

Solution:
$$\frac{V_{in}(\min) - 0.6}{R} = I_L(\max) + i_D(\min)$$


$$R = \frac{2.9 - 0.6}{10 + 1} \text{ k}\Omega = 0.209 \text{ k}\Omega$$

$$\therefore R = 209 \Omega$$

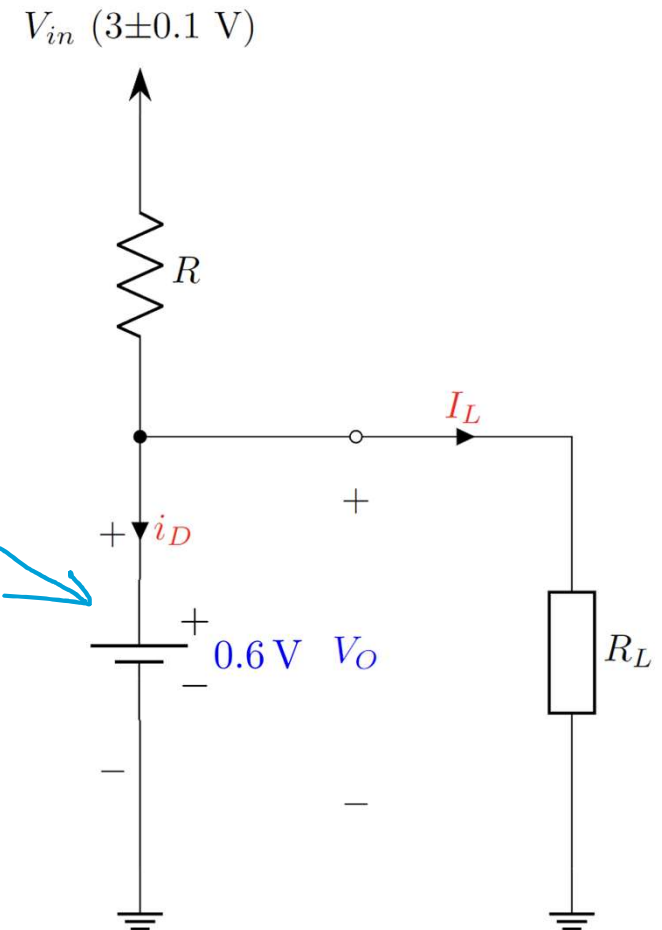

Drawbacks of Diodes as Voltage Regulators

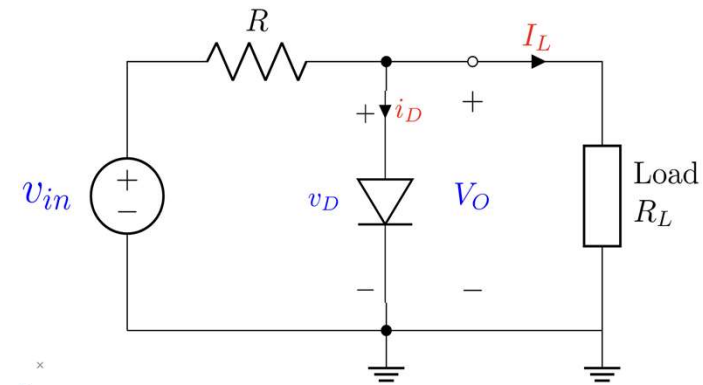
- Regulation voltage is low: $\sim V_{D0}$ (0.3 ~ 1 V)
- High i_D (min)
- R can be low \rightarrow High power loss



Possible Solution:


Stacked Diodes in Series: -- Regulation Voltage can be increased to $n \cdot V_{D0}$ for n stacked diodes.

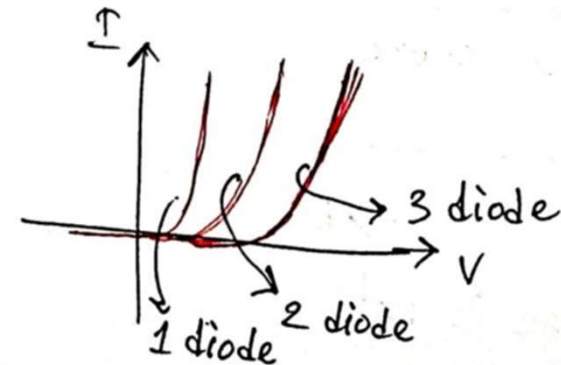However, this can make the diodes deviate more from ideal model. **IV characteristics** become flatter (more lossy).



Drawbacks of Diodes as Voltage Regulators

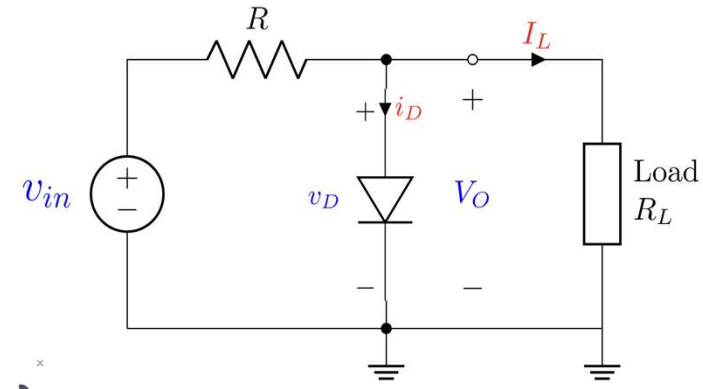- Regulation voltage is low: $\sim V_{D0}$ (0.3 ~ 1 V)
- High i_D (min)
- R can be low \rightarrow High power loss



Better Solution:


Use **Breakdown Region** of diodes as constant voltage source because:

1. **Breakdown Voltage** can be controlled during fabrication
2. i_D (min) for reverse breakdown is very low!

Diode Models

4. Exponential model:


The full IV characteristic

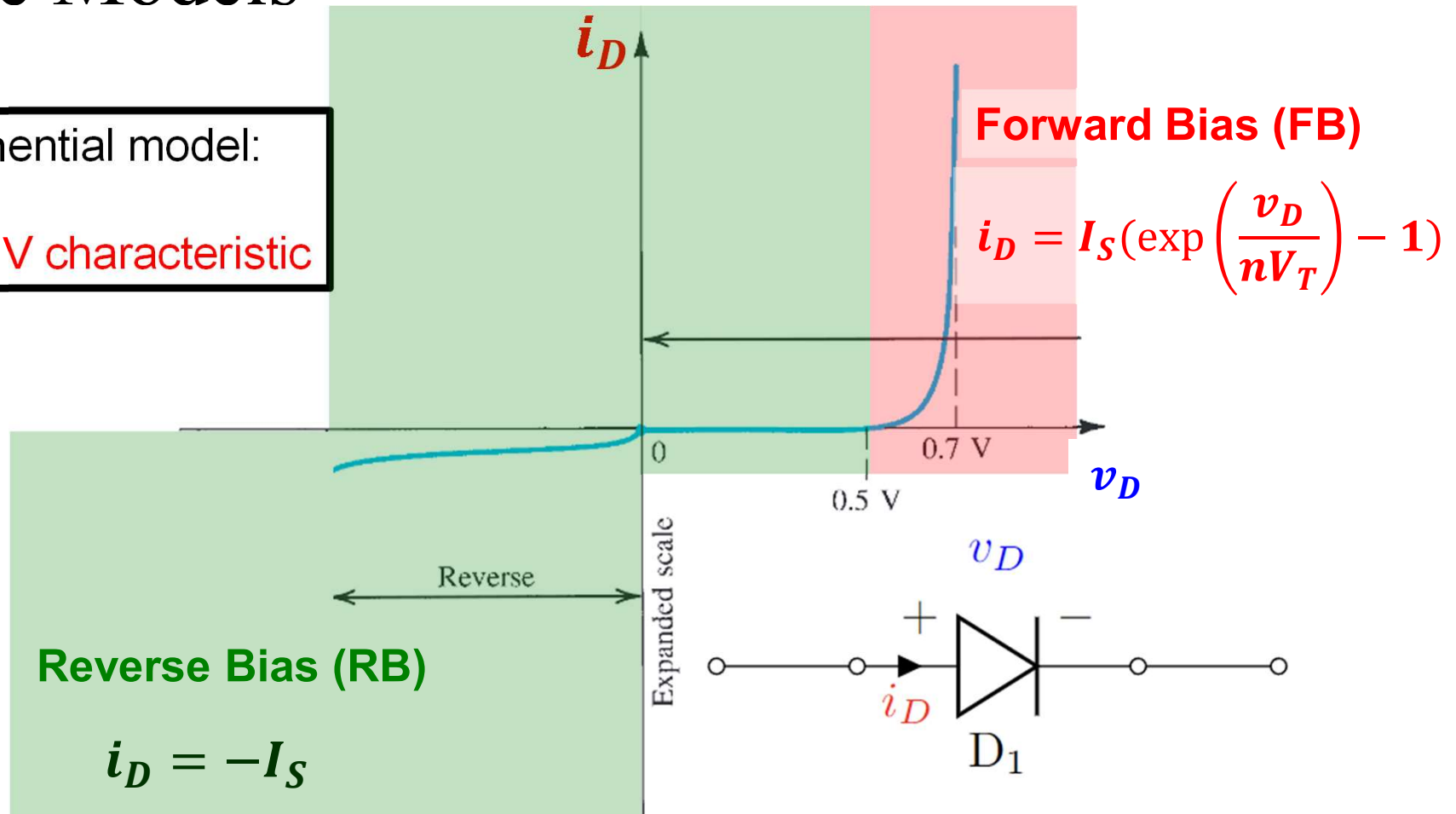

Diode Models

4. Exponential model:

The full IV characteristic

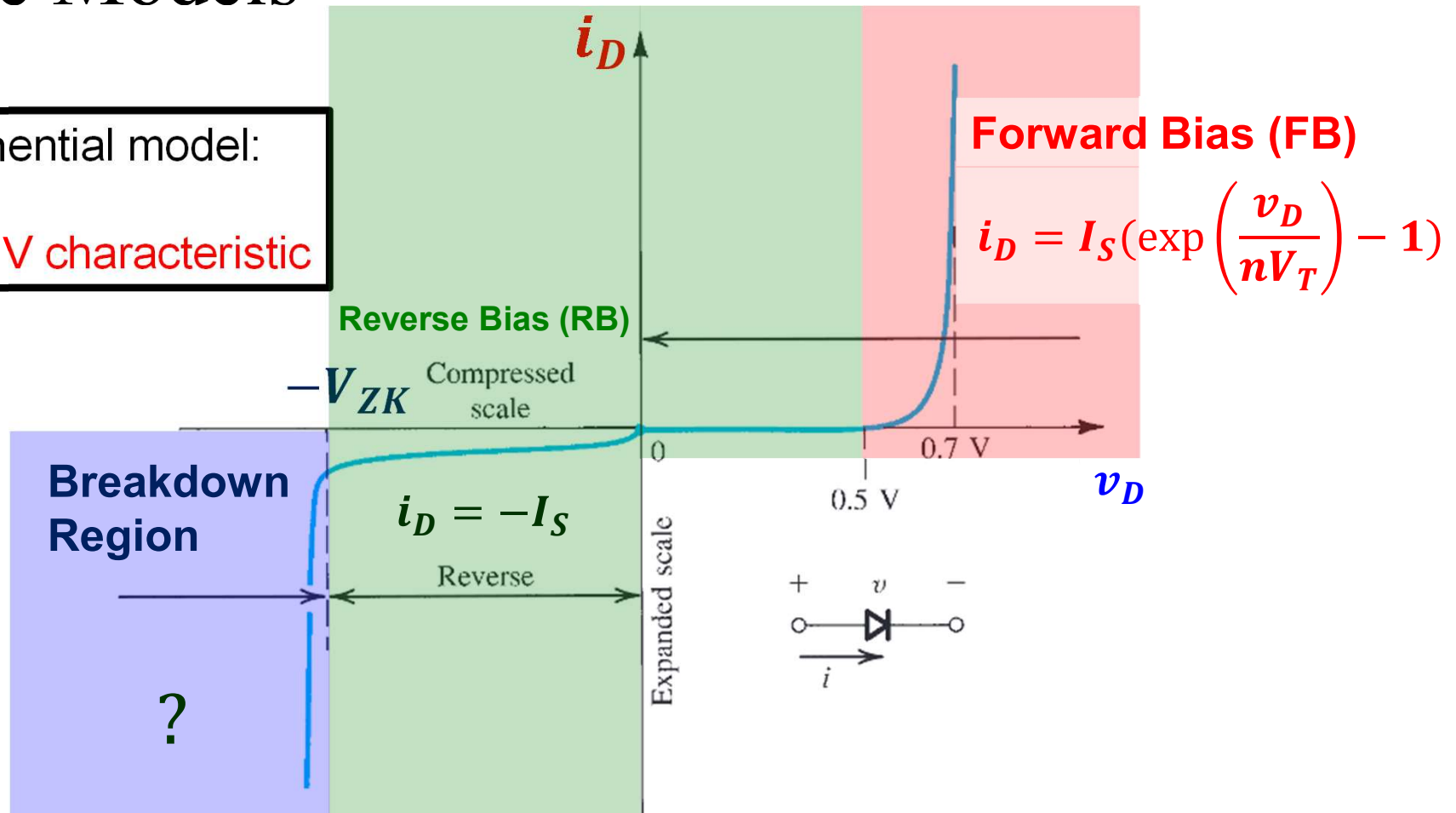


Diode IV Characteristic

Reverse Bias (RB)

$i_D = -I_S$ I_S in this case is the reverse leakage current.

$y = -I_S$ For $v_D < V_{D0}$ there is negligible current flow through the diode.

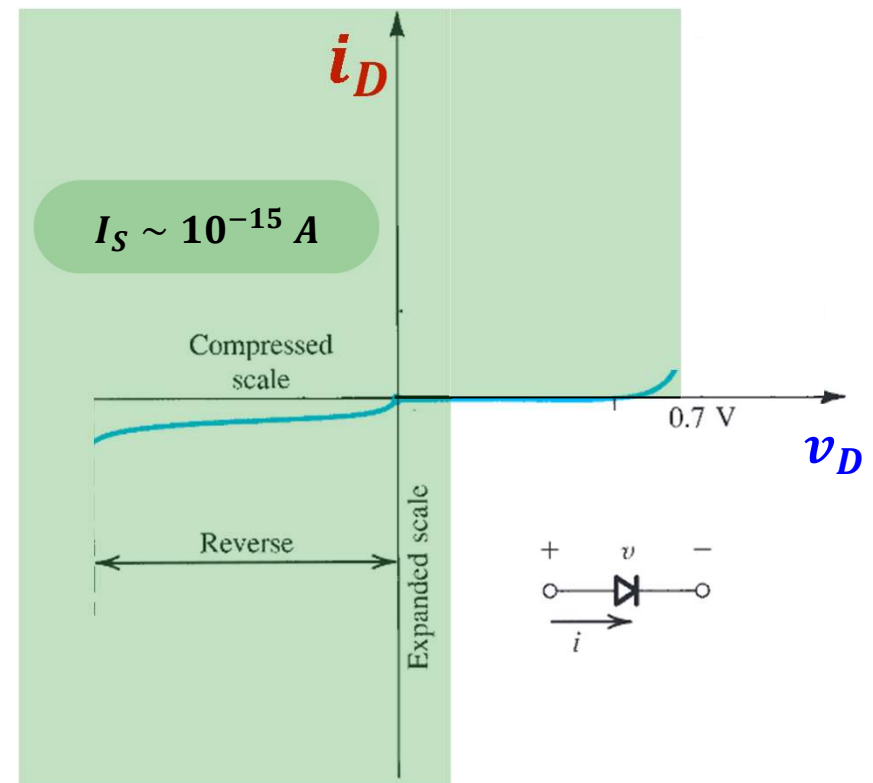Normal diodes cannot tolerate large voltages in reverse bias. **Applying large voltages in reverse bias may damage the diode.**



Diode IV Characteristic


Breakdown Region

Normal diodes cannot tolerate large voltages in reverse bias. **Applying large voltages in reverse bias may damage the diode.**

Special classes of diodes exist, that are primed to operate in large reverse bias voltages. These diodes are called

Zener diodes

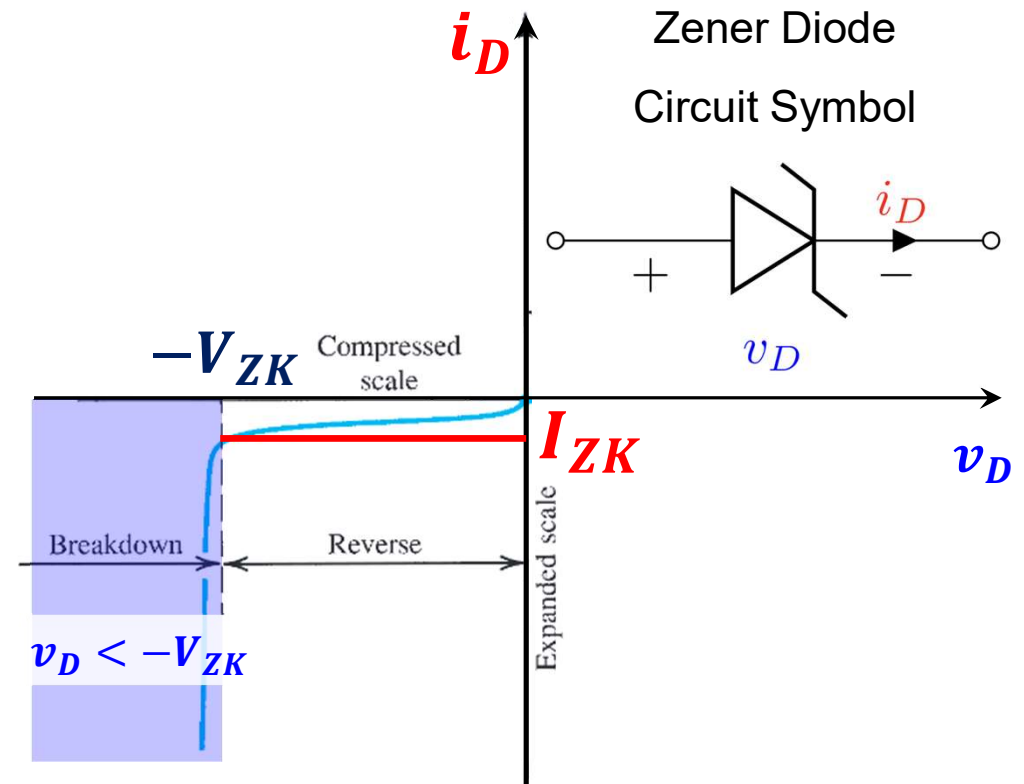In this **Breakdown region**, the diode acts almost like a “**constant voltage source**”.





Zener Diode IV

Breakdown Region

Zener knee voltage ($-V_{ZK}$): The RB voltage beyond which diode breaks down. The corresponding current is knee current (I_{ZK})

For $v_D < -V_{ZK}$,

$$\text{Slope} = \frac{1}{r_z}$$

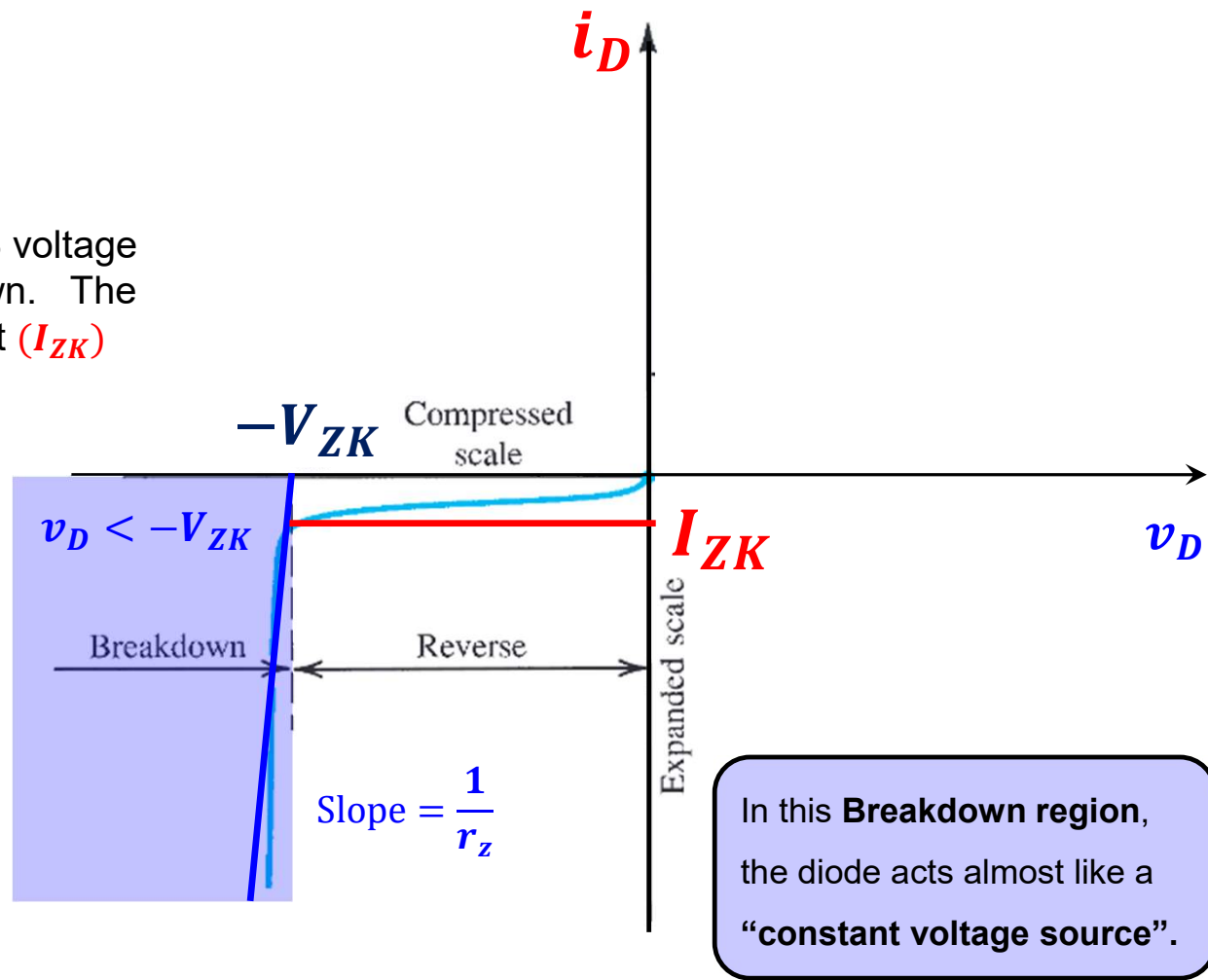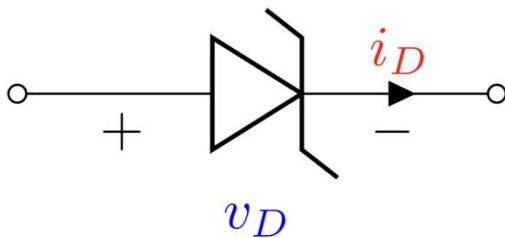


Zener Diode IV

Breakdown Region


Since this region is like the forward bias region of a normal diode, we invert the signs of voltage and currents across a Zener diode operating at breakdown voltage, to solve Zener diode circuits in a similar way.

For a voltage of $-V_Z$, the diode allows a breakdown current of $-I_Z$.

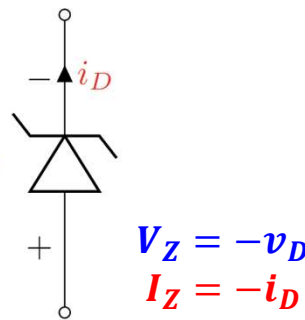The slope at this point of the graph is $\frac{1}{r_z}$




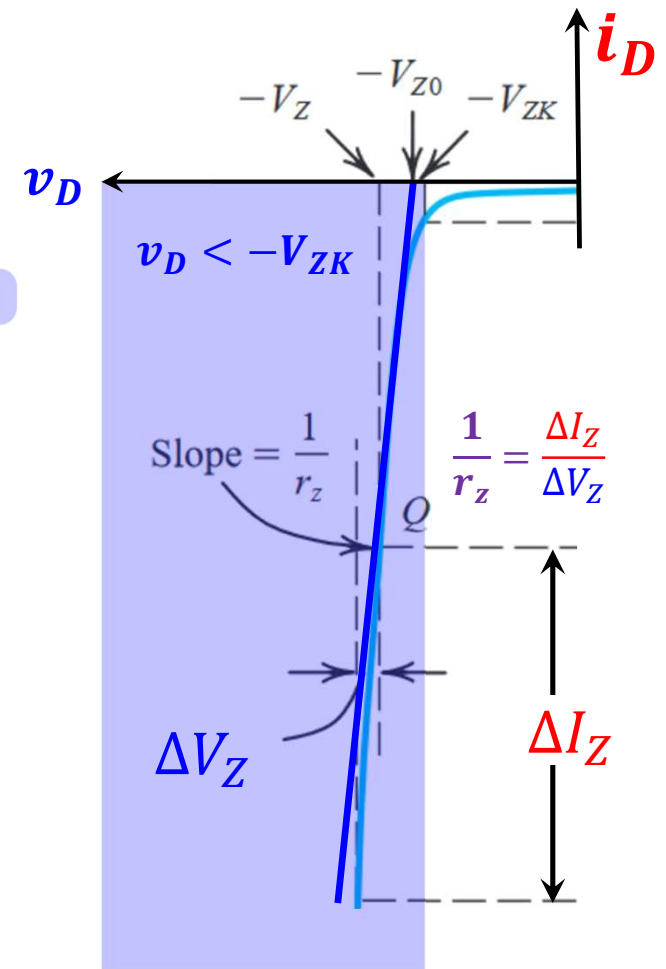
If we extrapolate a straight line from $(-V_Z, -I_Z)$ point, and extend it towards the x -axis, ($i_D = 0$ A), the intersecting point is V_{Z0} . ($V_{ZK} \approx V_{Z0}$)



Zener Diode IV

Breakdown Region ($V_Z > V_{Z0} \approx V_{ZK}$)


$$V_Z = V_{Z0} + I_Z r_z$$

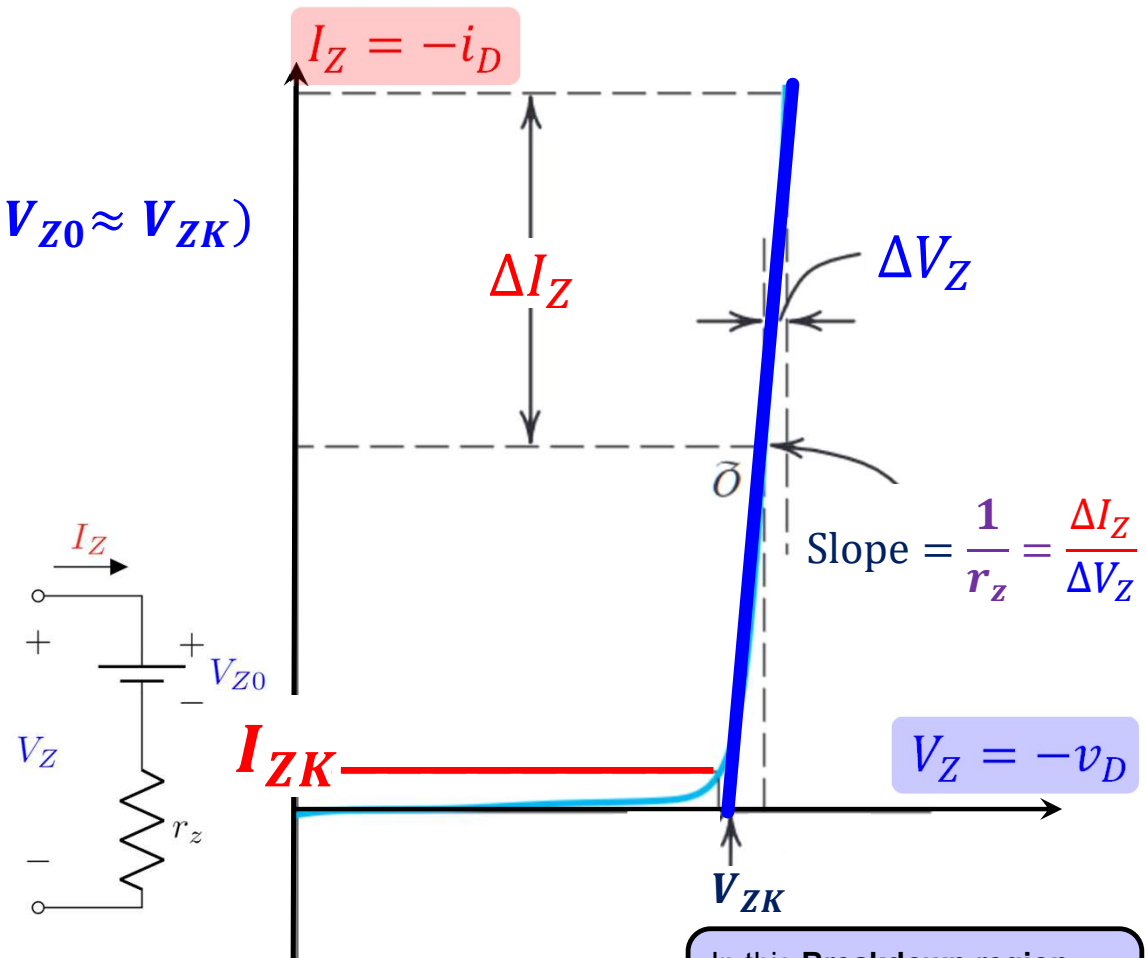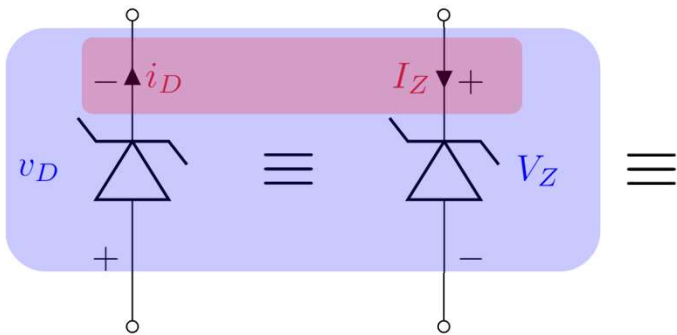

In this **Breakdown region**, the diode acts almost like a “constant voltage source”.


Zener Diode Breakdown IV Characteristic

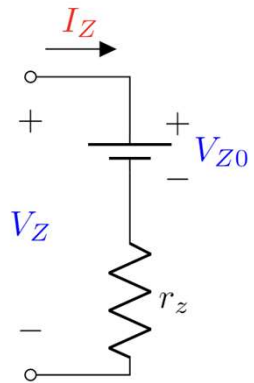Breakdown Region ($V_Z > V_{Z0} \approx V_{ZK}$)



$$V_Z = V_{Z0} + I_Z r_z$$

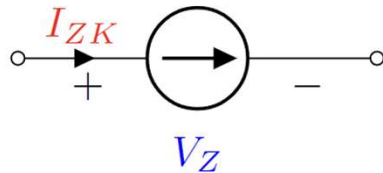
Reverse Bias Region ($V_Z < V_{Z0} \approx V_{ZK}$)



$$I_Z = I_{ZK}$$

V_Z : Total RB Voltage Across **Zener** diode

V_{Z0} : Zener knee voltage

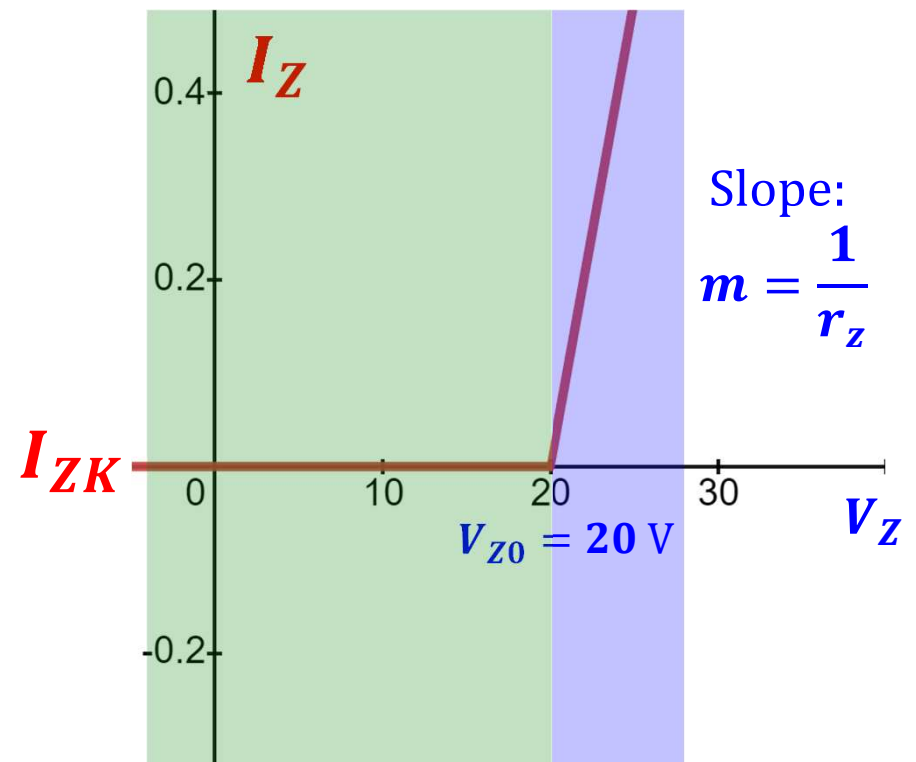

Practice Problem 2

The 6.8 – V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by ± 1 V.


$$V^+ = 10 \pm 1 \text{ V}$$

$$V_Z = 6.8 \text{ V at } I_Z = 5 \text{ mA}$$

$$r_z = 20 \Omega.$$

$$I_{ZK} = 0.2 \text{ mA}.$$


- Find V_O with no load and with V^+ at its nominal value
- (For $R_L = 0.5 \text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I
- Find the R_L that would give rise to worst-case scenario at worst case V^+ . In this worst-case scenario, calculate the Zener voltage V_Z , load current I_L and input current I
- (For $R_L = 2 \text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I
- Design the circuit, i.e., find the minimum value of the input voltage V^+ such that, voltage regulation is maintained even in the worst-case scenario for $R_L = 2 \text{ k}\Omega$. (Forget that V^+ is 10 V)
- Determine whether the circuit will maintain regulation if V^+ is increased. If yes, argue if it should be increased or not.

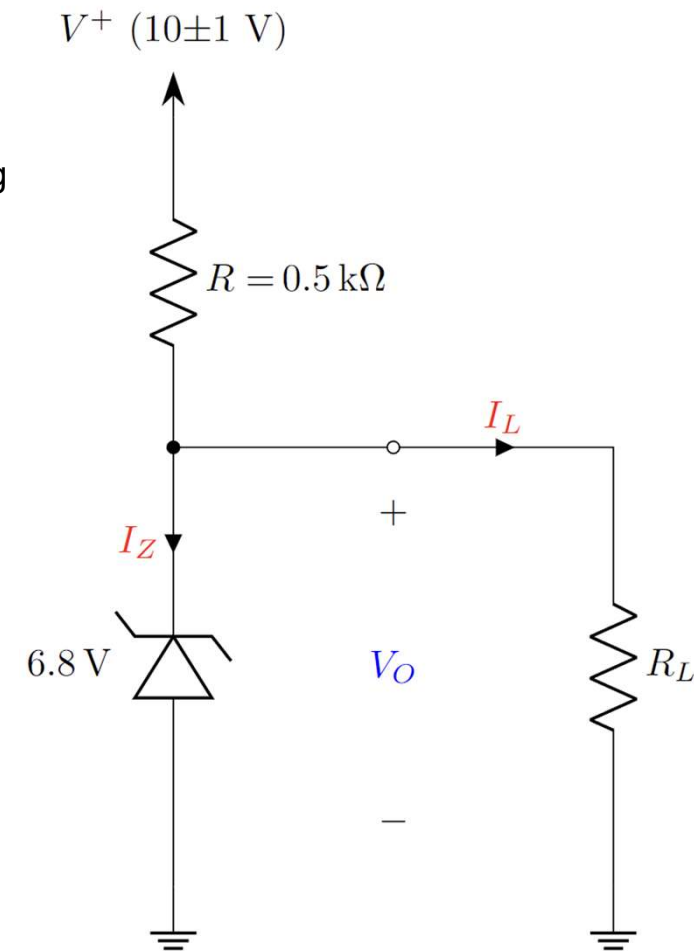

Practice Problem 2

The 6.8 V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1\text{ V}$.

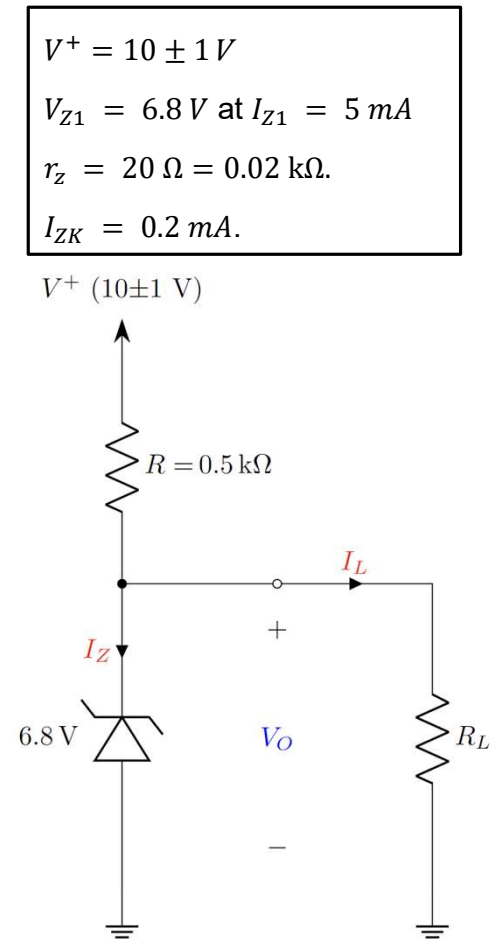(a) Find V_O with no load and with V^+ at its nominal value



Practice Problem 2

The 6.8 – V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by ± 1 V.

(a) Find V_0 with no load and with V^+ at its nominal value

Solution:


Extracting Zener diode 's reverse cut-in voltage

$$V_{ZO} = 6.8 - 5 \times 0.02 \text{ V}$$

$$\therefore V_{ZO} = 6.7 \text{ V}$$

Determining current from the 10 V source
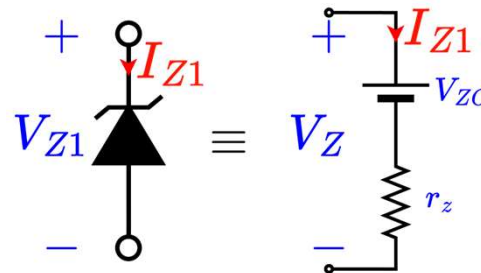
$$I = \frac{10 - 6.7}{0.5 + 0.02} \text{ mA} = 6.346 \text{ mA}$$



Determining output voltage

$$V_0 = 6.7 + 6.346 \times 0.02 \text{ V}$$


$$V_0 = 6.82692 \text{ V}$$

$$V^+ = 10 \pm 1 \text{ V}$$

$$V_{Z1} = 6.8 \text{ V at } I_{Z1} = 5 \text{ mA}$$

$$r_z = 20 \Omega = 0.02 \text{ k}\Omega.$$

$$I_{ZK} = 0.2 \text{ mA}.$$

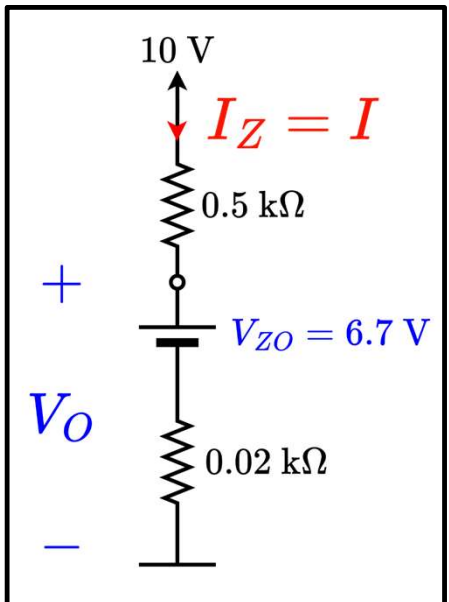


Practice Problem 2

The 6.8 V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1\text{ V}$.

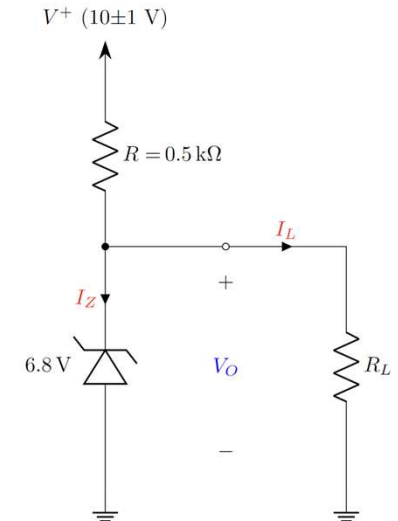(b) (For $R_L = 0.5\text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I

Solution:

$$\begin{aligned} V^+ &= 10 \pm 1\text{ V} \\ V_Z &= 6.8\text{ V at } I_Z = 5\text{ mA} \\ V_{ZO} &= 6.7\text{ V} \\ r_z &= 20\ \Omega. \\ I_{ZK} &= 0.2\text{ mA}. \end{aligned}$$



Practice Problem 2

The 6.8 – V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by ± 1 V.

(b) (For $R_L = 0.5 \text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I

Solution:


Solving the node equation at V_O .

$$\begin{aligned} \frac{(10 \pm 1) - V_O}{R} &= \frac{V_O - V_{ZO}}{r_z} + \frac{V_O}{R_L} \\ \frac{(10 \pm 1) - V_O}{0.5} &= \frac{V_O - 6.7}{0.02} + \frac{V_O}{0.5} \\ \therefore V_O &= 6.537 \sim 6.611 \text{ V} \end{aligned}$$

As, $V_O < V_{ZO}$, the Zener diode will not be in reverse breakdown mode, but in cut off

$$I_Z = I_{ZK}$$

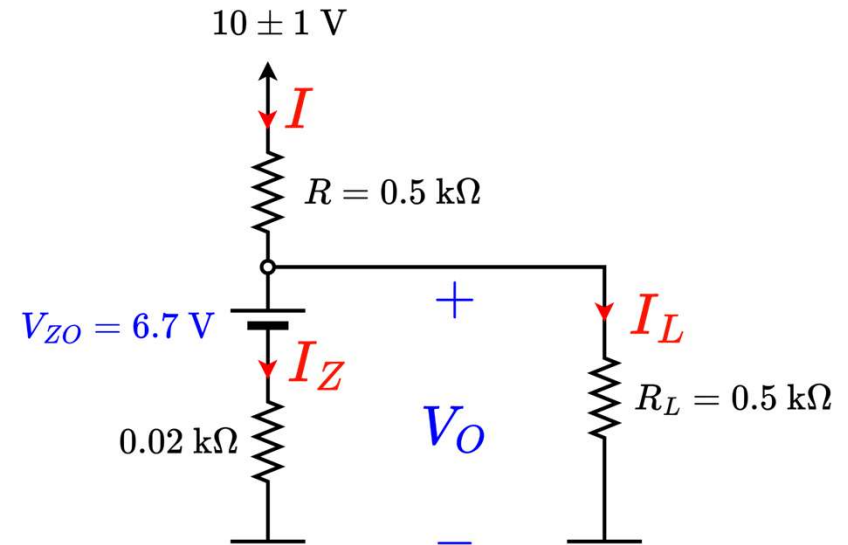$V^+ = 10 \pm 1 \text{ V}$ $V_Z = 6.8 \text{ V at } I_Z = 5 \text{ mA}$ $V_{ZO} = 6.7 \text{ V}$ $r_z = 20 \Omega$ $I_{ZK} = 0.2 \text{ mA}$
--



Practice Problem 2

The $6.8 - V$ Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally $10 V$ but can vary by $\pm 1 V$.

(b) (For $R_L = 0.5 k\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I

Solution:

$$\therefore V_O = 6.537 \sim 6.611 V$$

As, $V_O < V_{ZO}$, the Zener diode will not be in reverse breakdown mode, but in cut off

$$I_Z = I_{ZK}$$

So,

$$V_O \left(\frac{1}{0.5} + \frac{1}{0.5} \right) = \frac{10 \pm 1}{0.5} - 0.2$$

$$V_O = 4.95 \pm 0.5 V$$

$$I_L = \frac{V_O}{R_L} = \frac{4.95 \pm 0.5}{0.5} \text{ mA} = 9.9 \pm 1 \text{ mA}$$


$$V^+ = 10 \pm 1 V$$

$$V_Z = 6.8 V \text{ at } I_Z = 5 mA$$

$$V_{ZO} = 6.7 V$$

$$r_z = 20 \Omega.$$

$$I_{ZK} = 0.2 mA.$$

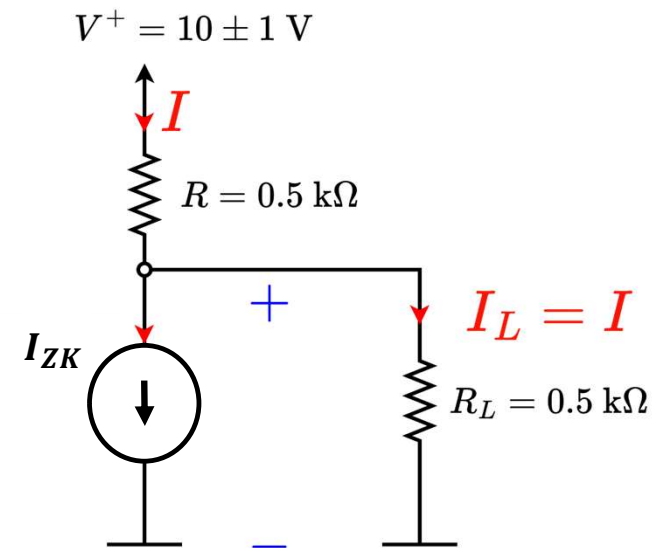

(c) Find the R_L that would give rise to worst-case scenario at worst case V^+ . In this worst-case scenario, calculate the Zener voltage V_Z , load current I_L and input current I

(d) (For $R_L = 2 \text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I

(c) The determining factor for worst-case scenario:

$$I_Z \geq I_{Zk}$$

$$\therefore \text{At } I_Z = I_{Zk} \text{ mA}$$



$$V_o = V_{Z0} + I_{Zk} r_z = 6.704 \text{ V}$$

$$\therefore I = I_L + I_Z$$

(Since $I_Z = I_{Zk}$)

$$\therefore I_L = I - I_{Zk}$$

$$\therefore I_L \leq I - I_{Zk}$$

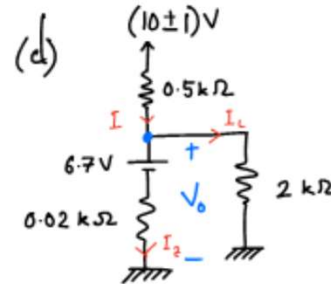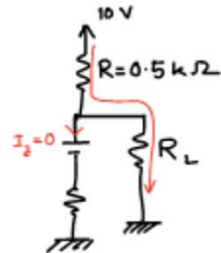

$$I = I_Z + I_L$$

$$\frac{V^+ - V_o}{R} = \frac{V_o - V_{Z0}}{r_z} + \frac{V_o}{R_L}$$

$$\Rightarrow V_o \left(\frac{1}{R} + \frac{1}{r_z} + \frac{1}{R_L} \right) - V_{Z0} \left(\frac{1}{r_z} \right) = \frac{V^+}{R}$$

$$\Rightarrow V_o \left(\frac{1}{0.5} + \frac{1}{2} + \frac{1}{0.02} \right) - 6.7 \left(\frac{1}{0.02} \right) = \frac{10}{0.5}$$

$$\Rightarrow V_o = \frac{355}{54} \text{ V} = 6.76 \text{ V}$$

$$I_Z = \frac{V_o - V_{Z0}}{r_z} = \frac{6.76 - 6.7}{0.02} = 3.1 \text{ mA} > I_{Zk}$$

So, the zener diode can sustain this load.

$$\therefore \begin{aligned} V_o &= 6.76 \text{ V} \\ I_Z &= 3.1 \text{ mA} \\ I_L &= \frac{6.76}{2} \text{ mA} = 3.38 \text{ mA} \end{aligned}$$

$$\frac{V_o}{R_L} \leq \frac{V^+ - V_o}{R} - I_{Zk}$$

$$R_L \geq \frac{6.704}{\frac{10 - 6.704}{0.5} - 0.2} \text{ k}\Omega$$

$$R_L \geq 1.526 \text{ k}\Omega$$

$$R_L \geq 1.526 \text{ k}\Omega$$


$$V_o = 6.704 \text{ V}$$

$$I_L \leq \frac{V_o}{R_L} = 4.392 \text{ mA}$$

$$I \geq I_L + I_{Zk}$$

$$I \geq 4.592 \text{ mA}$$

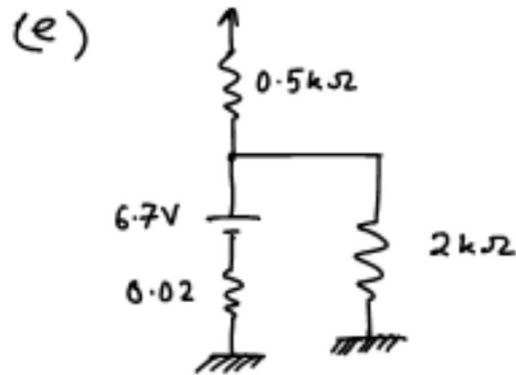(e) Design the circuit, i.e., find the minimum value of the input voltage V^+ such that, voltage regulation is maintained even in the worst-case scenario for $R_L = 2 \text{ k}\Omega$. (Forget that V^+ is 10 V)



At worst case: $I_Z = I_{ZK}$

$$\therefore V_o = V_{Z0} + I_{ZK} r_z$$

$$= 6.7 + 0.2 \times 0.02 = 6.704 \text{ V}$$

For $R_L = 2 \text{ k}\Omega$

$$I_L = \frac{6.704}{2} = 3.352 \text{ mA}$$



$$I = I_L + I_{ZK}$$

$$I = 3.552 \text{ mA}$$


$$\therefore V^+ \geq V_o + IR$$

$$V^+ \geq 8.48 \text{ V}$$

Solving Problems

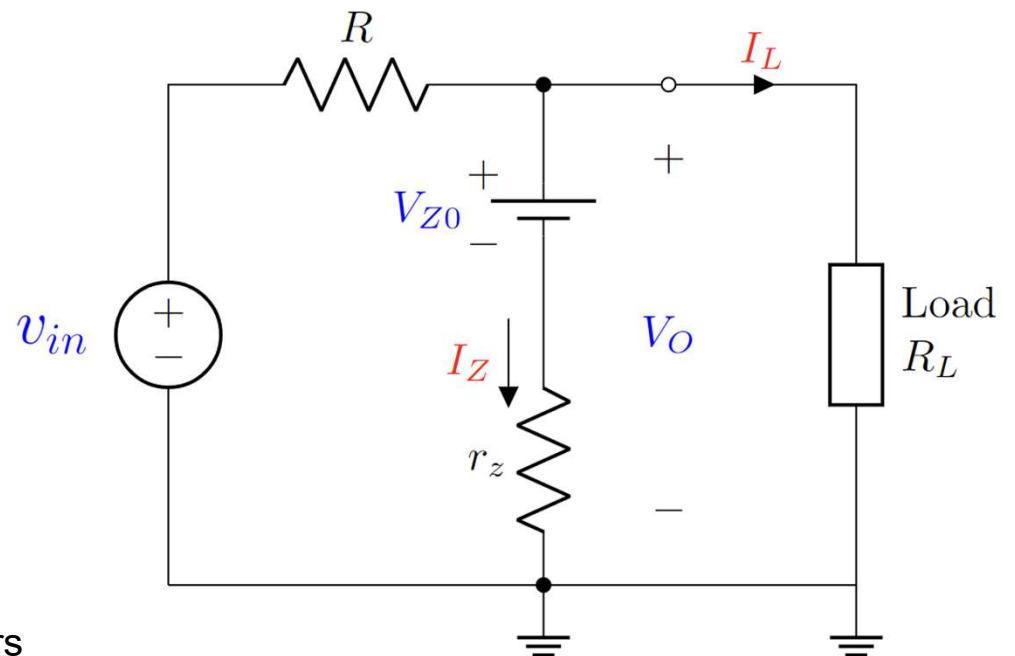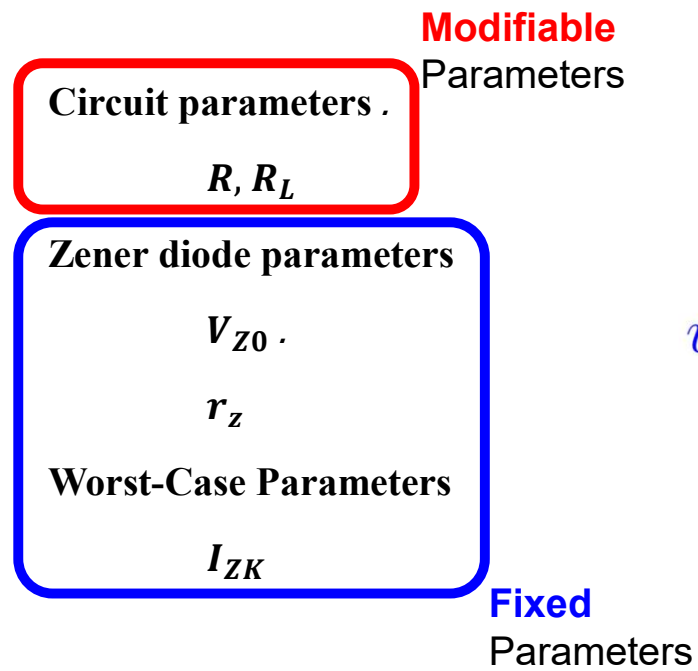

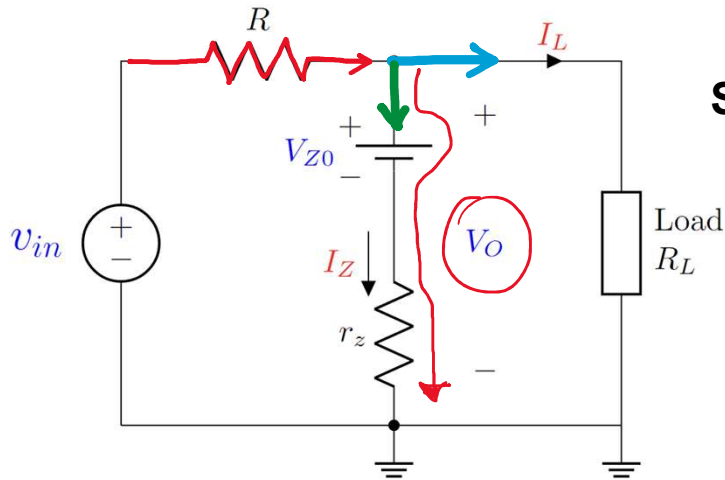Measures of Worst-Case Scenario (General)



Solving:

$$V_O = V_{Z0} + I_Z r_z$$

$$I_Z = \frac{V_O - V_{Z0}}{r_z}$$

Minimum Current through VR:

$$I_Z(\min) \geq I_{ZK}$$

$$\frac{V_O - V_{Z0}}{r_z} \geq I_{ZK}$$

$$V_O \geq V_{Z0} + I_{ZK} r_z$$

Minimum Input Voltage:

$$v_{in}(\min) > V_{Z0} + I_{ZK}(r_z + R) + I_L R$$

Worst Case Scenario occurs when

1. **Input Voltage is minimum:** $v_{in}(\min)$
2. **Load Current is maximum:** $I_L(\max)$
3. **VR current minimum:** $I_Z(\min)$

Maximum Load Current

$$I_L(\max) \leq \frac{v_{in} - V_O}{R} - I_{ZK}$$

Some important tips

- If V_{ZK} , V_{Z0} and r_z are given, we can calculate $I_{ZK} = \frac{V_{ZK} - V_{Z0}}{r_z}$
- If V_{Z0} and r_z are **not** provided, consider $V_{ZK} = V_Z = V_{Z0}$
- Consider $I_{ZK} = 0$ if not provided

