

# CSE251: Electronic Devices and Circuits

Lecture: 18 - 20 – BJT

**Prepared By:**




**Shadman Shahid (HAD)**

Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University

Email: [ext.shadman.shahid@bracu.ac.bd](mailto:ext.shadman.shahid@bracu.ac.bd)

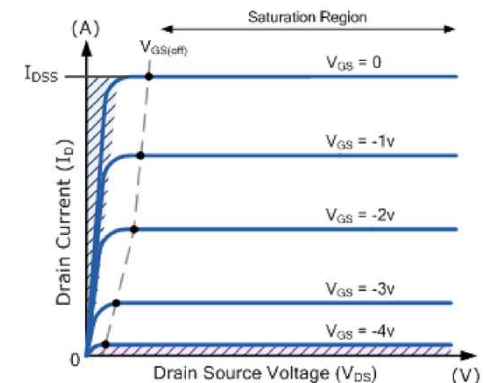
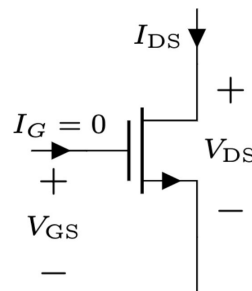
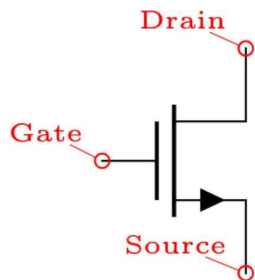
# Transistors as Digital Switch

- Transistors are 3 terminal non-linear devices, can be used as switch
- 2 types – **Voltage Controlled**, **Current Controlled**
- **M**etal **O**xide **S**emiconductor **F**ield **E**ffect **T**ransistor (**MOSFET**) are **voltage controlled**
- Control,  $C = V_{GS}$ . The IV characteristics ( $I_{DS}$  vs  $V_{DS}$ ) depends on  $V_{GS}$
- Actual dependency is complex.
- Will start with a simple (but approximate) one – **S-Model** (Switch Model)



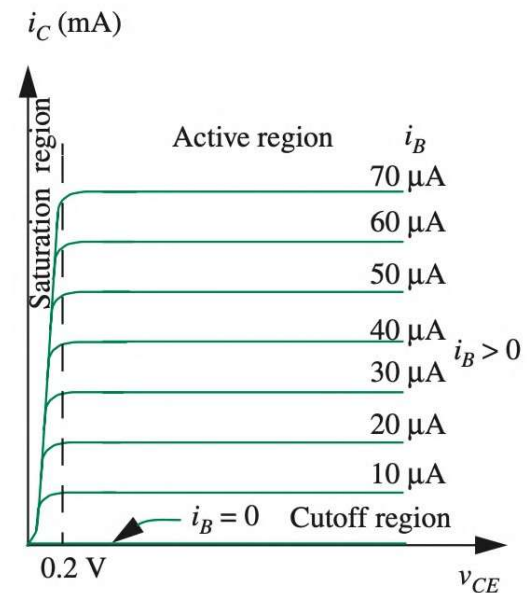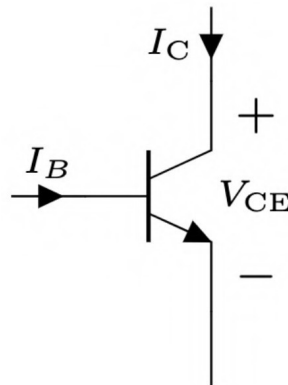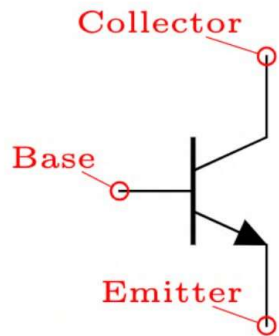
# Bipolar Junction Transistor

- **Current-controlled** transistor, 3 terminals – Base, Emitter, Collector
- $IV$  between  $C$  and  $E$  ( $I_C$  vs  $V_{CE}$ ) is controlled by base current,  $I_B$
- $IV$  is quite like MOSFET, but there are some differences
- We can use a S-model here too, but controlled by  $I_B$  (instead of  $V_{GS}$ )



# BJT vs MOSFET - Differences


## BJT

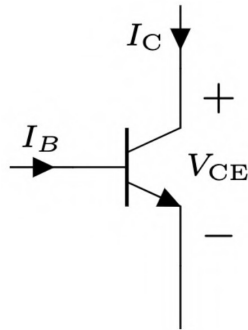

**Current** controlled,  $I_B$  controls ( $I_C$  vs  $V_{CE}$ )

**Base** current,  $I_B$ , is the control. Hence  $I_E \neq I_C$ , rather  
 $I_E = I_C + I_B$

## MOSFET

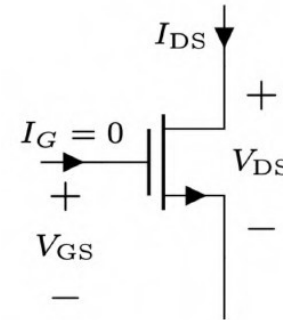


**Voltage** controlled,  $V_{GS}$  controls ( $I_{DS}$  vs  $V_{DS}$ )

**Gate** current,  $I_G$ , is always 0. Hence  $I_S = I_D = I_{DS}$ .

# BJT vs MOSFET - Differences

## BJT

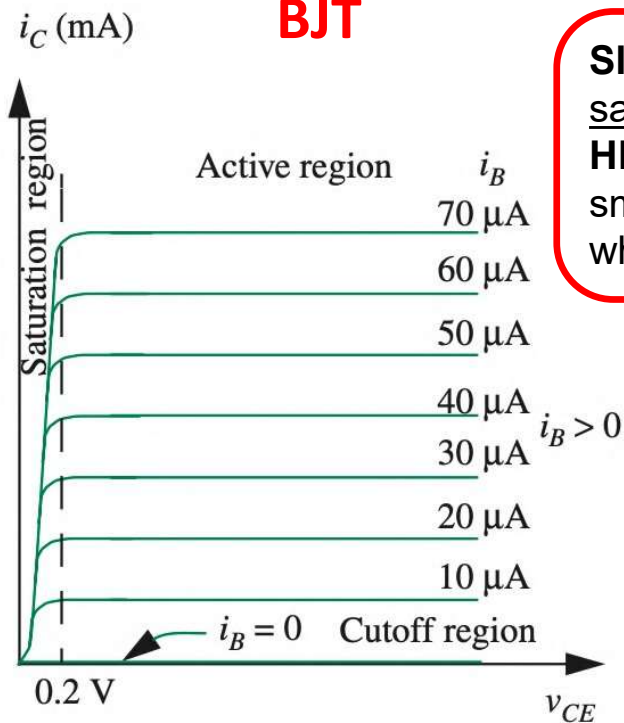


Slope in the saturation region is **HIGH**, hence very small resistance when "ON"

Slope in the Triode region is **LOW**, hence significant resistance when "ON"

Current in **active** region changes linearly with control  $I_B$ .  
Hence,  $I_C \propto I_B$


## MOSFET

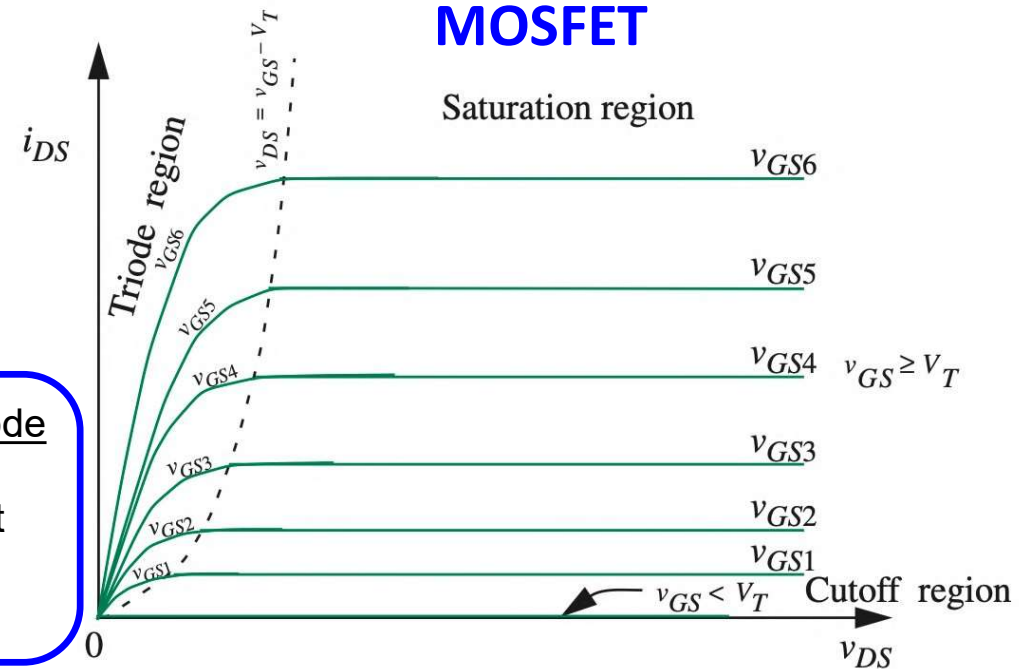

Current in **Saturation** region changes quadratically with control  $V_{GS}$ .  
Hence,  $I_{DS} \propto V_{GS}^2$

# BJT vs MOSFET - Differences

## BJT

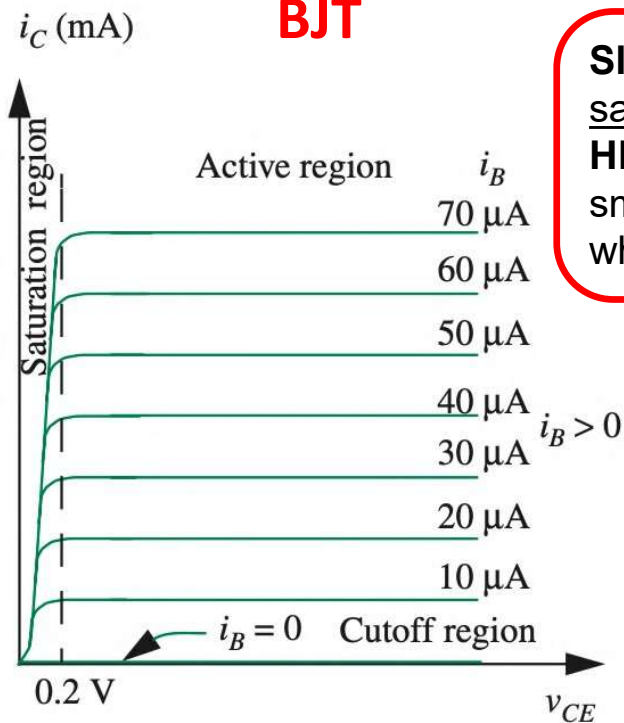


Slope in the saturation region is **HIGH**, hence very small resistance when "ON"

Slope in the Triode region is **LOW**, hence significant resistance when "ON"

Current in **active** region changes linearly with control  $I_B$ .  
Hence,  $I_C \propto I_B$


## MOSFET

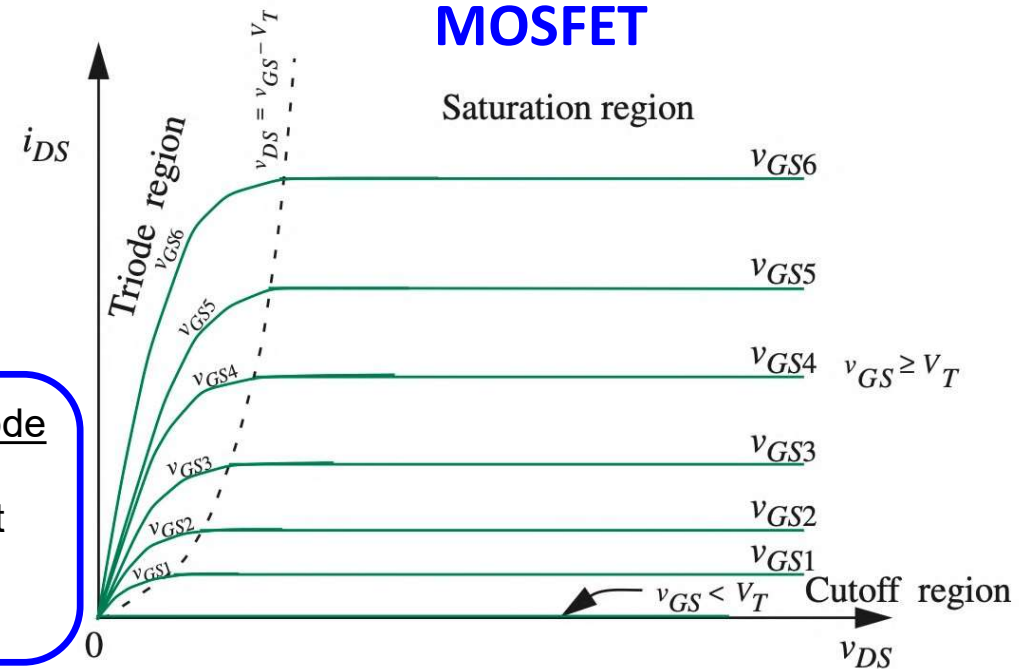

Current in **Saturation** region changes quadratically with control  $V_{GS}$ .  
Hence,  $I_{DS} \propto V_{GS}^2$


# BJT vs MOSFET - Similarities

## BJT

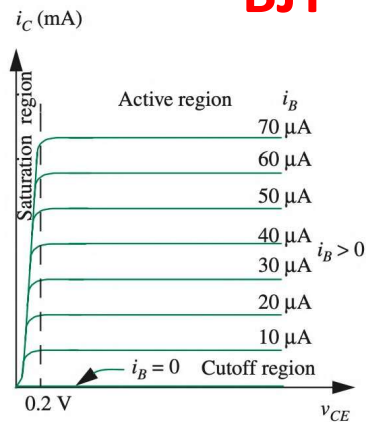

- **Saturation** mode for small  $V_{CE} (< 0.2 \text{ V})$
- Approximately Short circuit in **Saturation** mode ( $I_B$  **HIGH**)
- Open circuit in **Cutoff** mode ( $I_B = 0$ )
- Can use as a switch  $\Rightarrow$  S-Model!




## MOSFET

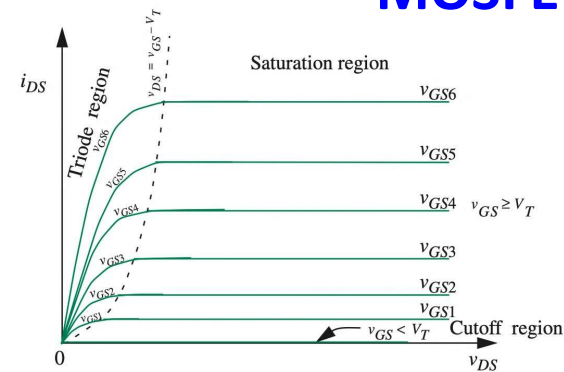

- **Triode** mode for small  $V_{DS} (< V_{OV})$
- Approximately Short circuit in **Triode** mode ( $V_{GS}$  **HIGH**)
- Open circuit in **Cutoff** mode ( $V_{GS} < V_T = 0$ )
- Can use as a switch  $\Rightarrow$  S-Model!
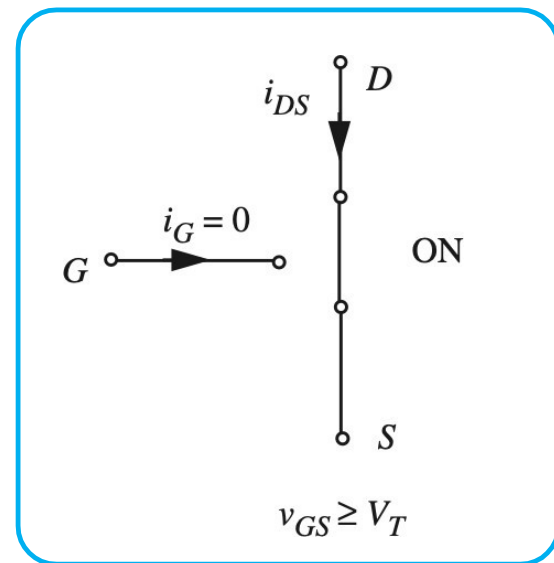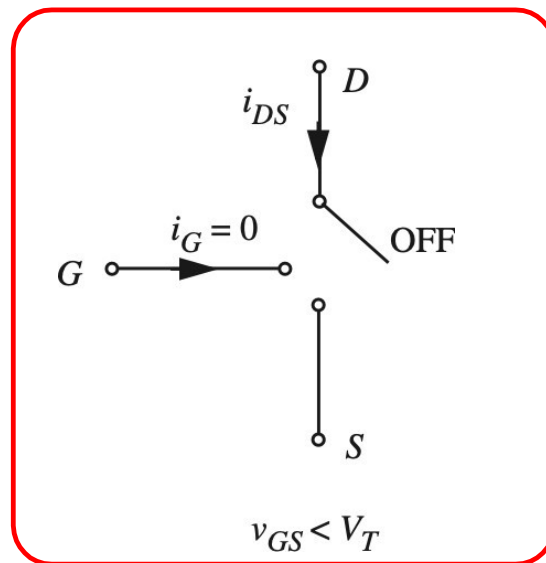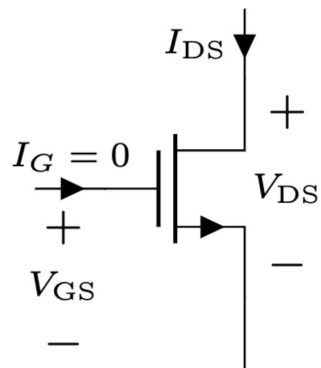
# MOSFET S-Model

- The MOSFET (approximately) behaves like a switch
- $C = V_{GS}$ . Here,  $C = "0" \Rightarrow V_{GS} < V_T$ , and  $C = "1" \Rightarrow V_{GS} > V_T$






# BJT S-Model

- The BJT (approximately) behaves like a switch


- $C = I_B$ . Here,  $C = \text{"0"} \Rightarrow I_B = 0$ , and  $C = \text{"1"} \Rightarrow I_B > I_{TH}$

	Representation
Logic 0	$I_B = 0$
Logic 1	$I_B > I_{TH}, I_B = \text{HIGH}$

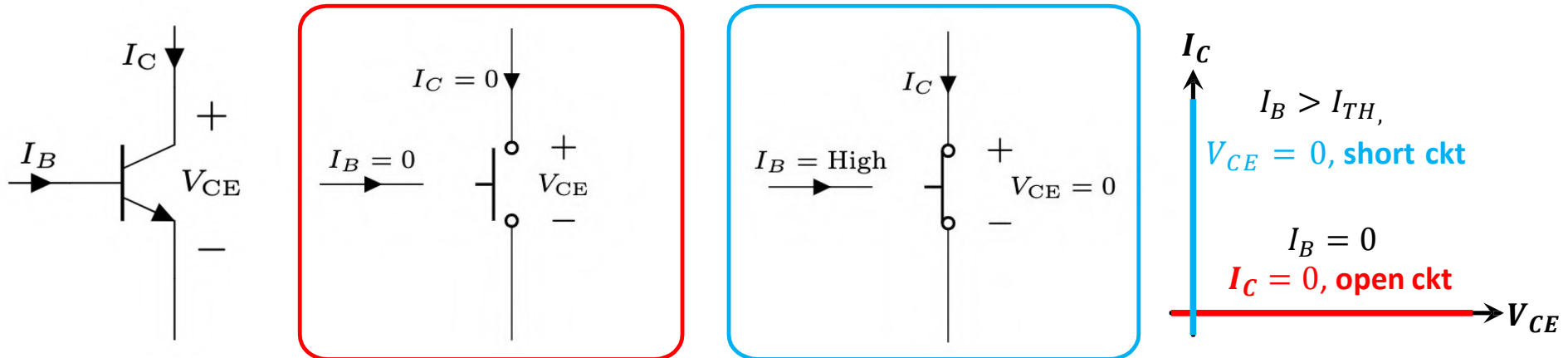

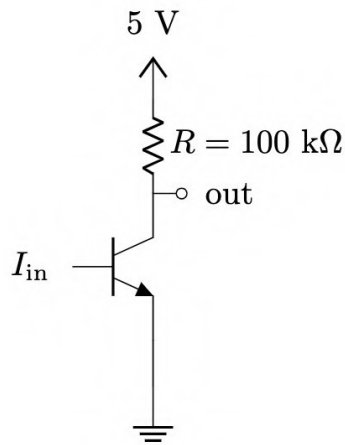
# Current-Controlled Logic Gates using BJT


- Just replace switches with BJTs!
- Major problem: Cannot cascade! (Why?)
  - Input Logic Variable: **Current**
  - Output Logic Variable: **Voltage**



BJT Inverter (NOT Gate)

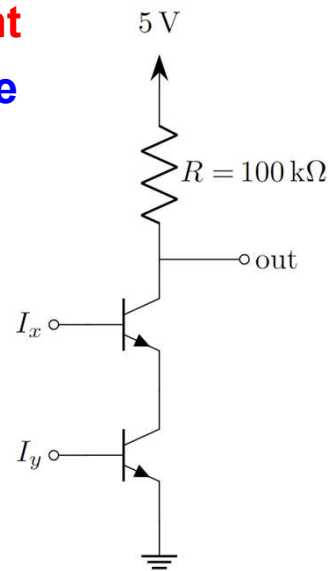


BJT NAND Gate

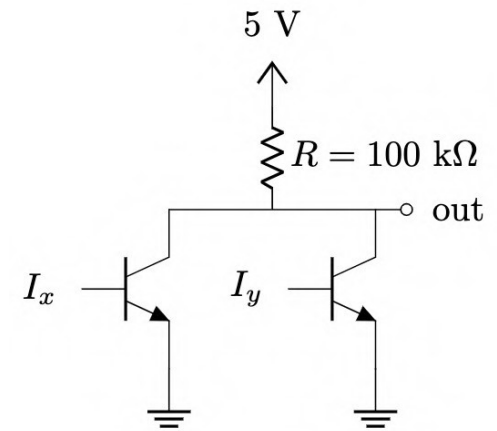


BJT NOR Gate
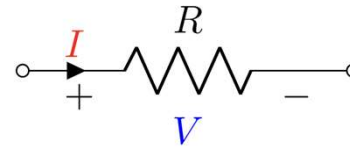
# From Current Controlled to Voltage Controlled

How to convert current  $I$  into voltage  $V$ ?



$$V = IR$$

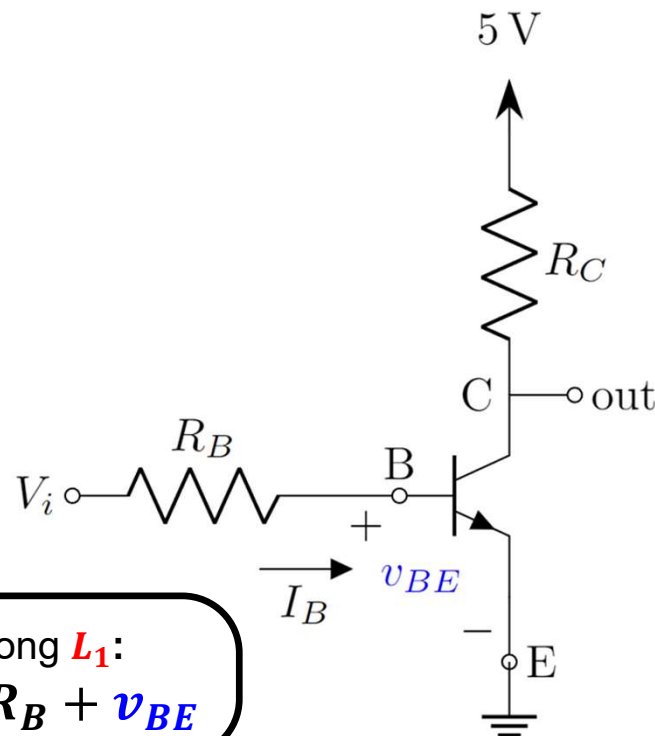

KVL along  $L_1$ :

$$V_i = I_B R_B + v_{BE}$$

$$V_i = I_B R_B + v_{BE}$$


$$I_B = \frac{V_i - v_{BE}}{R_B}$$

$v_{BE}$  depends on  $I_B$ .


How?
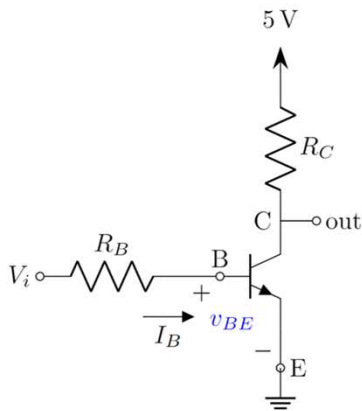
# Logic Gates using BJT


- Just replace switches with BJTs! – **and add a Resistor to the Base terminal**
- ~~Major problem: Cannot cascade!~~ (Why?) Can be cascaded.
  - Input Logic Variable: **Current-Voltage**
  - Output Logic Variable: **Voltage**



BJT Inverter (NOT Gate)

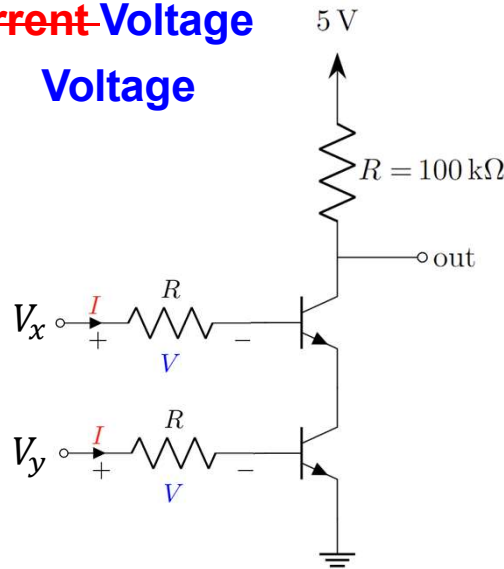


BJT NAND Gate

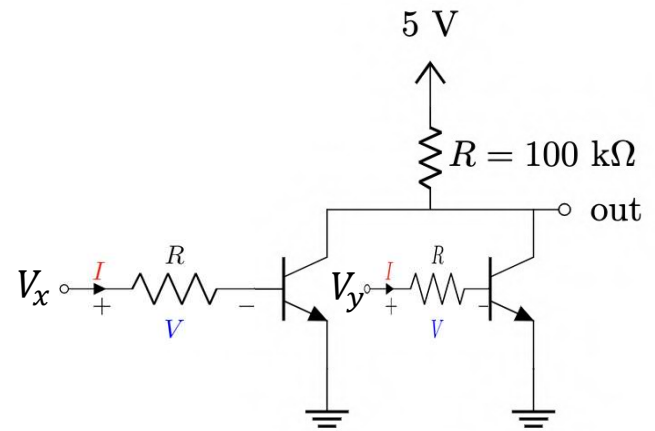

BJT NOR Gate
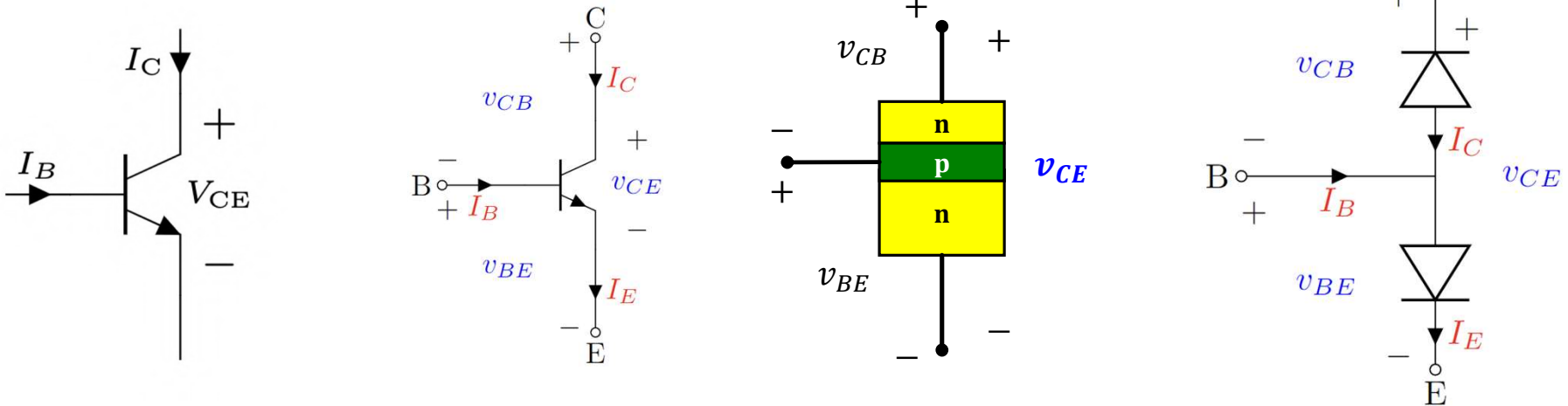
# Parameters of BJT


A BJT can be thought of as two “pn” junctions placed back-to-back.



1st pn junction: Across **Base – Emitter**: Voltage  $v_{BE}$   
 2nd pn junction: Across **Collector - Base**: Voltage  $v_{CB}$
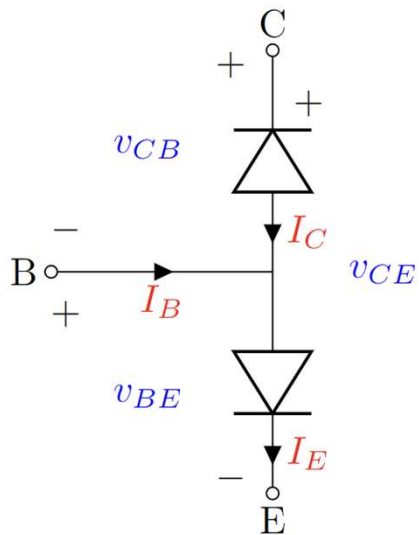
# Parameters of BJT

A BJT can be thought of as two “pn” junctions placed back-to-back.




Modes	BE Junction	$v_{BE}$	CB Junction	$v_{CB}$	$v_{CE}$
Cut-off	Reverse Bias	$v_{BE} < 0.7 \text{ V}$	Reverse Bias	$v_{CB} > -0.5 \text{ V}$	
Active	Forward Bias	$v_{BE} = 0.7 \text{ V}$	Reverse Bias	$v_{CB} > -0.5 \text{ V}$	$v_{CE} > 0.2 \text{ V}$
Saturation	Forward Bias	$v_{BE} = 0.7 \text{ V}$	Forward Bias	$v_{CB} = -0.5 \text{ V}$	$v_{CE} = 0.2 \text{ V}$
Reverse Active	Reverse Bias	$v_{BE} < 0.6 \text{ V}$	Forward Bias	$v_{CB} = -0.5 \text{ V}$	$v_{CE} < 0.2 \text{ V}$

1st pn junction: Across **Base – Emitter**: Voltage  $v_{BE}$   
 2nd pn junction: Across **Collector - Base**: Voltage  $v_{CB}$

$$v_{CE} = v_{CB} + v_{BE}$$
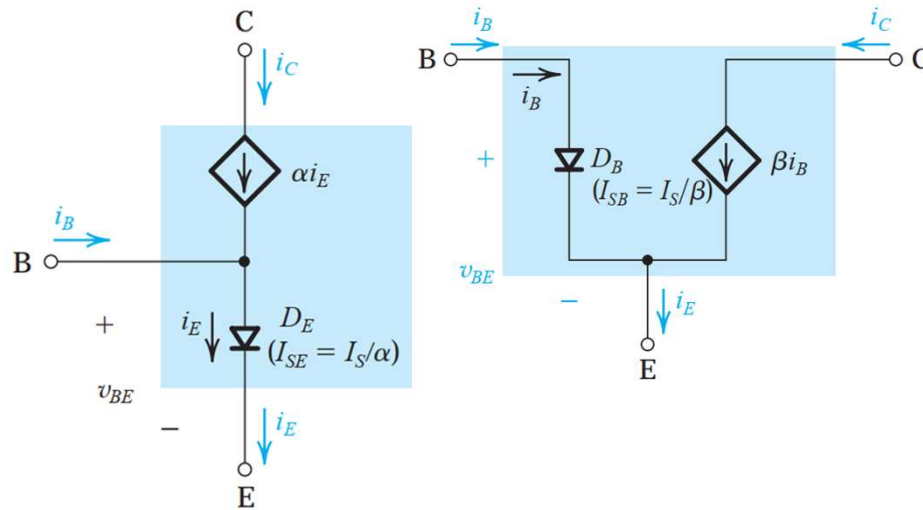
# Parameters of BJT: Active Mode

Equivalent circuit of an npn-BJT in **Active Mode**



Current relationships between the three currents in an npn BJT.

$$I_B + I_C = I_E$$

$\beta$ : Common Emitter Current Gain

$\alpha$ : Common Base Current Gain

$$I_C = \beta I_B$$

$$I_C = \alpha I_E$$


Only valid for active mode

1st pn junction: Across **Base – Emitter**: Voltage  $v_{BE}$   
 2nd pn junction: Across **Collector - Base**: Voltage  $v_{CB}$

$$v_{CE} = v_{CB} + v_{BE}$$
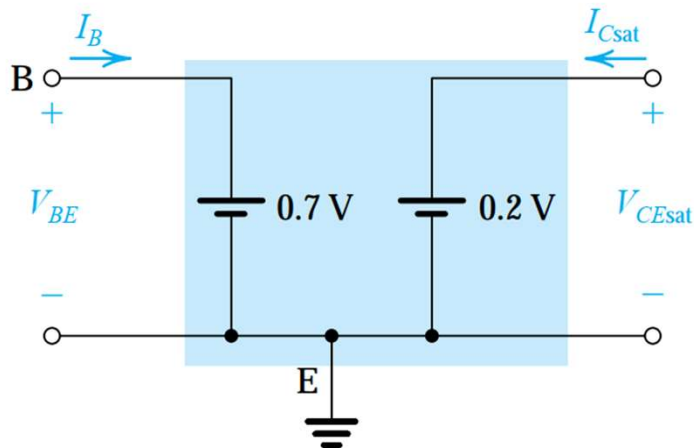
# Parameters of BJT: Saturation Mode

Equivalent circuit of an npn-BJT in **Saturation Mode**



Current relationships between the three currents in an npn BJT.

$$I_B + I_C = I_E$$

$$I_{C(sat)} < \beta I_B$$

$$I_C \neq \alpha I_E$$

$\beta$ : Common Emitter Current Gain  
 $\alpha$ : Common Base Current Gain

Only valid for **Saturation** mode

**Figure 6.20** A simplified equivalent-circuit model of the saturated transistor.


1st pn junction: Across **Base – Emitter**: Voltage  $v_{BE}$   
 2nd pn junction: Across **Collector - Base**: Voltage  $v_{CB}$

$$v_{CE} = v_{CB} + v_{BE}$$


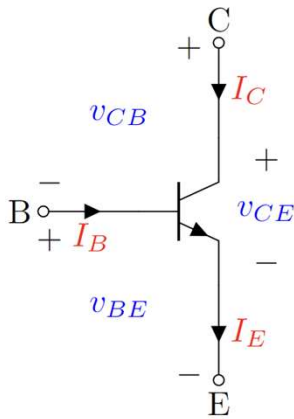
# Parameters of BJT

A BJT can be thought of as two “pn” junctions placed back-to-back.



Modes	Conditions!
Cut-off	$v_{BE} < 0.7\text{ V}$ and $v_{CB} > -0.5\text{ V}$
Active	$v_{BE} = 0.7\text{ V}$ and $v_{CE} > 0.2\text{ V}$
Saturation	$v_{BE} = 0.7\text{ V}$ and $v_{CE} = 0.2\text{ V}$ and $\frac{I_C}{I_B} < \beta$
Reverse Active	$v_{BC} = 0.5\text{ V}$ and $v_{EC} > 0.2\text{ V}$

1st pn junction: Across **Base – Emitter**: Voltage  $v_{BE}$   
 2nd pn junction: Across **Collector - Base**: Voltage  $v_{CB}$

$$v_{CE} = v_{CB} + v_{BE}$$

# Solving Circuits with ~~MOSFET~~ BJT

- Use **Method of Assumed State!**
- **Three steps:**
  - **Assume:** One of the modes  
(Cutoff, Triode **Saturation**, ~~Saturation~~ **Active**)
  - **Solve:** Use corresponding equation and KCL + KVL with currents
  - **Verify:** Check if the conditions of  $V_{GS}$   $v_{BE}$  and  $V_{DS}$   $v_{CE}$  are satisfied. If not, repeat.
- Might need to solve quadratic equation ( $ax^2 + bx + c = 0$ ).
- If we get two roots, choose the one that's *favorable* to your assumption

# BJT Problem 1

Analyze the circuit to find  $I_C$  and  $v_{out}$  using the Method of Assumed State. Here, the input of the BJT is  $V_i = 1\text{ V}$ . You must validate your assumptions.

## Assume:

Let the BJT be in **ACTIVE** mode

So,  $v_{BE} = 0.7\text{ V}$   
 $v_{CE} > 0.2\text{ V}$

## Solve:

Equations:  $I_B = \frac{V_i - v_{BE}}{R_B} = \frac{1 - 0.7}{100} \text{ mA} = 3\text{ }\mu\text{A}$


$$I_C = \beta I_B = 100 \times 3 \times 10^{-3} \text{ mA} = 0.3 \text{ mA}$$

$$v_{out} = 10 - I_C R_C = (10 - 0.3 \times 3) \text{ V} = 9.1 \text{ V}$$

**Verify:** For **ACTIVE** condition  $\rightarrow v_{CE} > 0.2\text{ V}$

Here,  $v_{CE} = v_{out} = 9.1\text{ V} > 0.2\text{ V}$

**Assumption is Correct!**

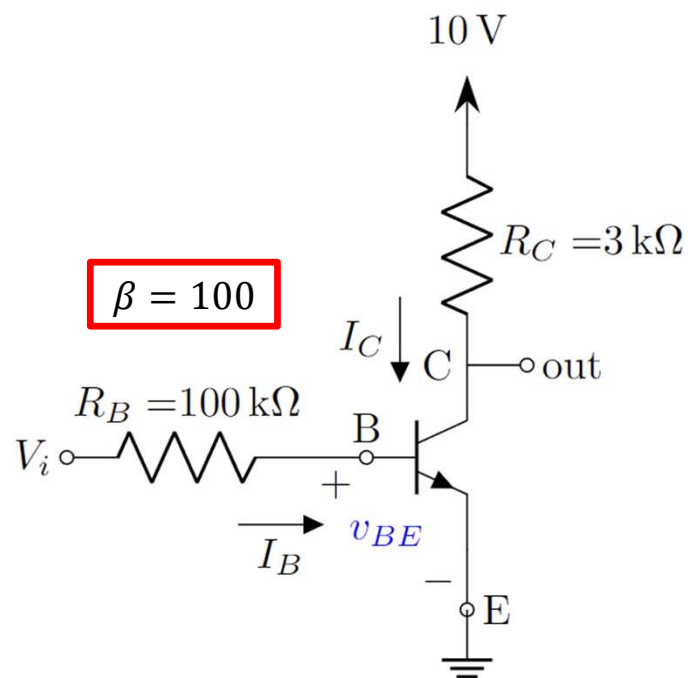

# BJT Problem 1

Analyze the circuit to find  $I_C$  and  $v_{out}$  using the Method of Assumed State. Here, the input of the BJT is  $V_i = 5\text{ V}$ . You must validate your assumptions.

## Assume:

Let the BJT be in **ACTIVE** mode

So,  $v_{BE} = 0.7\text{ V}$   
 $v_{CE} > 0.2\text{ V}$

## Solve:

Equations:  $I_B = \frac{V_i - v_{BE}}{R_B} = \frac{5 - 0.7}{100} \text{ mA} = 43\text{ }\mu\text{A}$


$$I_C = \beta I_B = 100 \times 43 \times 10^{-3} \text{ mA} = 4.3\text{ mA}$$

$$v_{out} = 10 - I_C R_C = (10 - 4.3 \times 3) \text{ V} = -2.9\text{ V}$$

**Verify:** For **ACTIVE** condition  $\rightarrow v_{CE} > 0.2\text{ V}$

Here,  $v_{CE} = v_{out} = -2.9\text{ V} \not> 0.2\text{ V}$

**Assumption is Wrong!**

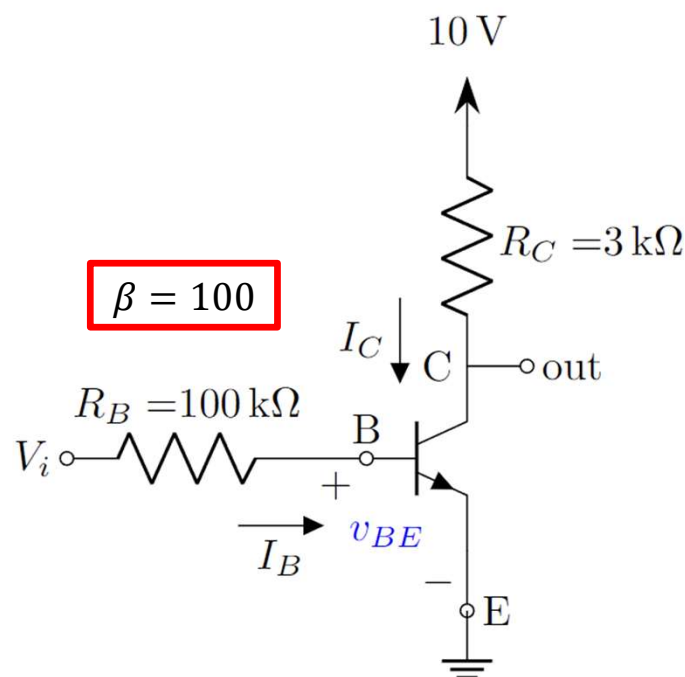

# BJT Problem 1

Analyze the circuit to find  $I_C$  and  $v_{out}$  using the Method of Assumed State. Here, the input of the BJT is  $V_i = 5\text{ V}$ . You must validate your assumptions.

## Assume:

Let the BJT be in **Saturation** mode

So,  $v_{BE} = 0.7\text{ V}$  and  $\frac{I_C}{I_B} < \beta$

$$v_{CE} = 0.2\text{ V}$$

## Solve:


Equations:  $I_B = \frac{V_i - v_{BE}}{R_B} = \frac{5 - 0.7}{100} \text{ mA} = 43\text{ }\mu\text{A}$

$$I_C = \beta I_B \frac{10 - v_{CE}}{R_C} = \frac{10 - 0.2}{3} \text{ mA} = 3.27\text{ mA}$$

$$v_{out} = v_{CE} = 0.2\text{ V}$$

**Verify:** For **Saturation** condition  $\rightarrow \frac{I_C}{I_B} < \beta$

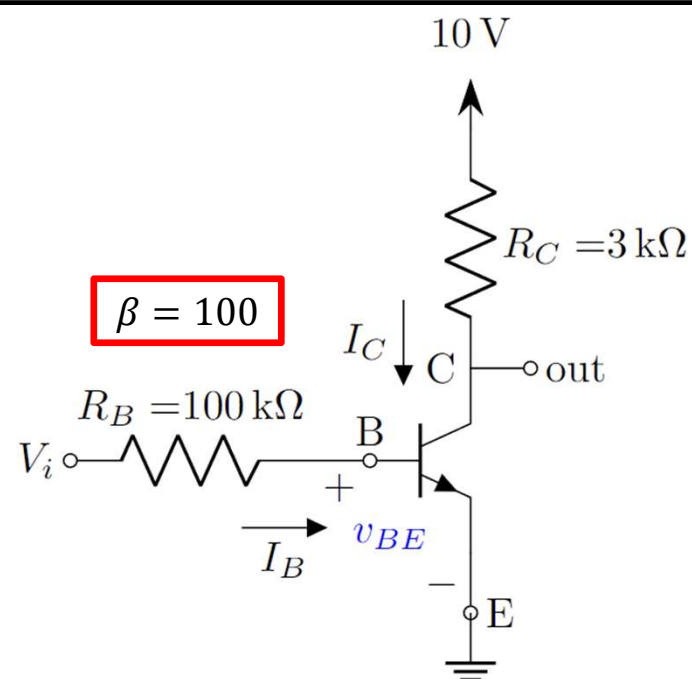Here,  $\beta = 100$   $\frac{I_C}{I_B} = \frac{3.27}{0.043} = 76 < 100$



**Assumption is Correct!**

# BJT Problem 2

Analyze the circuit to find  $I_B$ ,  $I_C$ ,  $I_E$  and  $v_{out}$  using the Method of Assumed State. You must validate your assumptions.

## Assume:

Let the BJT be in **Active** mode

So,  $v_{BE} = 0.7 \text{ V}$   
 $v_{CE} > 0.2 \text{ V}$





## Solve:

Equations:

$$I_E = \frac{v_E - (-10)}{10} = \frac{-0.7 + 10}{10} \text{ mA} = \mathbf{0.93 \text{ mA}}$$

$$I_B = \frac{1}{\beta} I_C = \frac{1}{\beta} \cdot \alpha I_E = \frac{1}{\beta} \cdot \frac{\beta}{\beta + 1} I_E = \frac{1}{\beta + 1} I_E = \mathbf{9.21 \text{ }\mu\text{A}}$$
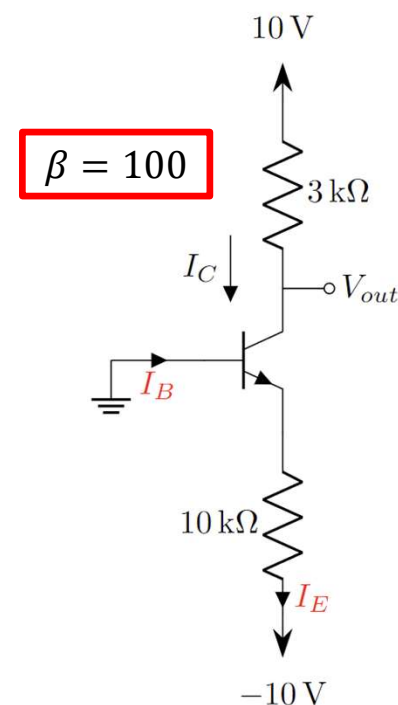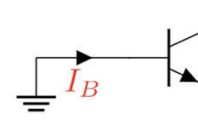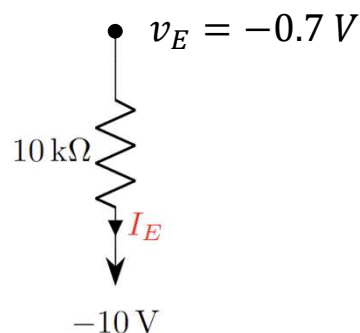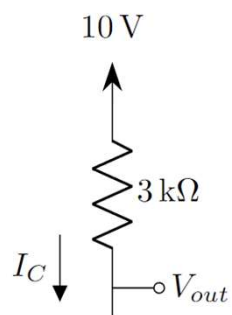
$$\begin{aligned} v_{out} = v_C &= 10 - 3I_C = 10 - 3\beta I_B \\ &= (10 - 3 \cdot 100 \cdot 9.207 \times 10^{-3}) \text{ V} \\ &= \mathbf{7.237 \text{ V}} \end{aligned}$$



# BJT Problem 2

Analyze the circuit to find  $I_B$ ,  $I_C$ ,  $I_E$  and  $v_{out}$  using the Method of Assumed State. You must validate your assumptions.

## Assume:

Let the BJT be in **Active** mode

So,  $v_{BE} = 0.7 \text{ V}$   
 $v_{CE} > 0.2 \text{ V}$

## Solve:

Equations:

$$I_E = 0.93 \text{ mA}$$



$$I_B = 9.21 \text{ } \mu\text{A}$$

$$v_{out} = v_C = 7.237 \text{ V} \quad v_B = 0 \text{ V} \quad v_E = -0.7 \text{ V}$$

**Verify:** For **ACTIVE** condition  $\rightarrow v_{CE} > 0.2 \text{ V}$


Here,  $v_{CE} = (7.237 + 0.7) \text{ V} = 7.937 \text{ V} > 0.2 \text{ V}$

**Assumption is Correct!**

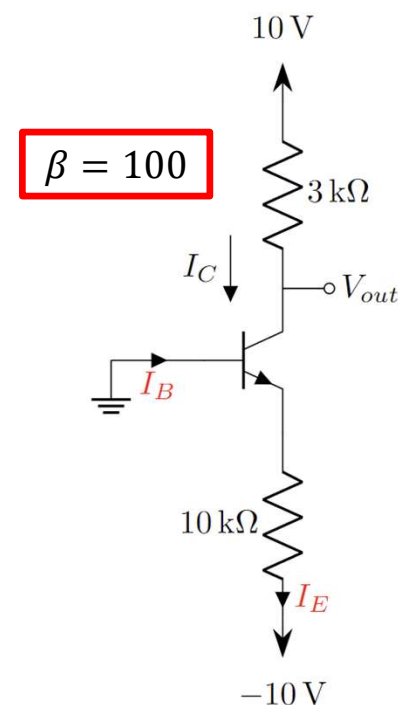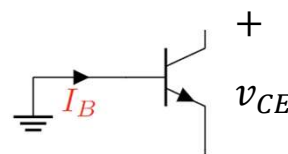

## Problem 3

Example 2:

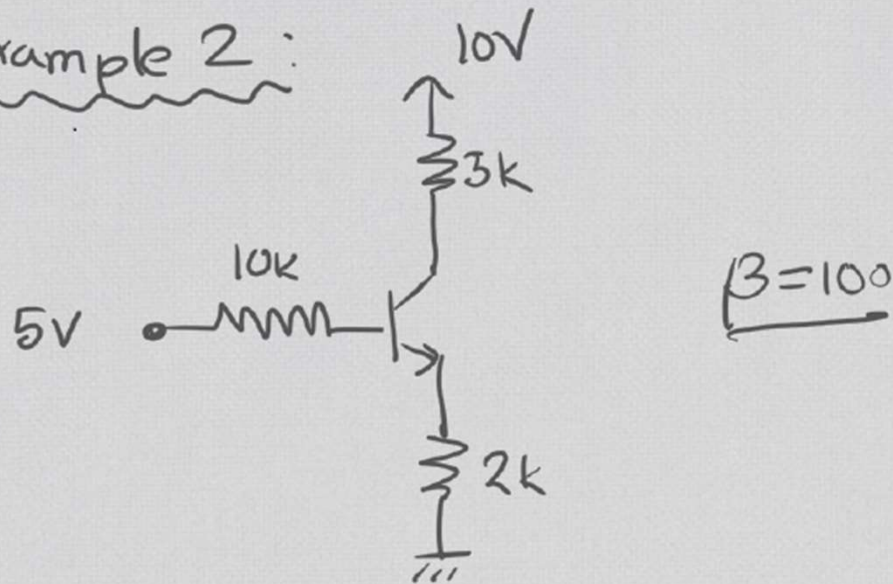

Find  $I_B$ ,  $I_C$ ,  $I_E$  and  $V_{CE}$ .

Solution in Example 2 of BJT2 slide