

Assignment 03

BRAC University
Semester: Spring 2024

Course No: CSE251

Marks: 40

Course Title: Electronic Devices and Circuits

Deadline: April 10, 2024-11:59 pm

Faculty: AGS


1. (CO1)

a) **Using** ideal MOSFETs (S-model) to implement the function-

$$f = \left((\overline{A \cdot C}) + B + D \right) \cdot E \quad [5]$$

b) **Draw** VTC of 2 input NOR Gate. [5]

2. (CO2) [10]

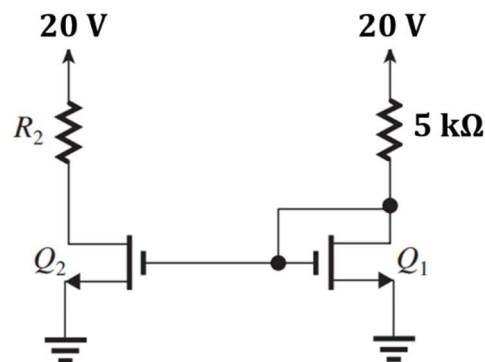

In the circuit above, the MOSFETs have the following parameters, $k'_n = 2 \text{ mA/V}^2$, $W/L = 2.5$, $V_T = 0.5 \text{ V}$.

(a) **Find out** the operating mode of Q1 [Hint: For Triode mode $V_{ds} < V_{ov}$ and for Saturation $V_{ds} \geq V_{ov}$] [3]

(b) **Determine** the value of R_2 that results in Q2 operating at the edge of the saturation region. [3]

[Hint: at the edge of the saturation region $V_{DS} = V_{OV}$]


(c) **Calculate the on-state resistance, R_{on}** for Q2. [2]

(d) An inverter is designed using Q2 and a 10k resistor. **Draw** the VTC graph for the inverter. [2]

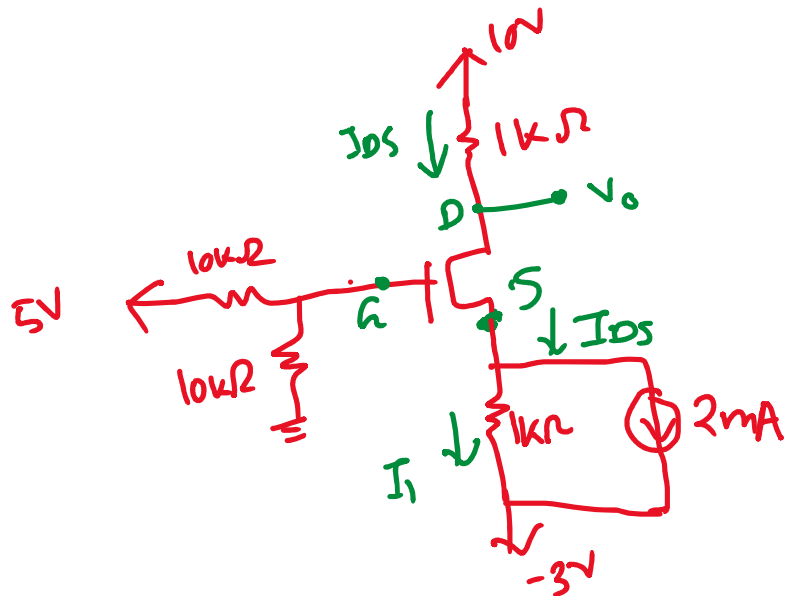3. (CO2) [10]

Analyze the circuit to find I_{DS} and V_O using Method of Assumed State. You must validate your assumptions.

[Hint: Gate current $I_G = 0\text{mA}$. Assume $I_{DS} = x$, Apply KCL at source (S) terminal to find relation between V_S and I_{DS}]



$$V_T = 1\text{V}$$

$$k = k_n' \frac{W}{L} = 2 \text{ mA/V}^2$$

4. (CO2) [10]

Analyze the circuit to find I_D and V_{DS} using Method of Assumed State. You must validate your assumptions.

[Hint: Gate current $I_G = 0\text{mA}$. Assume $I_D = x$, Express V_S & V_D in terms of I_D]

$$V_T = 1\text{V}$$

$$k = k_n' \frac{W}{L} = 2 \text{ mA/V}^2$$

