

BRAC University

Semester: Fall 2023

Course Code: CSE250

Circuits and Electronics

Section: 26

Faculty: A G S, E R D

Set

E

Assessment: Lab Test


Duration: 30 minutes

Date: December 4,



2023

Full Marks: 10

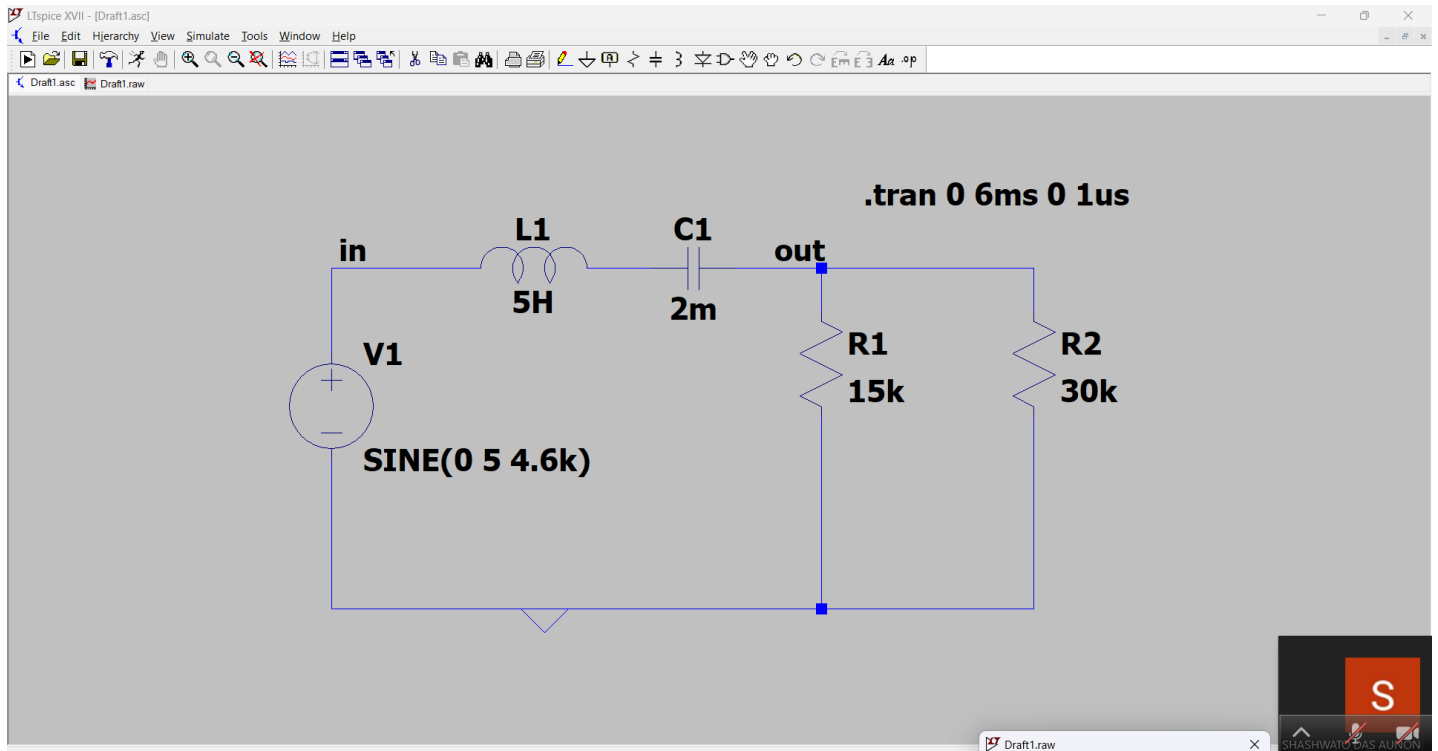1. Insert the screenshots of schematic diagrams (simulation commands must be visible).



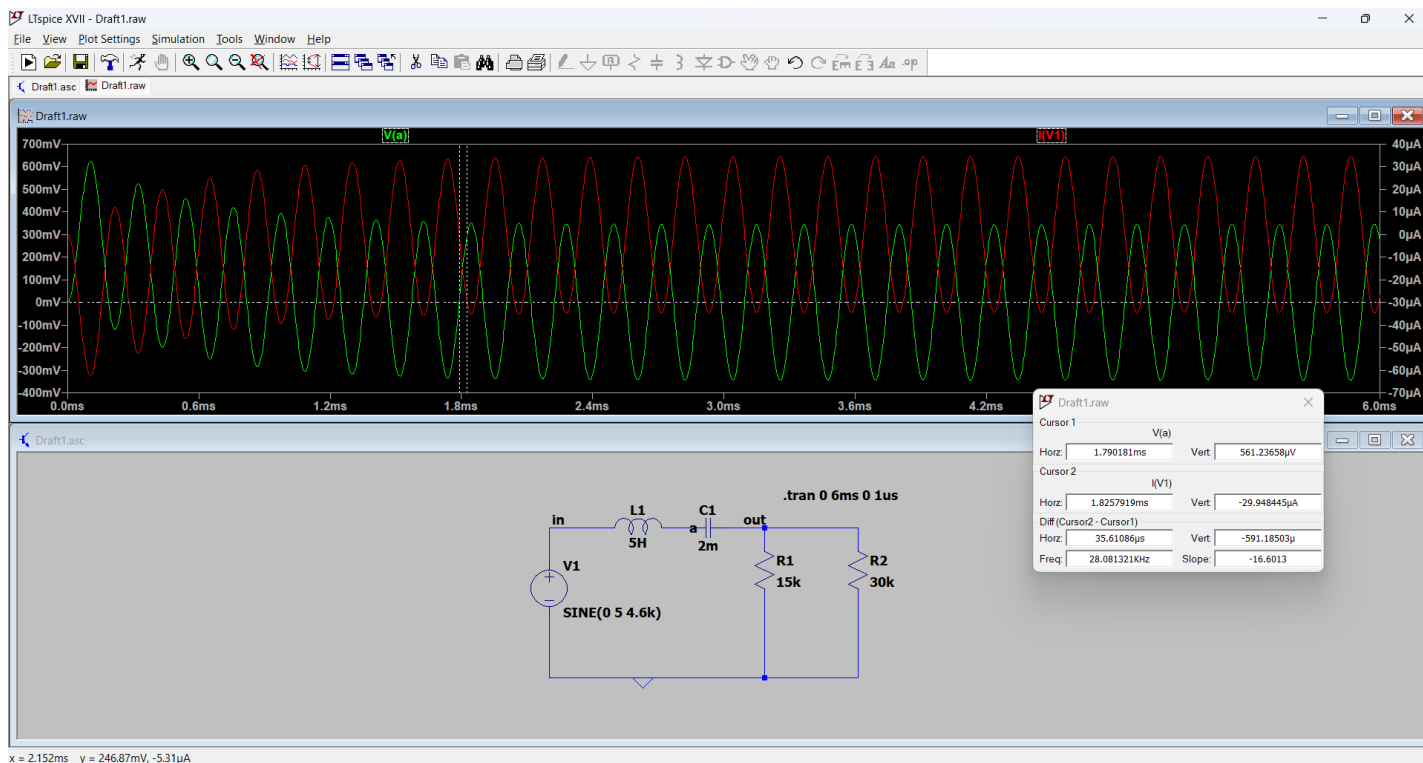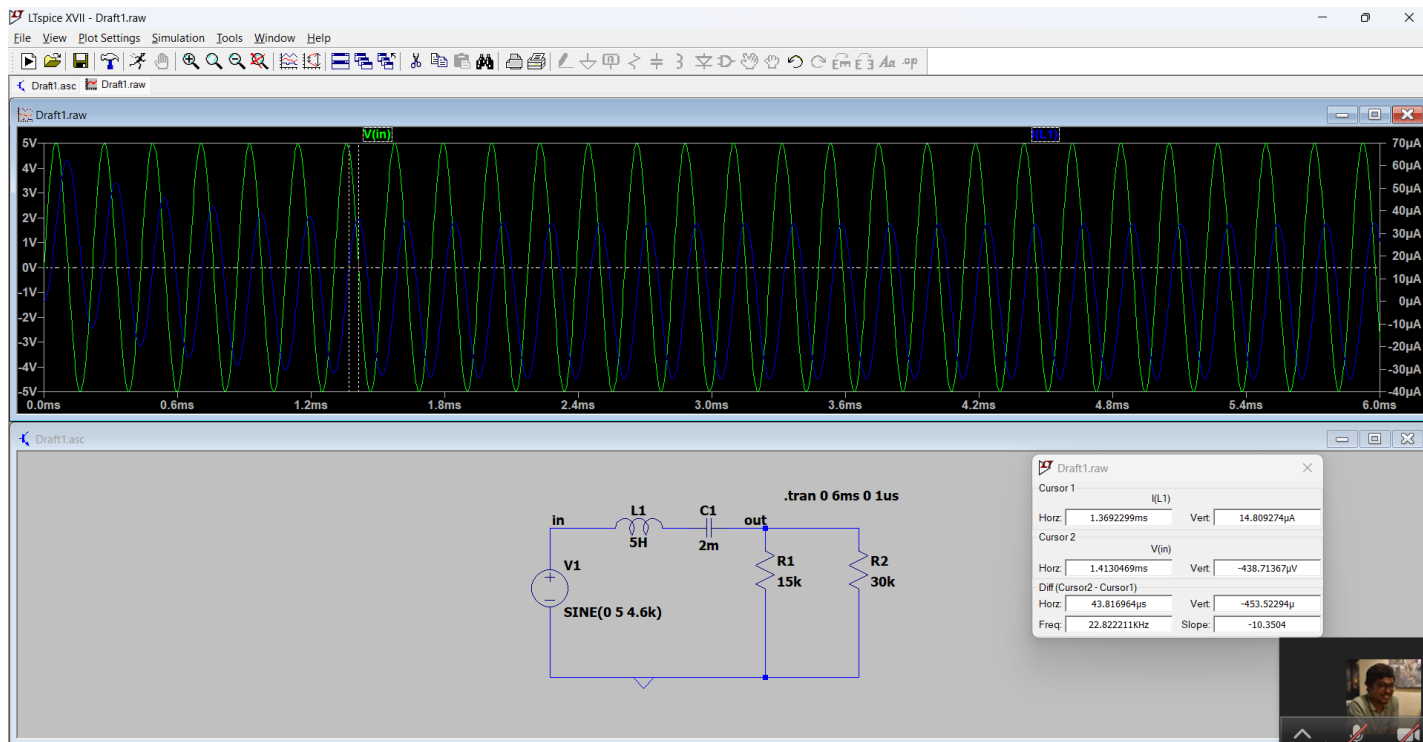2. Insert the screenshots of output graphs (if any).



3. Write down the answer values (if any).

Phase difference = 72.5652 degree

Phase difference = 90 degree

4. Submit the docx/pdf file and the zip file in the form provided.

You can convert a docx file by going to File>Export>Create PDF/XPS.

