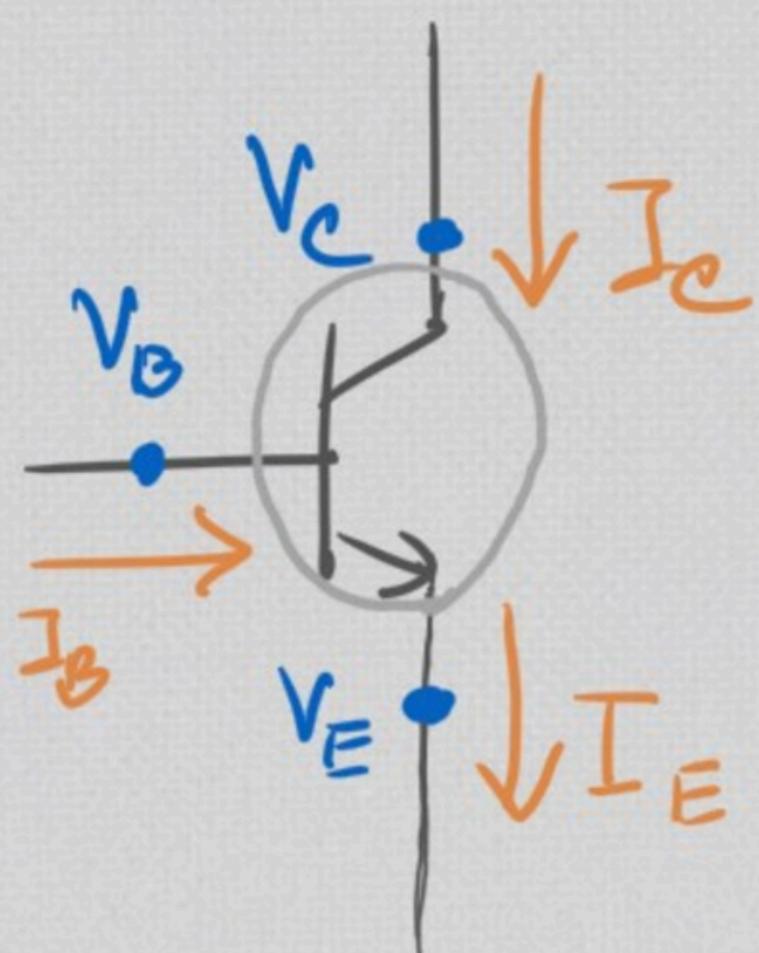


## BJT in DC

KCL at supernode BCE  $\Rightarrow$



$$I_E = I_C + I_B$$

$\hookrightarrow$  True for any mode.

In ACTIVE,  $I_C = \beta I_B$   $\rightarrow$  ONLY in ACTIVE

$$\therefore I_E = I_C + \frac{I_C}{\beta} = \frac{1+\beta}{\beta} I_C$$

$$\therefore I_C = \frac{\beta}{1+\beta} I_E \quad \rightarrow \text{ONLY in ACTIVE}$$

We define  $\frac{\beta}{1+\beta}$  as  $\alpha$


So,  $I_C = \alpha I_E$

The typical value for  $\beta = 100$ . So,  $\alpha \approx 0.99$  So, we can say, during ACTIVE region,  $I_C \approx I_E$ .

In SATURATION,  $V_{CE} = V_{CE(sat)} = 0.2V$ . This is the lowest possible value of  $V_{CE}$ . This implies that the voltage  $V_{RE}$  in the CE configuration can be, at

max,  $V_{CC} - 0.2V$ .

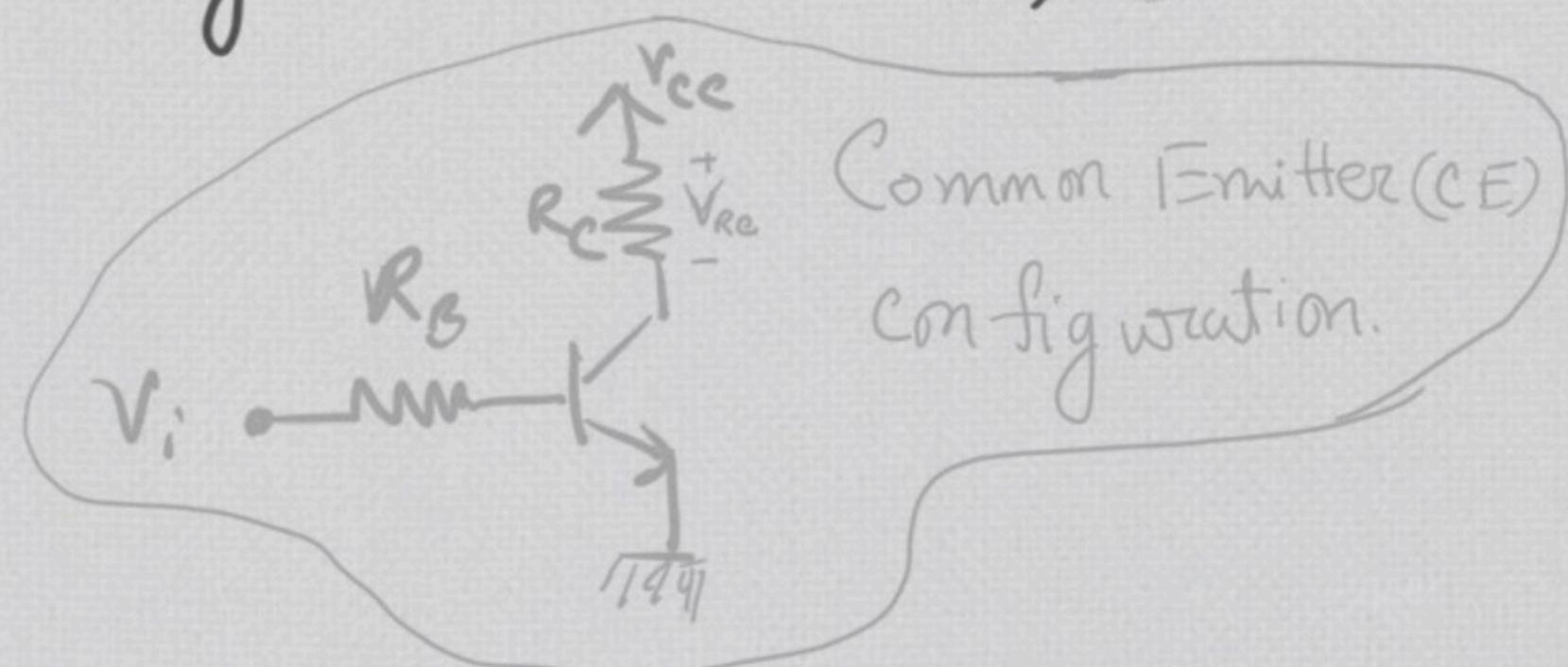$\hookrightarrow$  That is, 0.2V less than supply



# How to solve circuits with BJT?

⇒ Our old friend, Method of assumed state!

For BJT

① If assume in ACTIVE mode

$$V_{BE} = 0.7, I_C = \beta I_B \Rightarrow \text{Eqn true for ACTIVE}$$

You must show  $V_{CE} > 0.2$

② If assume in SATURATION

$$V_{BE} = 0.8, V_{CE} = 0.2 \Rightarrow \text{Eqn true for SAT.}$$

You must show  $I_C < \beta I_B$ ,

that is  $\frac{I_C}{I_B} < \beta$

3 steps

① Assume a state. There are 3 possible states: ACTIVE, SATURATION, CUTOFF

② Solve the ckt and find  $I_C, I_B, V_{CE}, V_{BE}$

③ Verify your assumption.  
If wrong, repeat ①, ②, ③


③ If assume in CUTOFF

$$\boxed{I_C = I_B = I_E = 0} \Rightarrow \text{Eqn true for CUTOFF}$$

You must show  $V_{BE} \leq 0.7V$  and  $V_{CE} > 0.2$


\*must show ⇒ condition

Example 1:

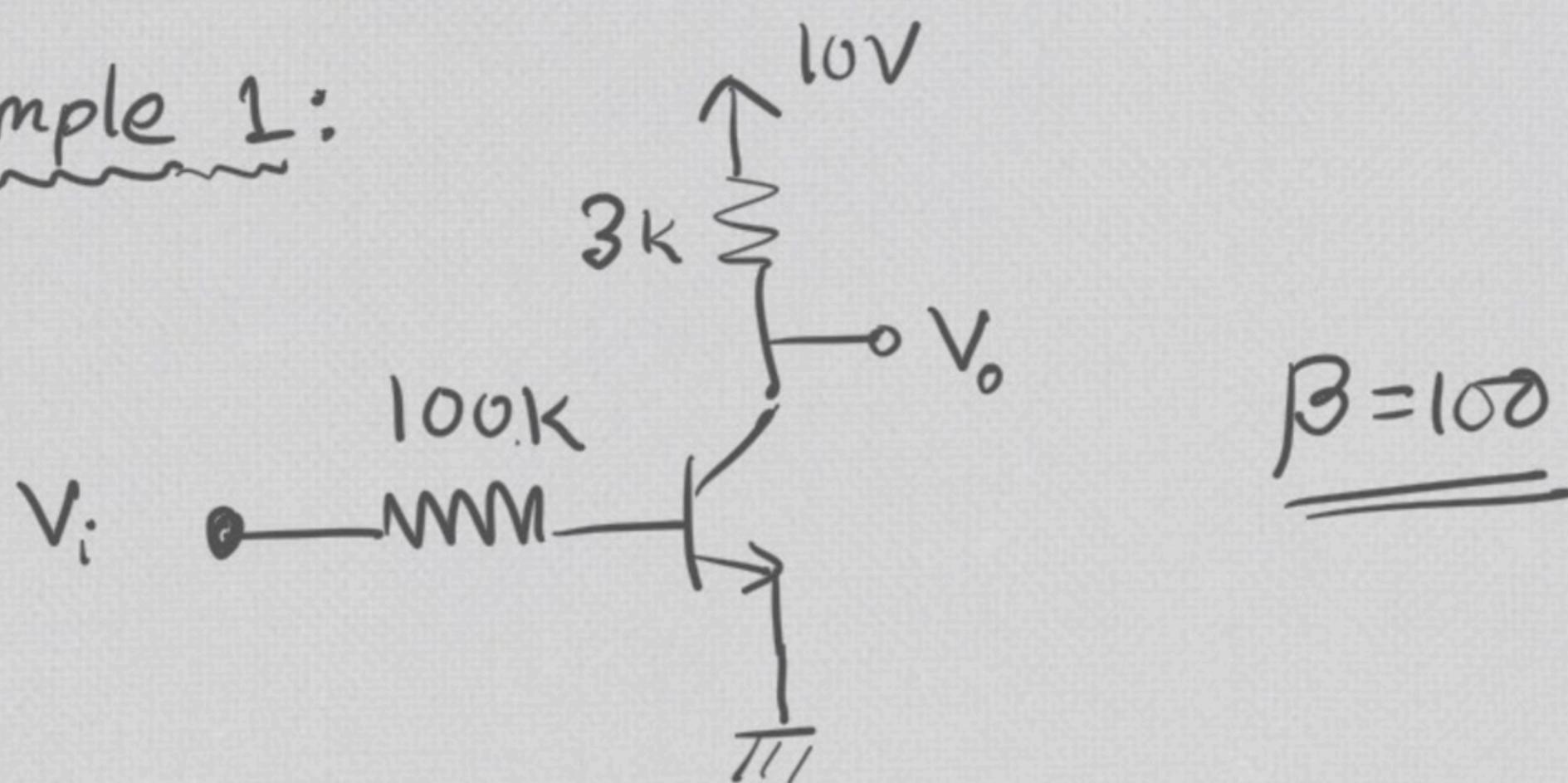

Find  $V_o$  for ①  $V_i = 1V$  ②  $V_i = 5V$

Sol:

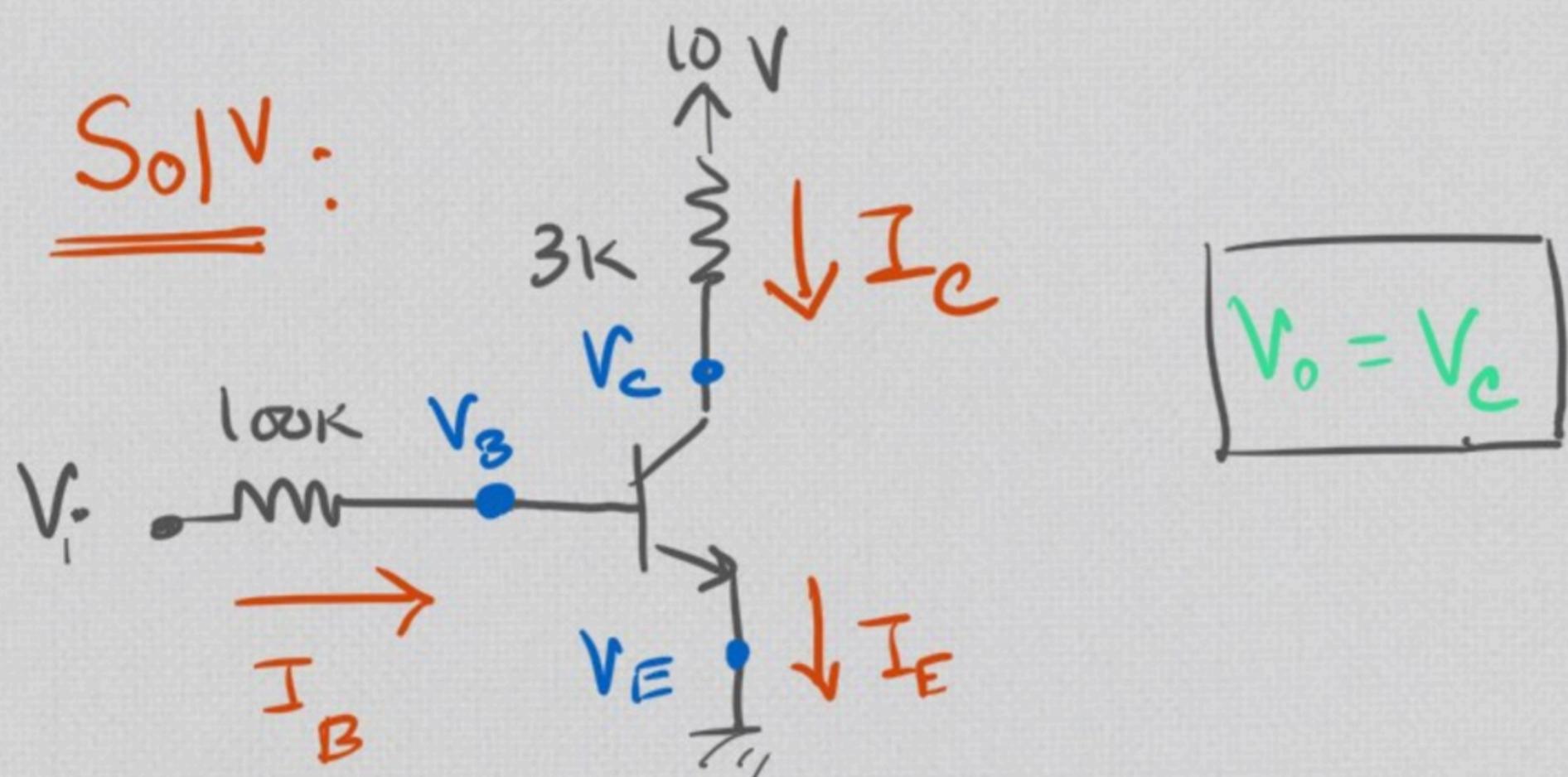

Since  $V_i > 0.7V$  in both ① and ②, it will

be either in ACTIVE or SATURATION

$$BE = 0V \Rightarrow V_{BE} = 0.7V$$

$$\text{since } V_E = 0V \Rightarrow V_B - V_E = 0.7V =$$

$$\Rightarrow V_B = 0.7V$$

④ Assume BJT in ACTIVE

$$\therefore I_B = \frac{V_i - V_B}{R_B} = \frac{1 - 0.7}{100} = 0.003 \text{ mA}$$

$$= 3 \mu A$$

Since active,  $I_C = \beta I_B = 100 \times 0.003 = 0.3 \text{ mA}$

from the circuit,

$$I_C = \frac{10 - V_C}{R_C}$$

$$\Rightarrow V_C = 10 - R_C I_C = 10 - 3 \times 0.3$$

$$\Rightarrow \boxed{V_o = V_C = 9.1 \text{ V}}$$

VERIFICATION: Since we assumed ACTIVE, we

need to check if  $V_{CE} > 0.2 \text{ V}$

Since  $V_E = 0 \Rightarrow V_{CE} = V_C - V_E = 9.1 \text{ V}$ .  $\Rightarrow$  Assumption Correct  
(yay!)

⑤ Assume BJT in ACTIVE

$$\Rightarrow I_B = \frac{V_i - V_B}{R_B} = \frac{5 - 0.7}{100} = 0.043 \text{ mA}$$

$$\Rightarrow I_C = \beta I_B = 4.3 \text{ mA}$$

$$\Rightarrow V_o = V_C = 10 - I_C R_C = 10 - 3 \times 4.3 = -2.9 \text{ V}$$

VERIFICATION:  $V_{CE} = -2.9V \therefore V_{CE} < 0.2V$

$\Rightarrow$  Assumption WRONG!  $\therefore$

Now assume in SATURATION

$$\therefore V_{CE} = 0.2V$$

since  $V_E = 0V$  and  $V_{CE} = V_C - V_E$

$$\therefore V_C = V_o = 0.2V.$$

$\rightarrow$  Because SAT  $\Rightarrow V_{BE} = 0.8V$

$$I_B = \frac{V_i - V_B}{R_B} = \frac{5 - 0.8}{100} = 0.043mA$$


$$I_C = \frac{10 - V_C}{R_C} = \frac{10 - 0.2}{3} = 3.2mA$$

VERIFICATION: Since we've assumed saturation,

we need to show  $\frac{I_C}{I_B} < \beta$ . Now,  $\frac{I_C}{I_B} = \frac{3.2}{0.043} = 76$

$\frac{I_C}{I_B} < 100 \Rightarrow$  Assumption CORRECT.  $\therefore$

Example 2:

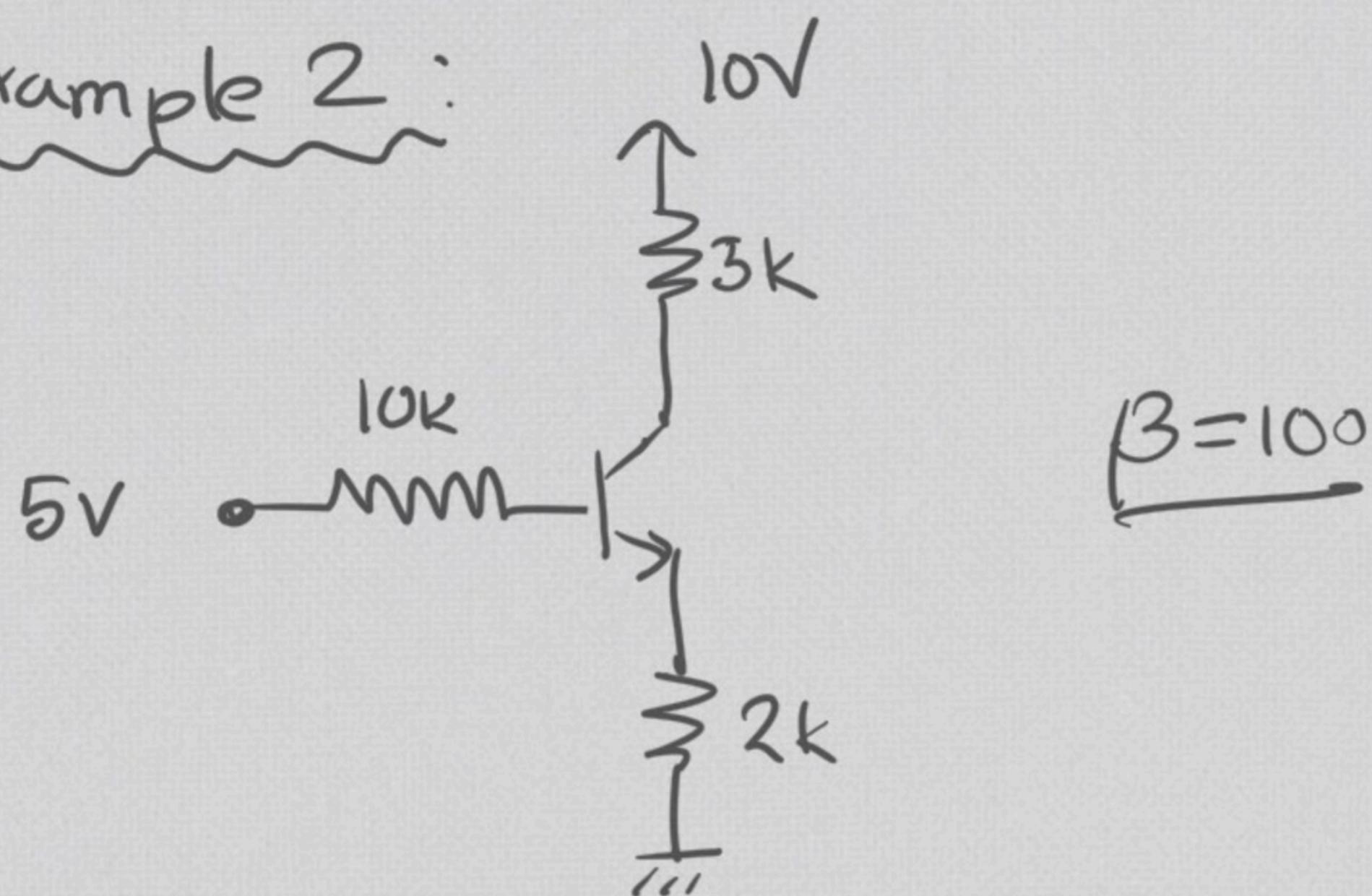

Find  $I_B$ ,  $I_C$ ,  $I_E$  and  $V_{CE}$ .


Soln: Assume in ACTIVE

$$\Rightarrow I_C = \alpha I_E \quad \text{--- (i)}$$

$$I_C = \beta I_B \quad \text{--- (ii)}$$

from (i) and (ii),  $\beta I_B = \alpha I_E$
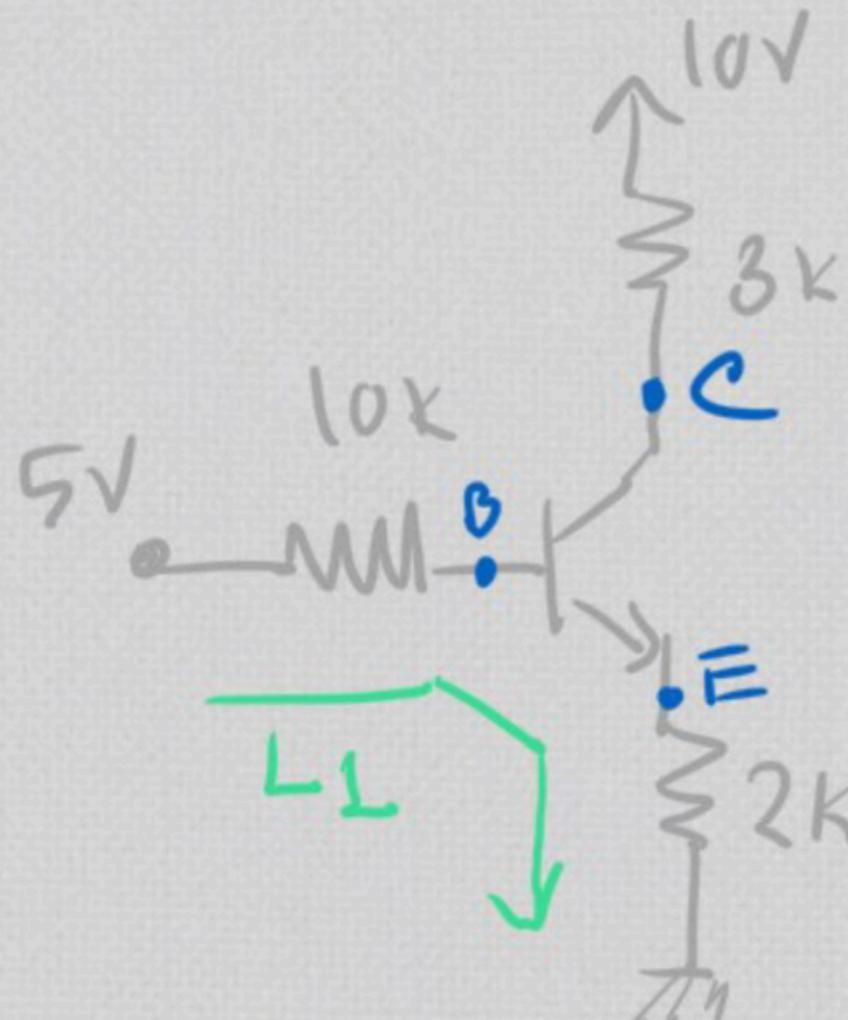
$$\Rightarrow I_E = \frac{\beta}{\alpha} I_B \quad \text{--- (iii)}$$



Writing KVL along  $L_L \Rightarrow$

$$5 = 10I_B + V_{BE} + 2I_E$$

$$\Rightarrow 5 = 10I_B + 0 \quad \text{from (iii)} + 2 \times \frac{\beta}{\alpha} I_B$$

$$\Rightarrow I_B = 0.02 \text{ mA}$$

Since assumed ACTIVE,  $V_{BE} = 0.7$

$$\therefore I_C = \beta I_B = 100 \times 0.02 = 2 \text{ mA}$$

$$\therefore \boxed{I_C = 2 \text{ mA}}$$

$$\therefore I_E = I_C + I_B \Rightarrow \boxed{I_E = 2.02 \text{ mA}}$$

From the ckt,  $V_E - 0 = I_E \times 2$


$$\Rightarrow V_E = 4.04 \text{ V}$$

Again, from the ckt,  $10 - V_C = I_C \times 3$

$$\Rightarrow V_C = 4 \text{ V}$$

$$\begin{aligned} \therefore V_{CE} &= V_C - V_E \\ \Rightarrow \boxed{V_{CE} = 0.04 \text{ V}} \end{aligned} \quad \left. \begin{array}{l} \text{Assumed ACTIVE, found} \\ V_{CE} < 0.2 \text{ V. So } \underline{\text{assumption}} \\ \underline{\text{WRONG!}} (- -) \end{array} \right.$$

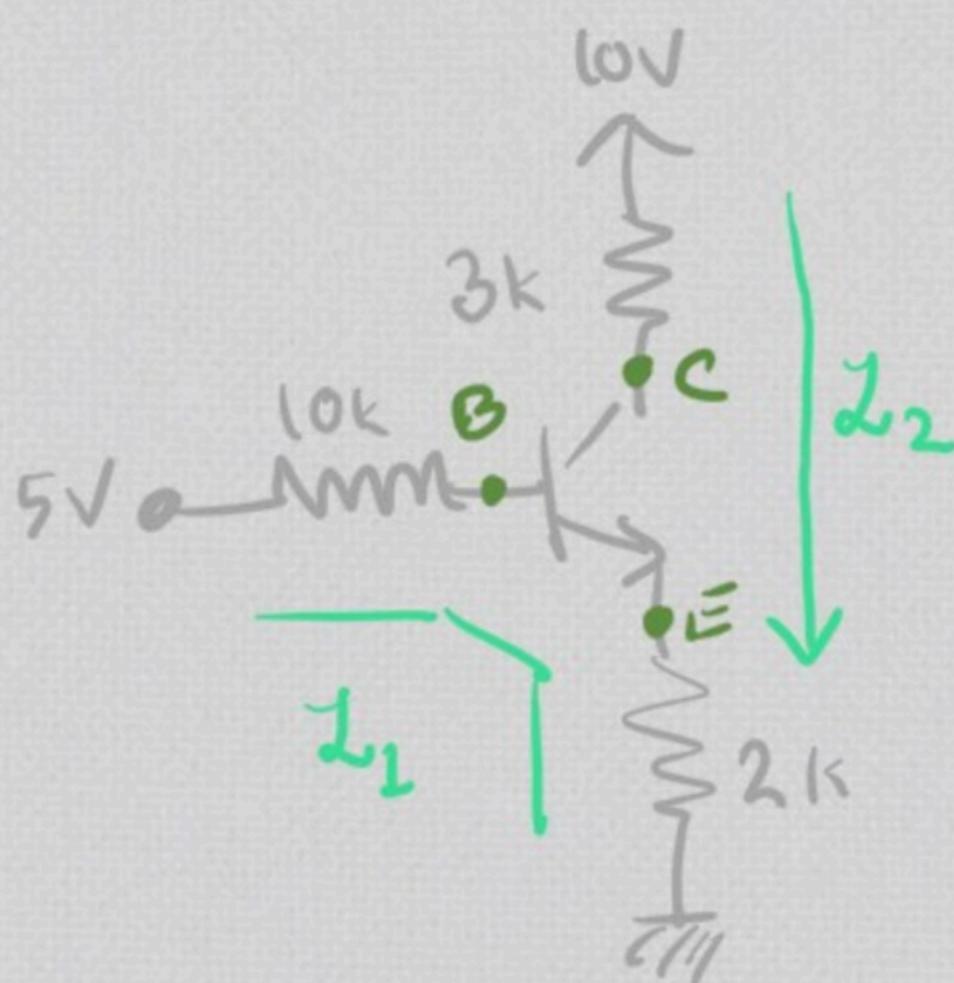Assume in SATURATION  $\Rightarrow \boxed{\therefore V_{CE} = 0.2 \text{ V}}$



KVL along  $Z_1$

$$5 = 10I_B + V_{BE} + 2I_E$$

$$\Rightarrow 5 = 10I_B + 0.8 + 2I_E \quad \text{--- (I)}$$

KVL along  $Z_2$

$$10 = 3I_C + V_{CE} + 2I_E$$

$$\Rightarrow 10 = 3I_C + 0.2 + 2I_E \quad \text{--- (II)}$$

PTO

From KCL  $\Rightarrow$

$$I_E = I_B + I_C \quad \text{--- (iii)}$$

Solving (i), (ii) and (iii)


$$I_B = 0.03 \text{ mA}$$

$$I_C = 1.95 \text{ mA}$$

$$I_E = 1.98 \text{ mA}$$

Since  $\frac{I_C}{I_B} = \frac{1.95}{0.03} < \beta$ , so assumption CORRECT!


Example 3 :

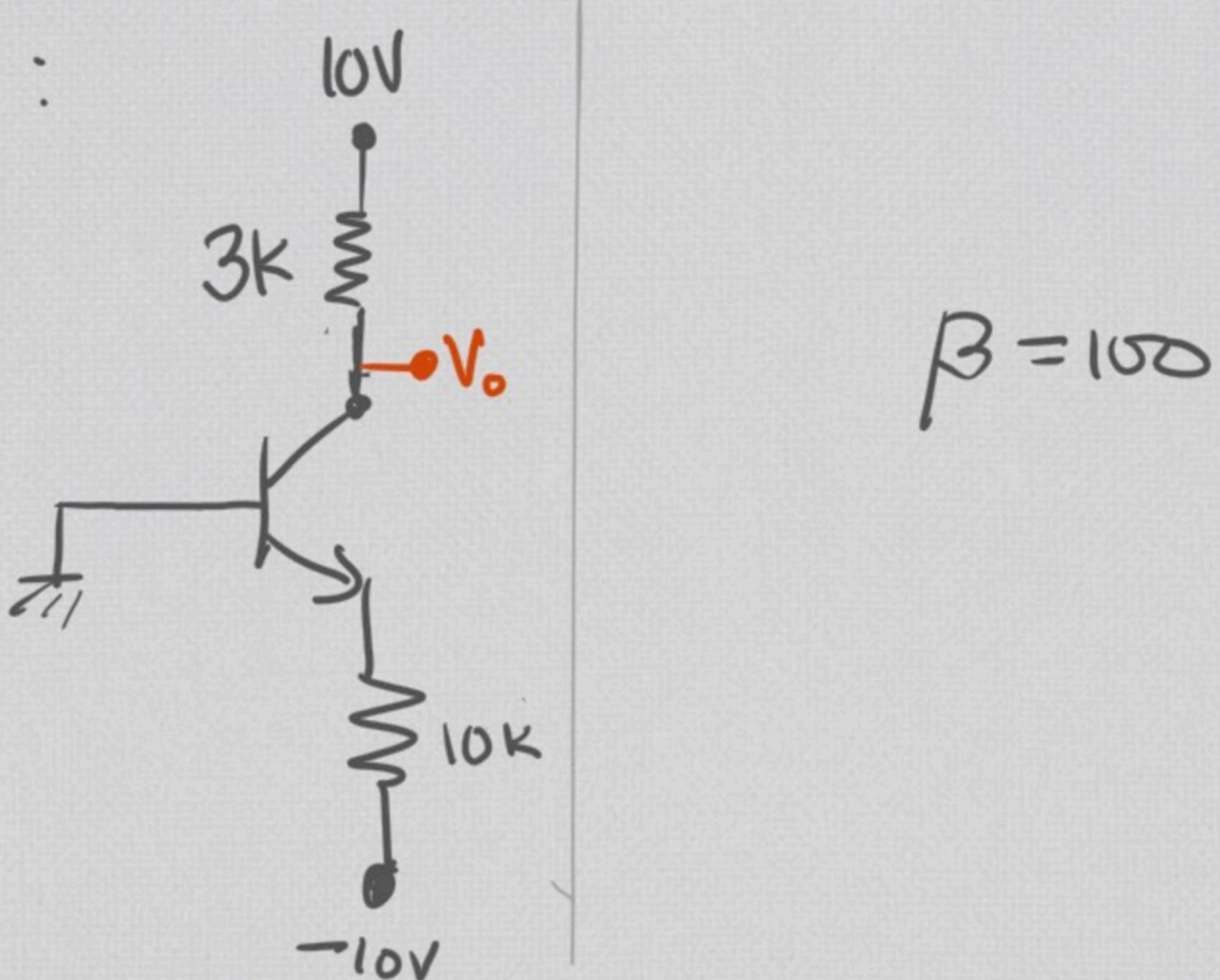

$$\beta = 100$$

find  $I_B$ ,  $I_c$ ,  $I_E$  and  $V_o$

Sol'n :

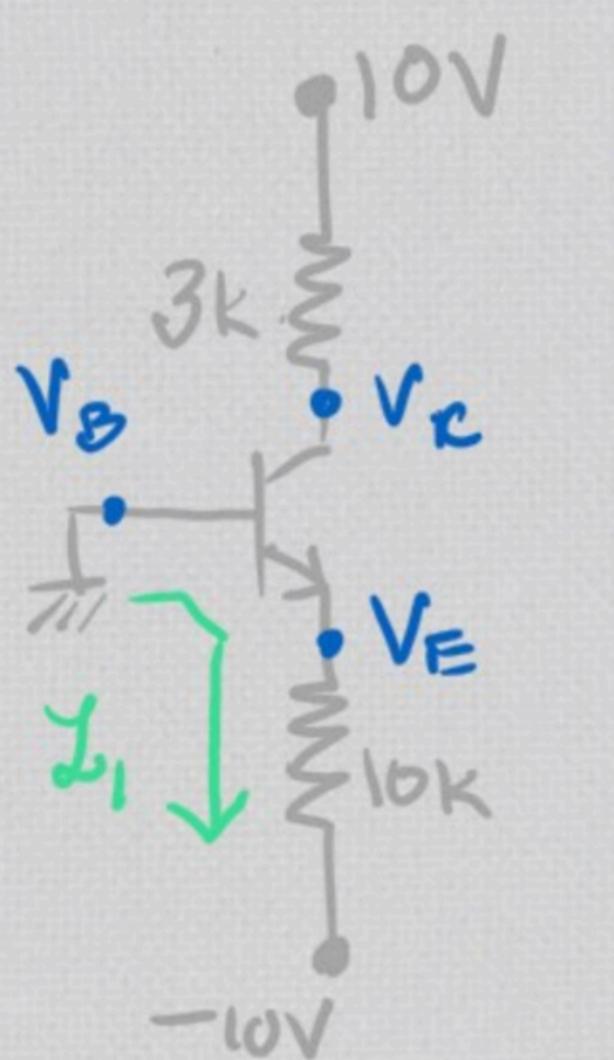

Base connected to GND

$$\therefore V_B = 0V$$

Assume BJT ACTIVE

$$\therefore V_{BE} = 0.7V$$

$$\Rightarrow V_B - V_E = 0.7V$$

$$\Rightarrow V_E = -0.7V$$

$$\boxed{\begin{aligned} \beta &= 100 \\ \therefore \alpha &= \frac{1+\beta}{\beta} \\ &= 0.99 \end{aligned}}$$

KVL along  $Z_2$ :  $0 = V_{BE} + 10I_E + (-10)$

$$\Rightarrow 0 = 0.7 + 10I_E - 10$$

$$\Rightarrow \underline{I_E = 0.93mA}$$

$$\therefore \underline{I_c = \alpha I_E = 0.99 \times 0.93 \Rightarrow I_c = 0.92mA}$$

$$\therefore \underline{I_B = I_E - I_c \Rightarrow I_B = 0.01mA}$$

From CKT,  $10 - V_C = 3I_C$

$$\Rightarrow \underline{\underline{V_C = 7.24V}}$$

Check:  $V_{CE} = V_C - V_E = 7.24 - (-0.2)$

$$\Rightarrow V_{CE} = 7.94V$$

$\therefore V_{CE} > 0.2 \Rightarrow \underline{\underline{\text{Assumption Correct!}}}$